



RM-6503

B. E. II (Sem. IV) (Ele.) Examination

May / June – 2010

Electronics Circuit - II

Time : 3 Hours]

[Total Marks : 100

Instruction :

(1)

नीचे दशावेल निशानीवाणी विगतो उत्तरवही पर अवश्य लभवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
B. E. 2 (Sem. 4) (Ele.)	<input type="text"/>
Name of the Subject :	<input type="text"/>
Electronics Circuit - 2	<input type="text"/>
Subject Code No. : <input type="text"/> 6 <input type="text"/> 5 <input type="text"/> 0 <input type="text"/> 3	Section No. (1, 2,.....) : <input type="text"/> 1&2
	Student's Signature


SECTION - I

- (2) Attempt **all** questions.
- (3) Assume suitable data whenever **necessary**.
- (4) Figures to **right** indicate full marks.
- (5) Use of scientific calculator (fx-82 100 W MS-82 F-100MS) is permitted.


1 (a) Answer the following questions :

- (i) The Darlington amplifier provides _____ i/p **1**
impedance and _____ current gain. (High-High,
Low-High)
- (ii) A differential amplifier has differential mode gain **2**
of 100 and common mode gain of 0.01. Calculate
its CMRR in dB.
- (iii) What is the difference between oscillator and **1**
amplifier?

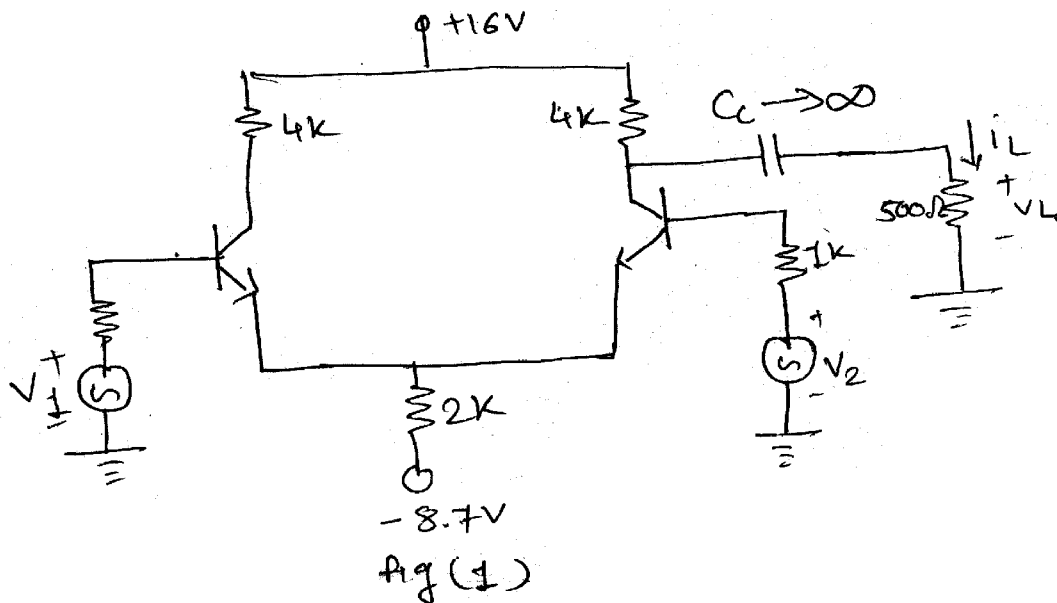- (iv) In RC phase shift oscillator each RC n/w provides _____° phase shift (0°, 30°, 60°, 180°). 1
- (v) For Hartley oscillator $f_o =$ _____. 1
- (vi) For colpits oscillator $f_o =$ _____. 1
- (vii) Draw the current shunt P voltage shunt topology. 2
- (viii) For ideal amplifier $R_i =$ _____ (0, ∞) 1
- (b) Draw cascade (CE-CB) amplifier. 2
- (c) In **fig. 1**, the transistors are identical with $h_{fe} = 100$, $h_{re} = h_{oe} = 0$. 8
- (i) Find $I_{E_{Q1}}$, $I_{E_{Q2}}$, assuming the dc common mode voltage is negligible.
- (ii) Find A_d , A_a , CMRR.



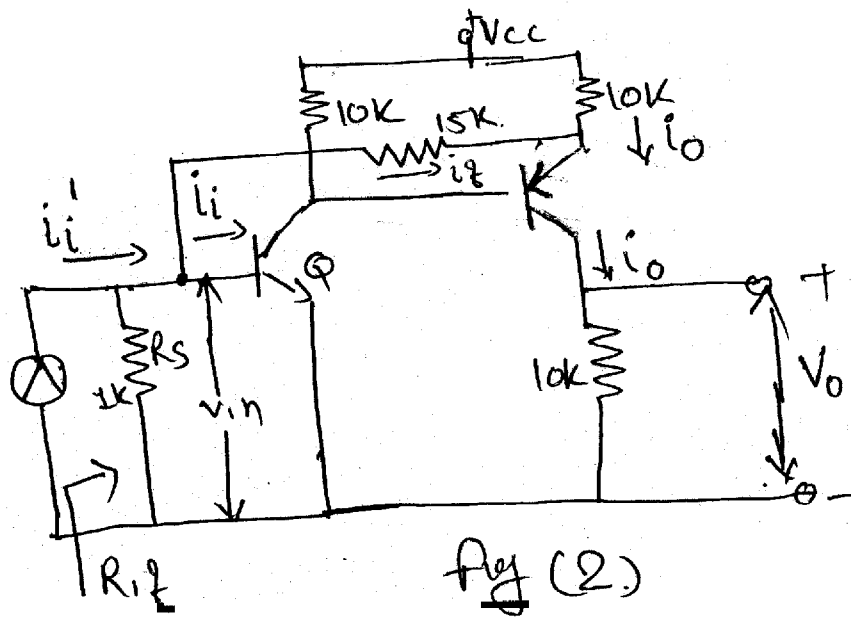- 2 (a) In the two stage feedback amplifier shown in **fig. 2** the transistors are identical and have the following parameters: $h_{fe} = 50$, $h_{ie} = 2k$. Calculate 8
- (i) $A_{if} = \frac{i_0}{i_s}$ (ii) $R_{if} = \frac{V_i}{i_0}$ (iii) $A_{if'} = \frac{i_0}{i_i}$
- (iv) $A_{vf} = \frac{V_0}{V_s}$ where $V_s = i_s R_s$.



- (b) List the advantages and disadvantages of negative feedback. 7

OR

- 2 (a) For the transistor feedback amplifier stage shown in **fig. 3** $h_{fe} = 100$, $h_{ie} = 1k$, determine with emitter resistor by passed by C_e : 10

(i) $R_{MF} = \frac{V_0}{i_s}$ where $i_s = \frac{V_s}{R_s}$


(ii) $A_{vf} = \frac{V_0}{V_s}$

(iii) R_{if}

(iv) R_{of}

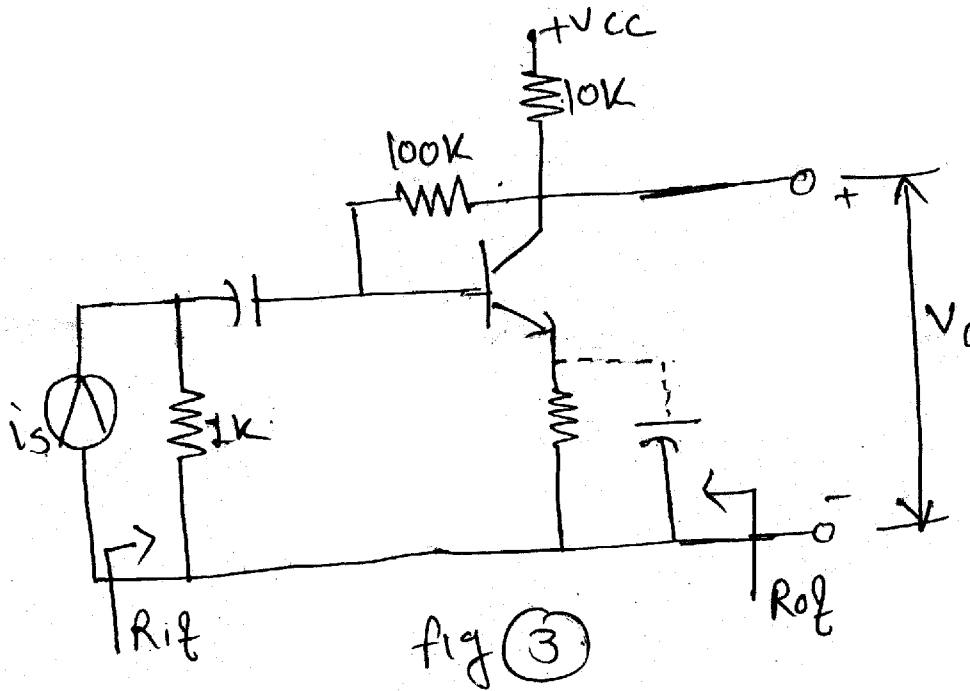- (v) Repeat the four

preceding calculations if emitter resistance is unbypassed.



- (b) For voltage series feedback obtain the expressions for input resistance R_{if} . 5
- 3 (a) Explain Wein bridge oscillator and derive the frequency of oscillation. 8
- (b) Explain Hartley oscillator and derive the frequency of oscillation. 7
- OR
- 3 (a) Explain RC phase shift oscillator and derive the frequency of oscillation. 8
- (b) Explain Colpitt's oscillator and derive the frequency of oscillation. 7

SECTION - II

- 4 (a) Do as directed : 10
- (i) Explain what do you mean by frequency response of an amplifier.
- (ii) Define pulse input.
- (iii) What capacitors affect the gain at high frequency ?

- (iv) Explain clipping.
 - (v) Clamping circuit is known as DC restorer circuit. State true or false.
 - (vi) MOSFET stands for _____.
 - (vii) After pinch off voltage _____ becomes constant (current, voltage)
 - (viii) Draw the symbol of P - channel JFET.
 - (ix) For N-channel JFET the gain to source voltage is positive. State true or false.
 - (x) Draw the frequency response of RC coupled amplifier.
- (b) (i) Draw and explain construction and transfer characteristic of P-channel JFET. 6
- (ii) Explain ramp input in high pass RC circuit. 4
- 5 (a) For the CE amplifier in the **fig. 4** calculate the mid-frequency voltage gain and lower 3-dB point. The circuit details are $R_s = 600 \Omega$, $R_L = 5 K \Omega$, $R_E = 1k\Omega$, $V_{CC} = 12V$, $R_1 = 15 k\Omega$, $R_2 = 2.2 k\Omega$, $C_e = 50 \mu F$. Draw the bode plot $h_{ie} = 1k\Omega$, $h_{fe} = 50$. 7

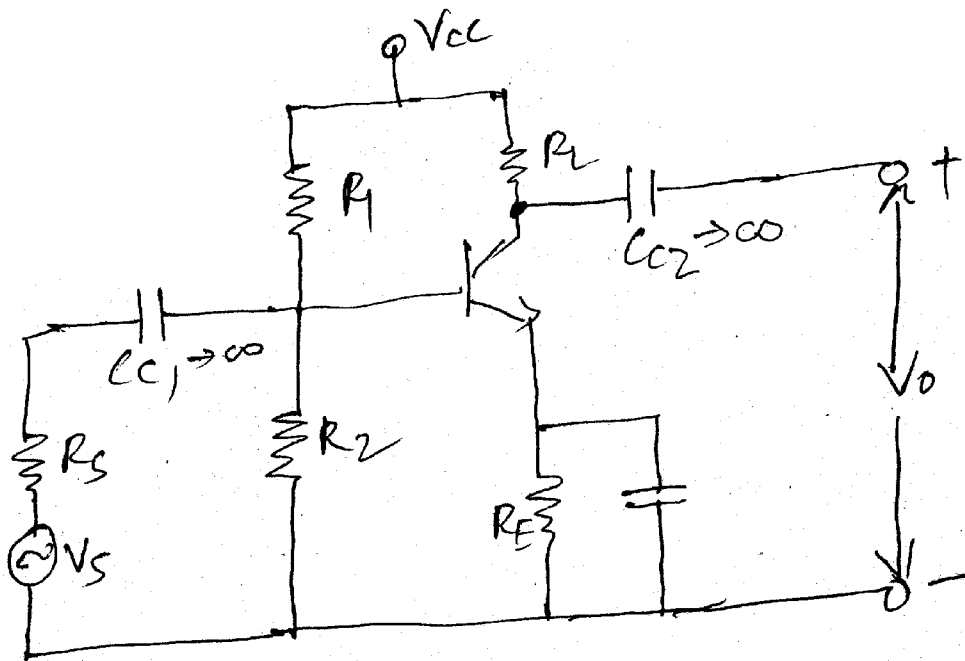


Fig. 4

- (b) Obtain transfer characteristic for **fig. 5** below. Assume 7
ideal diodes. Sketch the output if $V_i = 150 \sin \omega t$.

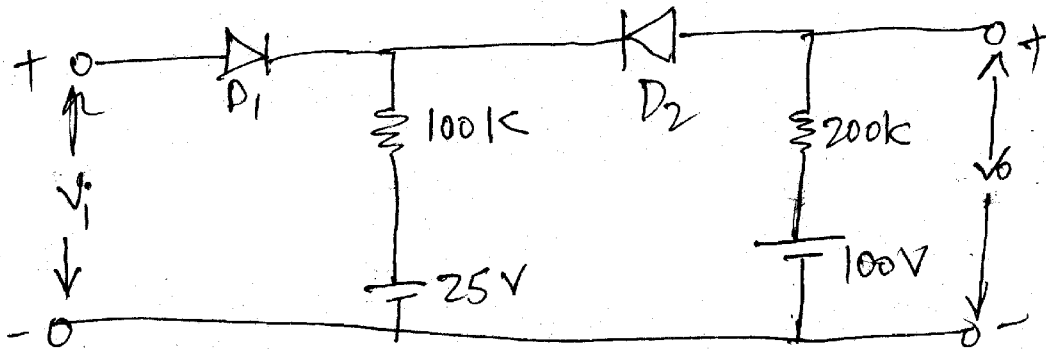


Fig. 5

OR

- 5 (a) Draw and explain the response of square wave to 7
the RC low pass circuit.
- (b) Obtain transfer characteristic for the circuit shown 8
below. Assume ideal diodes. Sketch output for
 $V_i = 40 \sin \omega t$.

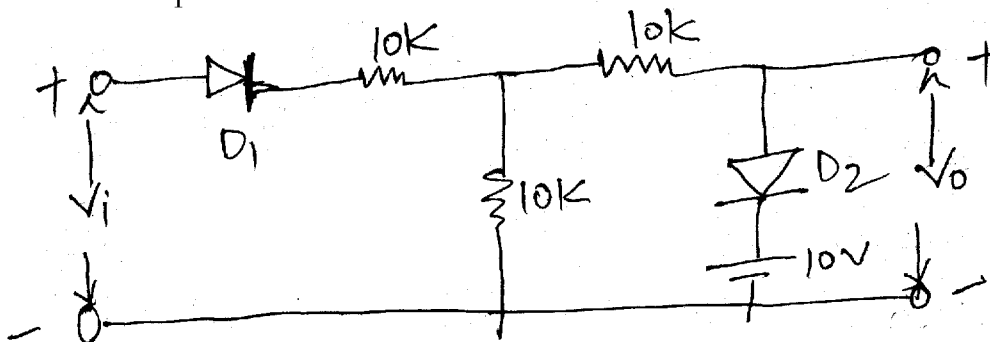


Fig. 6

- 6 Attempt any **three** : 15
- (i) State and prove clamping circuit theorem.
- (ii) The amplifier shown in the figure below is to have lower 3dB frequency at 20Hz. Select C_{C1} , C_{C2} and C_e to meet specifications for BJT $h_{fe} = 100$, $h_{ie} = 1 \text{ k} \Omega$.

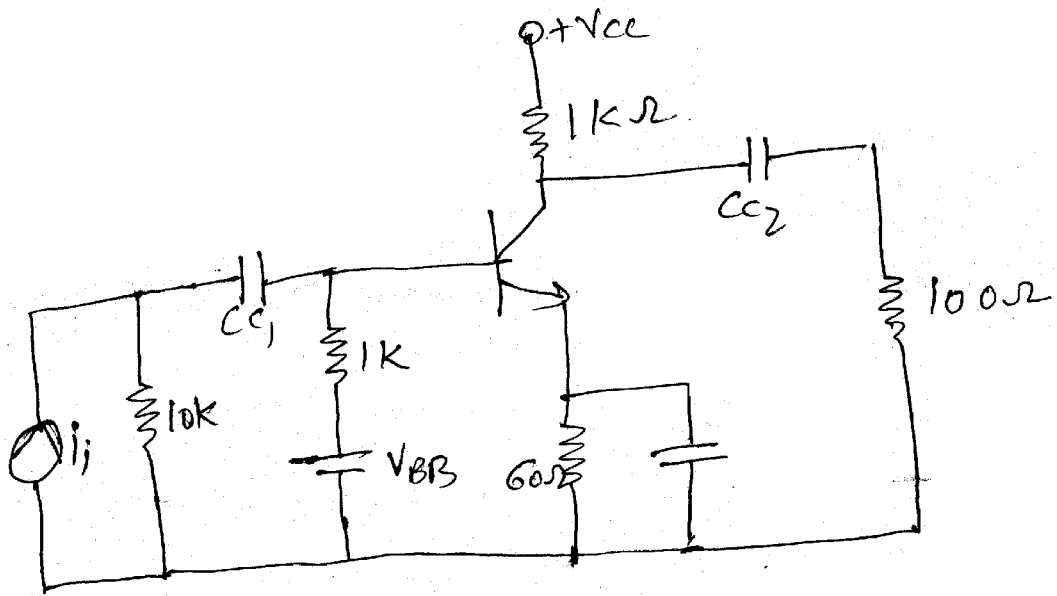


Fig. 7

- (iii) Write short note on comparators.
- (iv) Explain Enhancement MOSFET.