



RM-6525

B. E. II (Sem. IV) (IC) Examination

May / June – 2010

Pulse & Switching Circuit

Time : 3 Hours]

[Total Marks : 100

Instruction :

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. 2 (Sem. 4) (IC)

Name of the Subject :
Pulse & Switching Circuit

Subject Code No. : 6 5 2 5 Section No. (1, 2,.....): 1&2

Seat No. :

Student's Signature

- (2) Attempt all questions.
- (3) Figures to the **right** indicate full marks.
- (4) Assume suitable data wherever **necessary**.
- (5) Answers to the **two** sections must be written in **separate** answer books.

- 1 (a) Answer the following : 10
- (i) The waveform which preserves its form when transmitted through linear network is _____.
 - (ii) Diode clippers are used only for one level clipping _____. (True/False)
 - (iii) The lower cut-off frequency of a low pass circuit is _____.
 - (iv) A high pass circuit acts as a _____ if the time constant of the circuit is very small in comparison with the time required for the input signal to make an appreciable change.
 - (v) Clipping circuits require non-linear elements _____. (True/False)
 - (vi) Clipping circuits are _____ comparators.
 - (vii) The _____ circuit is often referred to as dc restorer.
 - (viii) Energy storage elements are must for clipping circuits _____. (True/False)
 - (ix) In _____ clamping the negative extremity of the waveform is fixed at the reference level and the entire waveform appears above the reference.
 - (x) A signal which maintains the value zero for all times $t < 0$ and maintains the value V for all times $t \geq 0$ is called a _____.

- (b) With the help of a neat circuit diagram explain the working of a two-level diode clipper. 6
- (c) Explain the clamping theorem. 4
- 2 (a) A 10 Hz symmetrical square wave whose peak to peak amplitude is 2V is impressed upon a high-pass RC circuit whose lower 3 dB frequency is 5 Hz. Calculate and sketch the output waveform for the first two cycles. What is the peak-to-peak output amplitude under steady-state conditions? 10
- (b) Draw the transfer characteristics for the circuit shown in figure 1. Also draw the output waveform for a sinusoidal input of amplitude 20 V peak. 5

 


fig.1.

OR

- 2 (a) In the clamping circuit shown in figure 2 $R_s = 100 \Omega$, $R_f = 50 \Omega$, $R = 20 k \Omega$ and $C = 2 \mu F$. A symmetrical square wave signal of amplitude 20 V and frequency 5 kHz is applied at $t=0$. Draw the first three cycles of the output waveform. 10

 


fig.2

- (b) For sinewave input to the clipper circuit shown in figure 3 and figure 4, plot output voltage waveform. 5

 


fig.3


 


fig.4

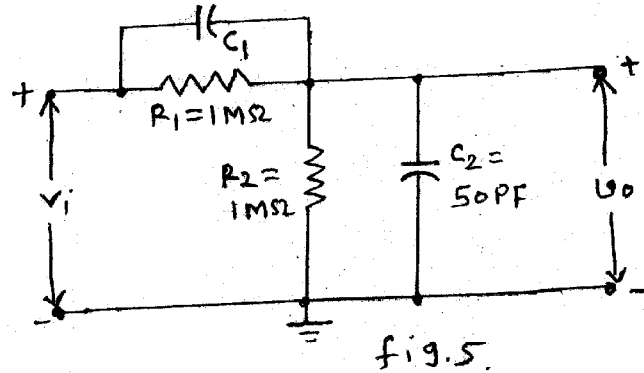
- 3 (a) Compute and draw to scale the output waveform for (a) $C_1 = 50 \text{ PF}$, (b) $C_1 = 75 \text{ pF}$ and (c) $C_1 = 25 \text{ pF}$ respectively for the circuit shown in figure 5. The input is a 20 V step. 8



 - (b) Derive the expression for the percentage tilt for the square input, which is applied to high pass RC circuit. 7

OR

- 3 (a) Assuming that the capacitor is initially uncharged, determine the output response of the low-pass RC circuit with time constant 0.05 mS, to the input waveform shown in figure 6. 10



- (b) Design a diode clamper to restore a dc level of +5V to an input signal of peak to peak value of 20 V. 5

SECTION - II

- 4 (a) Attempt the following : 10
- (i) During transition, the loop gain is _____.
 - (ii) The _____ multivibrator is used as a master oscillator.
 - (iii) _____ triggering is used in binary counting circuits.
 - (iv) Two or more generators are said to be running _____ if all of them arrive at some reference point in the cycle at exactly the same instant of time.
 - (v) When generators with equal frequencies run in synchronism, the synchronization is said to be on a _____.

- (vi) Counting circuits are an examples of synchronization with _____.
- (vii) The reciprocal of the resolving time of the flip-flop is the _____ at which the binary will respond.
- (viii) What is the use of collector catching diodes?
- (ix) Define blocked condition.
- (x) Define resolving time.

- (b) Explain non saturating binary. 5
- (c) Explain triggering symmetrically through a unilateral device 5

- 5 (a) For a circuit diagram shown in figure 7
 $V_{CC} = V_{BB} = 6 \text{ V}$, $R_c = 1.2 \text{ k}\Omega$, $R_1 = 4.7 \text{ k}\Omega$,
 $R_2 = 27 \text{ k}\Omega$. Find $h_{FE}(\text{min})$ and stable state voltages and currents. Take $V_{CE}(\text{sat}) = 0.5 \text{ V}$, $V_{BE}(\text{sat}) = 1\text{V}$.

 


Fig. 7

- (b) Write a short note on DCTL. 5

OR

- 5 (a) Derive the expression of gate width T of a monostable multivibrator by neglecting the reverse saturation current I_{CBO} . 5
- (b) Silicon transistors with $h_{FE}(\text{min})$ equal to 20 are available. If $V_{CC}=V_{BB} = 10 \text{ V}$, design the bistable multivibrator. 10

- 6 (a) Design a Schmitt trigger circuit to have $V_{CC} = 12 \text{ V}$, $U_{TP} = 6\text{V}$, $L_{TP} = 3\text{V}$, using two silicon n-p-n transistors with $h_{FE}(\text{min}) = 60$. Take $I_{C2} = 2\text{mA}$ and $V_{r1}=0.5 \text{ V}$. 8
- (b) Draw and explain collector coupled monostable multivibrator. 7

OR

- 6 (a) Silicon n-p-n transistor with $h_{FE}(\text{min}) = 40$ are available. Design an astable multivibrator to generate a square wave 1 kHz frequency with a duty cycle of 25%. 8
- (b) Explain the working of Emitter coupled astable multivibrator with the help of circuit diagram and waveform. 7