



**RM-6541**

**B. E. II (Sem. IV) (IT) Examination**

**April / May – 2010**

**Electronics - II**

Time : Hours]

[Total Marks : 100

**Instruction :**

(1)

नीचे दृशविले निशानीवाणी विगतो उत्तरवही पर अवश्य लपवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
B. E. 2 (Sem. 4) (IT)

Name of the Subject :  
Electronics - 2

Subject Code No. : 6 5 4 1 Section No. (1, 2,.....): 1&2

Seat No. :  
[ ] [ ] [ ] [ ] [ ] [ ]

Student's Signature

- (2) Figures to the **right** indicate full marks.  
(3) Assume **necessary** data wherever **necessary**.  
(4) Draw neat and clean circuit diagrams.

**SECTION - I**

- 1 (a) Fill in the blanks. 10
- (i) Transfer function for voltage series is \_\_\_\_\_.
- (ii) Efficiency of class-B push-pull power amplifier is \_\_\_\_\_.
- (iii) Distortion with negative feedback \_\_\_\_\_.
- (iv) Desensitivity D for voltage shunt is expressed as \_\_\_\_\_.
- (v) Input impedance of current shunt amplifier with feedback \_\_\_\_\_.
- (vi) 7912 IC gives us \_\_\_\_\_ as output voltage.
- (vii) Efficiency of class A transformer coupled power amplifier is \_\_\_\_\_.
- (viii) 79xx ICS are \_\_\_\_\_ voltage regulator.
- (ix) Figure of merit defined as \_\_\_\_\_.
- (x) Distortion with -ve Feedback \_\_\_\_\_.
- (b) Plot the output waveforms of class A, B and C power amplifier. Write your comments regarding waveforms. 4

- (c) A transformer coupled class-A power amplifier draws a current of 200 mA from a collector supply of 10 V. when no signal is applied to it. Determine
- Maximum output power
  - Maximum collector efficiency
  - Power rating of the transistor.
- 2 (a) Derive the expression for current series amplifier for its gain, input impedance and output impedance with feedback. 8
- (b) Find the topology for the circuit shown in **fig. 1**. Also find out ac. voltage  $v_i$  as a function of  $v_s$  and  $v_f$ . Assume that the inverting amplifier input resistance is infinite and  $A = A_v = -1000$ ,  $B = V_f/V_j = 1/100$ ,  $R_S = R_C = R_E = 1k$ ,  $h_{fe} = 100$ . Also find  $A_{vf} = V_o/V_s$ . 8

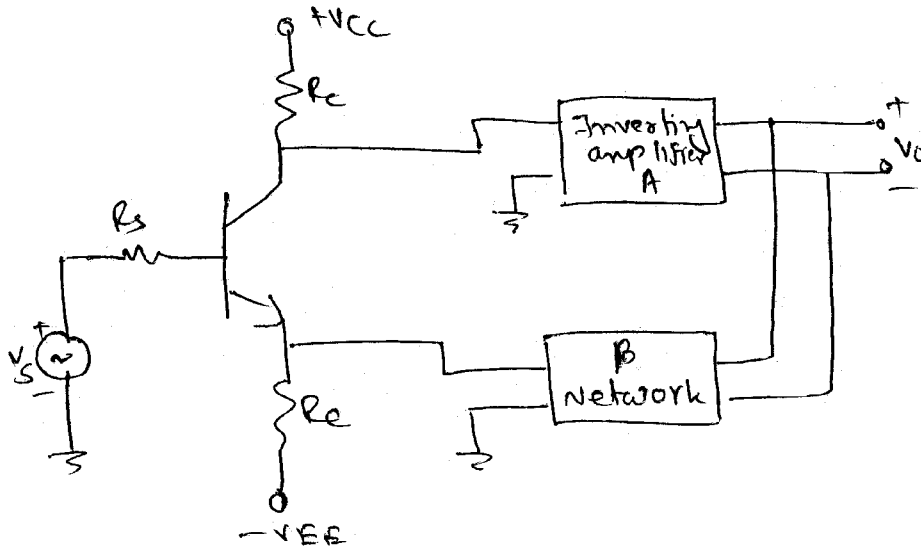


Fig. 1

OR

- 2 (a) Explain the basic block diagram of feedback amplifier. Also, list steps to recognize the type of topology of given feedback amplifier. 8
- (b) The transistor in the feedback amplifier shown in **figure 2** are identical having  $h_{ie} = 1.1 k$ ,  $h_{fe} = 50$ . Calculate (i)  $A_{if}$  (ii)  $A_{vf}$  (iii)  $R_{if}$  and (iv)  $R_{of}$  8

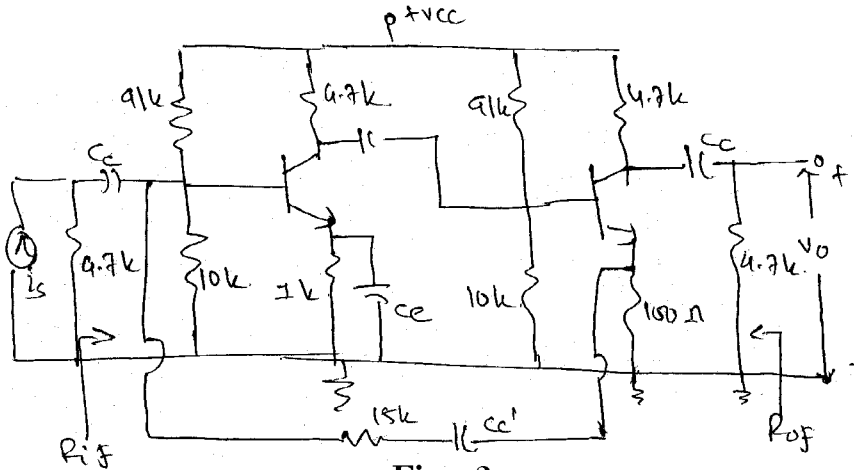


Fig. 2

- 3 Attempt any **three** : 15
- Explain following related to voltage regulation
    - Line regulation
    - load regulation
    - Ripple rejection.
  - Explain the design of a low voltage regulator using 7C 723.
  - Explain foldback current limiting.
  - Design a current source using 7805 regulator.

### SECTION - II

- 4 (a) Do as directed :
- Define : Slew rate, PSRR.
  - Explain virtual ground concept in an op-amp.
  - Define : line regulation, load regulation
  - Draw the 555 timer functional block diagram.
  - Applications of 555 timer.
- (b) Explain voltage series feedback amplifier. 8
- OR**
- (b) Draw the ckt. diagram for integrator and explain the same. 8
- 5 (a) Draw the ckt diagram for the instrumentation amplifier and explain the same. 8
- OR**
- (a) Explain the first order high pass butterworth filters. 8
- (b) Explain the working of monostable multivibrator using op-amp and obtain the expression for the output pulse width and recovery time. 8
- OR**
- (b) Explain RC phase shift oscillator. 8
- 6 Attempt any **two** : 16
- Phase locked loop
  - Triangular wave generator
  - SMPS
  - Protection circuitry for voltage regulators.