



**RN-6125**

**B. E. - II (Sem. III) (Chemical) Examination**  
**May / June - 2010**  
**Basic Electronics**

Time : 3 Hours]

[Total Marks : 100

**Instructions :**

(1)

नीचे दशावेव निशाचीवाणी विगतो उत्तरवडी पर अवश्य वपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<b>B. E. - 2 (Sem. 3) (Chemical)</b>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<b>Basic Electronics</b>	<input type="text"/>
Subject Code No. : <input type="text"/> 6 <input type="text"/> 1 <input type="text"/> 2 <input type="text"/> 5	Section No. (1, 2,.....) : <input type="text"/> 1&2
	Student's Signature

- (2) Attempt all questions.  
(3) Figures to the right indicate full marks.  
(4) Assume suitable data wherever necessary and specify your assumption clearly.

- 1 (a) Answer the following : 10
- (i) A bridge type rectifier has \_\_\_\_\_ diodes.  
(ii) A pentavalent impurity has \_\_\_\_\_ valence electrons.  
(iii) Define :  
(a) PIV  
(b) Filters  
(c) Cut in voltage  
(iv) At room temperature, an intrinsic semiconductor acts as \_\_\_\_\_.  
(v) A zener diode is used as a \_\_\_\_\_.  
(vi) The ripple factor of a half wave rectifier is \_\_\_\_\_.  
(vii) The relation between B and D is \_\_\_\_\_.  
(viii) In a transistor, signal is transferred from a \_\_\_\_\_ circuit.
- (b) Explain half wave rectifier and derive equation for its efficiency. 6
- (c) Define filter and compare various filters. 4

2	(a)	Explain with the help of neat diagram transistor working as an amplifier.	8
	(b)	Describe with the characteristics, the voltage stabilization of zener diode.	7
<b>OR</b>			
2	(a)	Define biasing of transistor. List the various methods of biasing and explain voltage divider biasing.	8
	(b)	Describe the working of following filters	7
		(i) Capacitive filter	
		(ii) $\pi$ filter.	
3		Write short notes on : (any <b>three</b> )	15
	(i)	Comparison of CE, CB, CC configuration of transistor.	
	(ii)	Classification of amplifiers	
	(iii)	Uni-junction transistor	
	(iv)	Push pull amplifier.	


## SECTION - II

4	(a)	(i) An astable multivibrator_____	1
		(a) Gives one output pulse for every two input pulse.	
		(b) Give a timed output pulse for trigger input.	
		(c) Gives a train of output pulses for trigger input.	
		(d) Gives four output pulses for single input pulse.	
	(ii)	The electrons emitted by a thermionic emitter are called _____.	1
		(a) Free electron	
		(b) Loose electron	
		(c) Thermionic electron	
		(d) Bound electron	
	(iii)	In signal generators energy is converted from simple _____ source into _____ energy at some specific frequency.	2
	(iv)	Define work function.	2
	(v)	What is full form of LED?	2
	(vi)	What is deflection sensitivity of CRT?	2
	(b)	(i) List various devices used for measurement of temperature.	4
		(ii) What is field emission?	3
		(iii) Give merits and demerits of multimeter.	3

- 5 (a) What is secondary Emission? Explain with labelled diagram. 7  
 (b) Explain function of internal parts of CRT with diagram. 8

OR

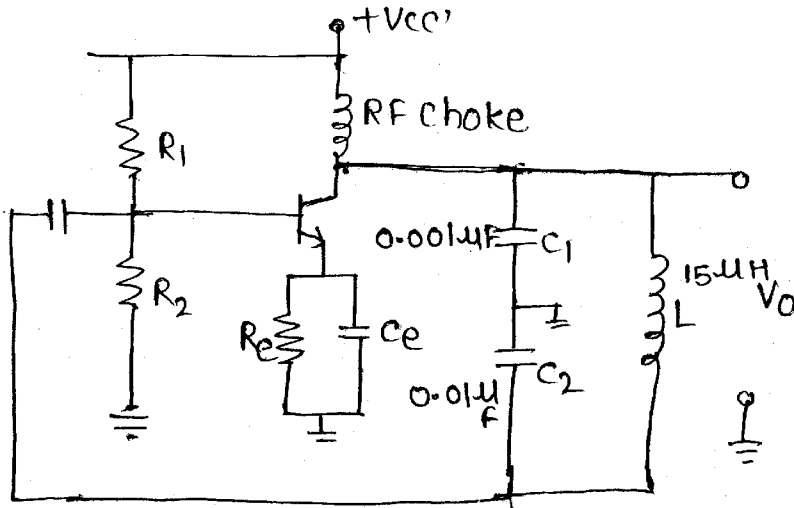- 5 (a) Determine frequency of oscillation and feedback fraction for colpitts oscillator. 8  
 Given  $C_1 = 0.001$  Micro Faeade,  $C_2 = 0.01$  Micro faeade  
 $L = 15$  Micro henry



- (b) Explain Barkhausen criteria with neat block diagram. 7
- 6 Any three : 15  
 (i) Explain frequency measurement using CRO. 5  
 (ii) What is Photo Electric emission? Explain with diagram. 5  
 (iii) Write about Thermionic Emitter. 5  
 (iv) Write a note on photodiode with characteristics. 5