



RN-6203

B. E. II (Sem. III) (Electrical) Examination
May / June – 2010
Electronics-I

Time : Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दृशविले निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. 2 (Sem. 3) (Electrical)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Electronics-1"/>	<input type="text"/>
Subject Code No. : <input type="text" value="6"/> <input type="text" value="2"/> <input type="text" value="0"/> <input type="text" value="3"/>	Section No. (1, 2,.....) : <input type="text" value="1&2"/>
	<input type="text" value="Student's Signature"/>

- (2) Attempt all questions.
- (3) Assume suitable data wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Use scientific calculator casio FX-82, 83, 100 or equivalent of any other company.

SECTION - I

- 1 (a) Answer the following in brief : 10
- (i) What is meant by the term "Barrier potential" ?
What are its values for Si and Ge diodes ?
 - (ii) Does temperature affect breakdown voltage of diode ? Explain it.
 - (iii) Define and explain the significance of Ripple and form factors in relation with the rectifying circuits.
 - (iv) Define and explain the significance of common emitter amplification factor B_{dc}
 - (v) Why is CE configuration preferred over the other configuration ?

(b) Answer the following : 10

- (i) For the circuit of Fig. 1, find $V_o(t)$ if $V_i(t)$ is
- Square wave with $\pm 10V$ amplitude
 - Sine wave with 1V peak. Assume Ideal diode

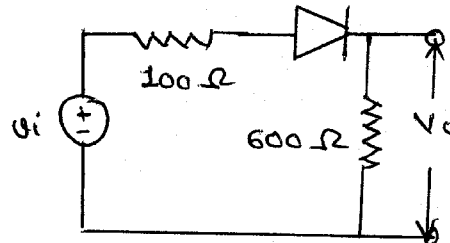


Fig. 1

- (ii) State the regions of operation of transistor and explain the biasing condition for the three regions.

- 2 (a) Draw the circuit diagram and explain the operation of a full wave rectifier and state its advantages and disadvantages 8
- (b) For the transistor shown in Fig. 2, $\beta = 100$, $I_{CO} = 20$ nA. Find the transistor currents and state in which region it is operating. Assume that it is a silicon transistor. 7

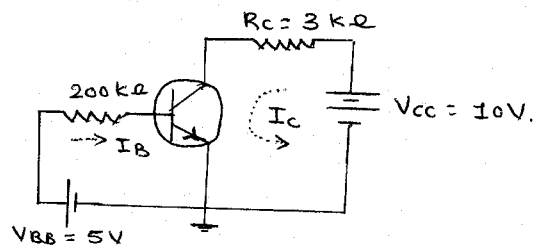


Fig. 2


OR

- 2 (a) Explain the function of emitter bypass capacitor. Draw AC and DC load lines for CE amplifier with bypass capacitors. 8
- (b) In a centre tapped full wave rectifier the rms half secondary voltage is 9V. Assuming ideal diodes and load resistance $R_L = 1k\Omega$ find : 7
- Peak current
 - DC load voltage
 - RMS current
 - Ripple factor
 - Efficiency.


- 3 Write short notes on : (any three) 15
- (i) Potential Divider Bias
 - (ii) Schottky diode
 - (iii) LC and PIE filters
 - (iv) Diode capacitance
 - (v) Input and output characteristic of NPN Transistor.

SECTION - II

- 4 (a) Answer the following : 10
- (i) Full form of BJT is _____.
 - (ii) True/False : BJT is current controlled device.
 - (iii) The reverse saturation current I_{CBO} approximately doubles for every _____.
 - (iv) The saturation drain current I_O in an FET is _____.
 - (v) True/False : Input impedance of JFET is greater than BJT but less than MOSFET.
 - (vi) The point of intersection of AC and DC load line is the _____.
 - (vii) Define amplification.
 - (viii) True/False : The maximum efficiency of class A power amplifier is 25%.
 - (ix) In class C amplifier Q point is well beyond the cut-off region. True/False.
 - (x) What is the main application of CC configuration of transistor?
- (b) (i) Explain working of class B push-pull power amplifier. Draw AC and DC load lines. 8
- (ii) Explain by graphical method how h_{oe} and h_{fe} parameters are obtained. 2
- 5 (a) Explain the effect of temperature on Q-point. 8
- (b) For the given ckt $h_{re} = h_{oe} = 0$, $50 < h_{fe} < 150$, calculate the range of A_i and Z_i to be expected. 8

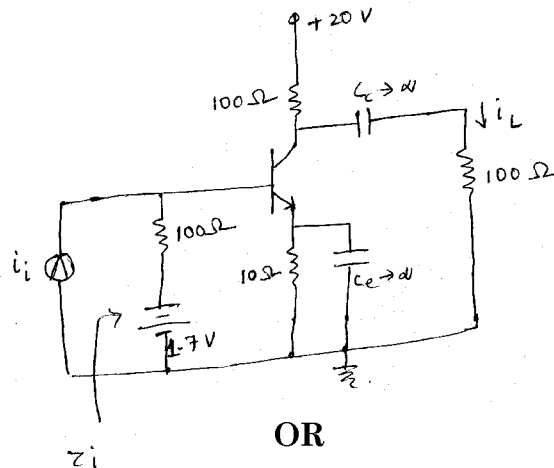

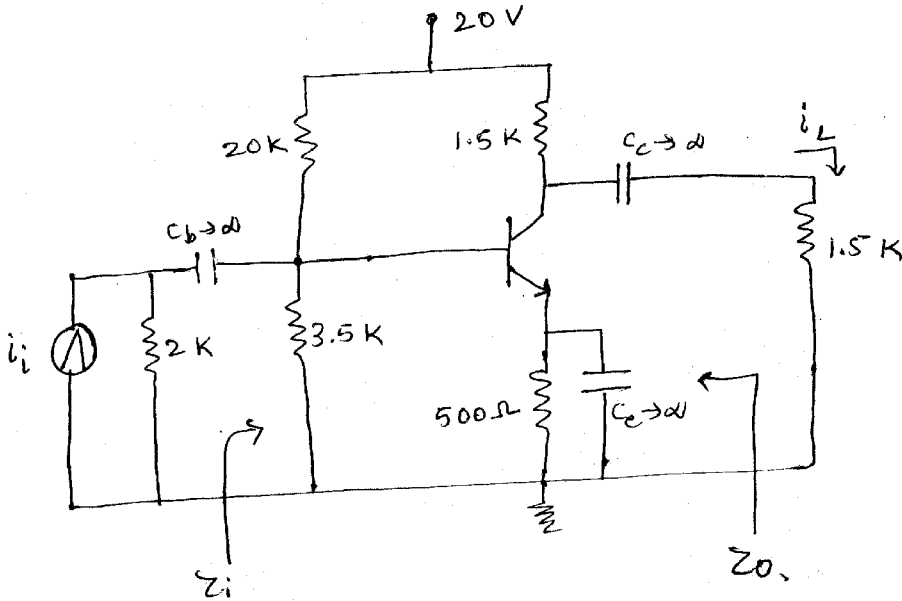- 5 (a) Explain n-channel FET and its characterisation. 8
 (b) For the Si transistor in figure $h_{fe} = 100$, $h_{re} = h_{oe} = 0$. 8
 Find h_{ie} , A_i , Z_i , Z_o .



- 6 Attempt any two : 14
 (i) Phase splitting ckt.
 (ii) Compare BJT and FET. Classify FET devices.
 (iii) Discuss the effect on Q-point due to variation in β .