



RN-6223

B. E. - II (Sem. - III) (I & C) Examination

May / June - 2010

Electrical Circuit Theory

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दशांशों में निशानीवाणी विगतो उत्तरवही पर अवश्य लिखनी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
B. E. - 2 (SEM. - 3) (I & C)

Name of the Subject :  
ELECTRICAL CIRCUIT THEORY

Subject Code No. : 6 2 2 3 Section No. (1, 2,.....) : 1&2

Seat No. :

Student's Signature

- (2) Attempt all questions.
- (3) Answer to the two sections must be written in separate answer book.
- (4) Assume necessary data and give sketches whenever necessary.
- (5) Use the graph paper and semilog paper whenever necessary.
- (6) Extreme right figures indicate full marks of the question.
- (7) Scientific calculator FX-100W or equivalent students may use.

### SECTION - I

- 1 (a) Do as directed :
  - (1) The input resistance of the network shown in fig. 1 is : 2

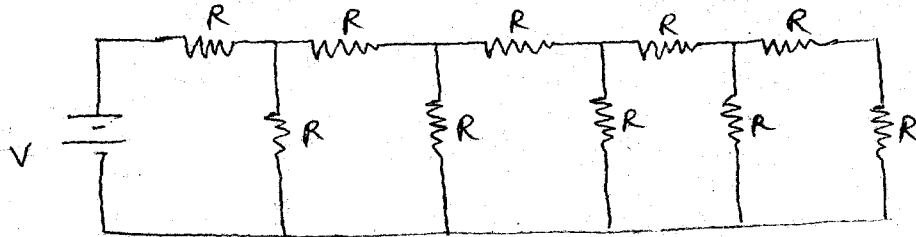


Fig. 1

- (2) Explain superposition theorem. 2
- (3) KCL is a consequences of law of conservation of energy. (True / False) 1
- (4) Distinguish between dependent and Independent sources. 2

(5) Match List - I with List - II : 3

**List - I**  
(Network Theory)

**List - II**  
(Most Distinguish  
property of network)

- (1) Reciprocity  
(2) Tellegen's

- (1) Impedance matching  
(2) Bilateral

- (3) Superposition

(3)  $\sum_{k=0}^b V_k(t_1) i_k(t_2) = 0$

- (4) Maximum power transfer

- (4) Linear

- (5) Non Linear

(b) Using node voltage analysis obtain  $V_1$  voltage for the network shown in fig. 2. 10

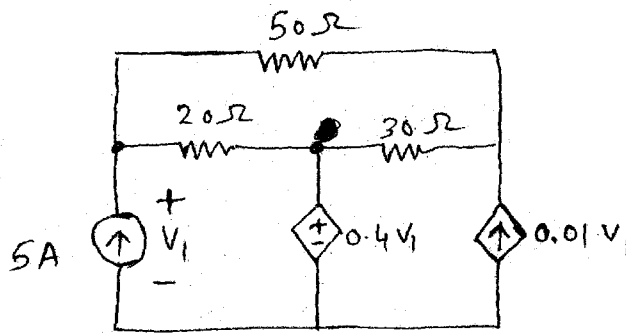


Fig. 2

2 (a) For the network shown in fig. 3, determine the current through the branch AB. 10


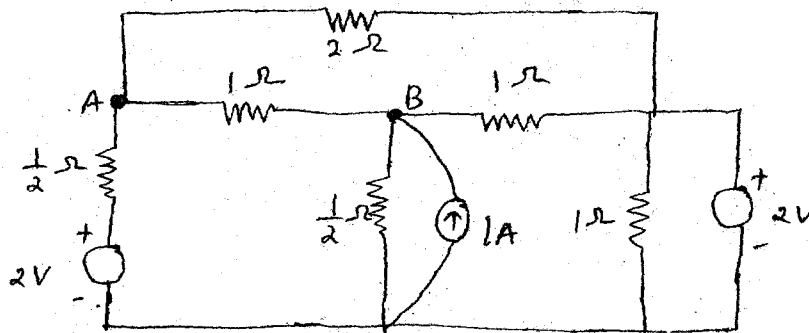


Fig. 3


- (b) Determine the current  $i_x$  for the network shown in **fig. 4**. 5

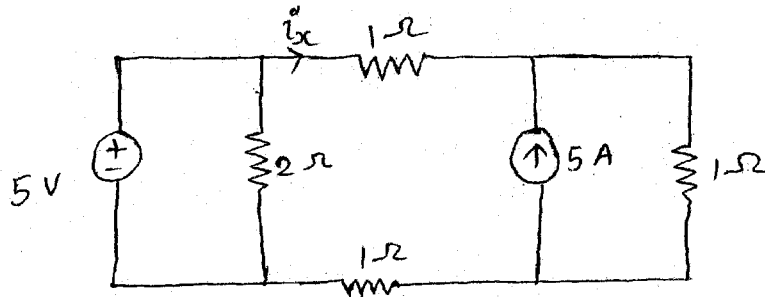

**Fig. 4**

OR


- 2 (a) For the network shown in **fig. 5** find the power consumed in each resistor and prove power supplied equal to power consumed using mesh current analysis. 12

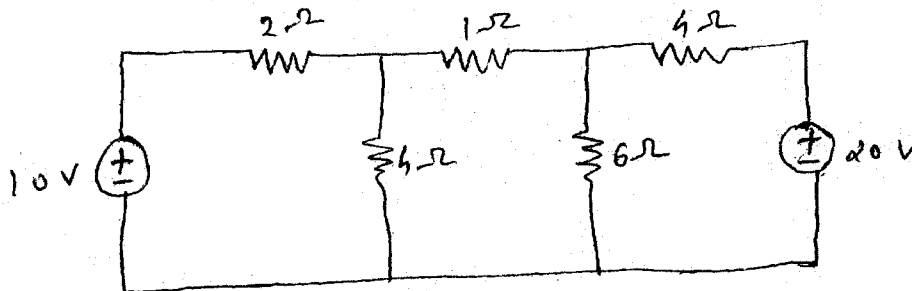

**Fig. 5**


- (b) Explain Reciprocity theorem. 3
- 3 Attempt any three out of following questions : 15
- (1) Explain the term mutual inductance and compare with self inductance of coil.
  - (2) What is duality ? How can be obtain dual of the network ? What is neat of duality.

- (3) Obtain dual of the given network shown in **fig. 6**.

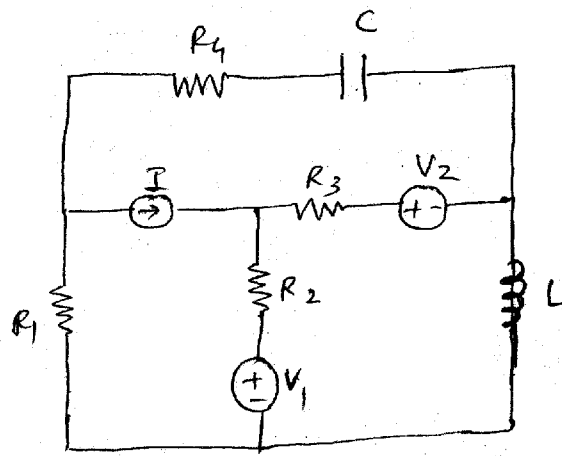

**Fig. 6**

- (4) Find the equivalent inductance of the three series connected coupled coils shown in **fig. 7**.

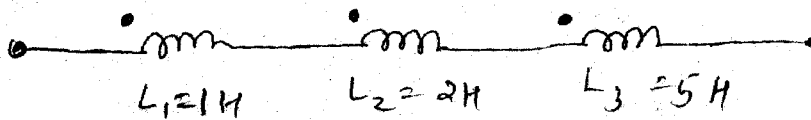


**Fig. 7**

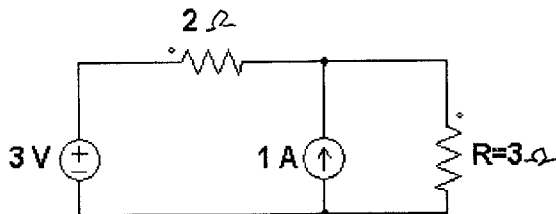- (5) For the mutually coupled coils prove the mutual inductance  $M = K\sqrt{L_1L_2}$ .

## SECTION – II

- Q-4(a)** Attempt *ALL*. (Each question carries equal marks) 10
- (1) Explain Dependent and Independent Energy sources.
  - (2) State and Explain Norton's theorem with suitable example.
  - (3) (a) Laplace Transformation of  $t^2$  is \_\_\_\_\_  
 (b) Laplace Transformation of  $\delta(t)$  is \_\_\_\_\_
  - (4) Find the current through Resistor R using Thevenin's theorem.



- (5) Define and explain Initial Value Theorem.
- Q-4(b)** Prove that the Laplace Transformation of  $f(t-a) * u(t-a)$  is given by  $e^{-as}F(s)$ . 5
- Q-4(c)** Find Inverse Laplace Transformation of using Partial Fraction Expansion method. 5


$$F(s) = \frac{(2s^2 + 3s + 2)}{(s^2 + 2s - 3)}$$

- Q-5(a)** For RLC circuit  $Y(s) = \frac{s}{(s^2 + 6s + 25)}$  7

Find

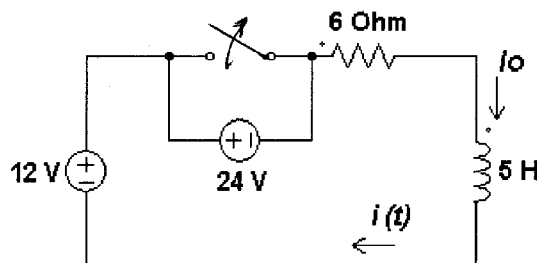- 1) Damping factor
- 2) Damping ratio
- 3) Actual frequency of oscillation
- 4) Bandwidth
- 5) Q- factor
- 6) Half power frequency
- 7) Pole-zero location


- Q-5(b)** Find the current in the circuit shown in the figure below at an instant  $t$ , after opening the switch if a current of 1 A had been passing through the circuit at the instant of opening. 8



OR

**Q-5(b)** Draw and explain the Impulse response of series RC network using Laplace Transform.


8

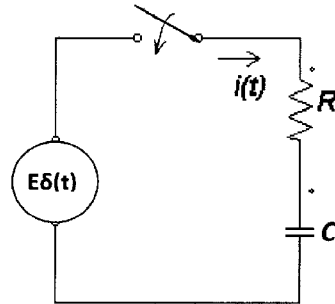

**Q-6** Attempt ANY THREE.

15

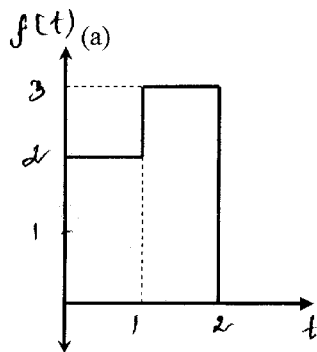
(1) Find the Laplace Transform of following waveform.



(b) Draw the waveform from wave equation

$$f(t) = 6a(t - t_1) + 2a(t - t_2) - 10a(t - t_3)$$

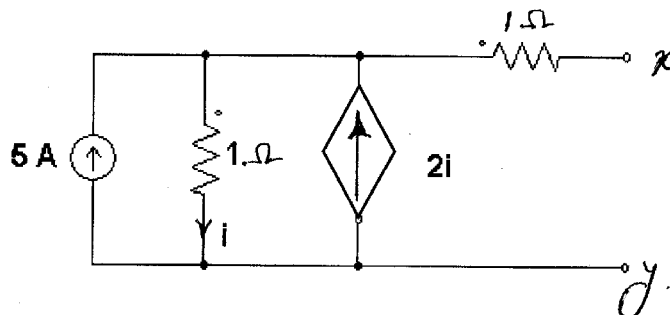
(2) In the circuit shown in figure below, find the Norton's equivalent at x-y terminals.



(3) A series RLC circuit has for its driving point admittance zero at origin and pair of conjugate poles at  $-1 \pm j25$ . Write admittance function. Also, find the values of R, L and C.

(4) If  $f_1(t) = 2u(t)$  and  $f_2(t) = e^{-3t}u(t)$ , determine convolution between  $f_1(t)$  and  $f_2(t)$ .

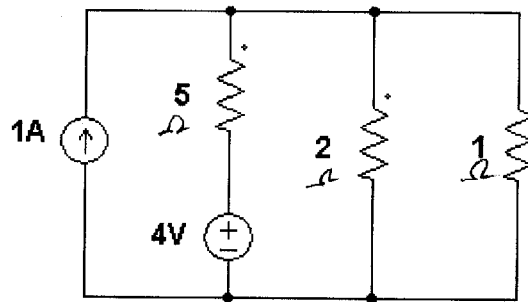- (5) Using Thevenin's Theorem, Find current in 1 ohm Resistor.



---