



RN-6225

B. E. II (Sem. III) (I & C) Examination

May / June – 2010

Measurement & Instruments

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दृष्टावित्त निशानीवाणी विगतो उत्तरवडी पर अवश्य दभवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
B. E. 2 (Sem. 3) (I & C)

Name of the Subject :  
Measurement & Instruments

Subject Code No. : 6 2 2 5 Section No. (1, 2,.....) : 1&2

Seat No. :

Student's Signature

- (2) Answers to each sections must be written in separate answer books.  
(3) Figures to the right indicate full maximum marks.  
(4) Draw neat figure wherever required.

SECTION - I

Q1		
(a)	Define the following: i. Hysteresis ii. Threshold iii. Fidelity iv. Repeatability v. Range	[10]
(b)	What is error? State and explain each of its types.	[8]
Q2		
(a)	Explain the construction of PMMC meter with the help of a neat sketch. How are different forces produced? Derive the torque equation.	[8]
(b)	Describe the lag adjustment devices used in single phase induction type meters.	[8]
OR		
(a)	Draw the necessary circuit diagram for the measurement of three phase power by two wattmeter method. Make necessary derivations. In case of balanced load, discuss the effect of following load power factors on the two wattmeter readings: zero, 0.5 and unity.	[8]
(b)	Describe the working of a frequency meter, which depends on mechanical resonance for its action.	[8]

		[16]
Q3	Attempt any TWO:	
(a)	A Wheatstone bridge has ratio arms of $1000\Omega$ and $100\Omega$ and is being used to measure an unknown resistance of $25\Omega$ . Two galvanometers are available. Galvanometer A has a resistance of $50\Omega$ and sensitivity of $200\text{ mm}/\mu\text{A}$ and galvanometer B has values of $600\Omega$ and $500\text{ mm}/\mu\text{A}$ . Which of the two galvanometers is more sensitive to a small unbalance on the above bridge, and what is the ratio of sensitivities? The galvanometer is connected from the junction of the ratio arms to the opposite corners.	
(b)	The inductance of a moving iron ammeter is given by the expression: $L = (12 + 5\theta - 2\theta^2)\mu\text{H}$ Where $\theta$ is the angular deflection in radians from zero position. Determine i) the spring constant iii) the angular deflection in radians for a current of $10\text{A}$ if the deflection for a current of $5\text{A}$ is $30^\circ$ .	
(c)	Describe briefly how Wien bridge can be used for the measurement of frequency.	

## SECTION - II

Q4		
(a)	i. What are the limitations of a Wheatstone bridge? ii. What are the applications of a CRO? iii. What is the difference between: <ul style="list-style-type: none"> <li>• Range and span.</li> <li>• Accuracy and Precision.</li> <li>• CGS and MKS system?</li> </ul>	[2] [6] [2]
(b)	Explain how a simple AC bridge circuit operates and derive an expression for the unknown parameters.	[8]
Q5		
(a)	With the help of block diagram, explain the working of sampling oscilloscope.	[8]
(b)	Explain the multi range voltmeters.	[8]
	OR	
(a)	Draw a neat diagram of digital storage oscilloscope and explain its working.	[8]
(b)	Explain briefly any two of the following methods of frequency measurement: i) Lissajous figures                      ii) spot wheel method iii) Gear wheel method	[8]
		[16]
Q6	Attempt any TWO:	
(a)	A Maxwell's inductance comparison bridge arm AB consists of a coil with inductance $L_1$ and resistance $R_1$ in series with a non inductive resistance $R$ . Arm BC and arm AD are non inductive resistances of $100\Omega$ . Arm AD consists of standard variable inductor $L$ of resistance $32.7\Omega$ . Balance is obtained when $L_2 = 47.8\text{ mH}$ and $R = 1.36\Omega$ . find the resistance and inductance of the coil in arm AB.	
(b)	A $50\text{V}$ range spring controlled electrodynamic voltmeter has an initial inductance of $0.25\text{ H}$ , the full scale deflection torque of $0.4 \times 10^{-4}\text{ Nm}$ and full scale deflection current of $50\text{mA}$ . Determine the difference DC and $50\text{Hz}$ AC readings at i) $50\text{V}$ and    ii) $25\text{ V}$ if the voltmeter inductance increases uniformly over the full scale of $90^\circ$ .	
(c)	Explain the different circuits of a CRO.	