



RN-6785

B. E. III (Sem. V) (ECC) Examination

May / June - 2010

Pulse & Switching Circuits

Time : 3 Hours]

[Total Marks : 100

Instruction :

(1)

नीचे दृष्टावेक निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
B. E. 3 (Sem. 5) (ECC)

Name of the Subject :  
Pulse & Switching Circuits

Subject Code No. : 6 7 8 5 Section No. (1, 2,.....) : 1&2

Seat No. :

Student's Signature

- (2) Attempt **all** the questions.
- (3) Assume data if **necessary**.
- (4) Figures to the **right** indicate full marks.
- (5) Answers to the two sections must be written in separate answer books.

### SECTION - I

- 1 (a) Attempt the following : 10
- (i) The wave form which preserves its form when transmitted through a linear network is a:
    - (a) Sine wave
    - (b) Step signal
    - (c) Impulse signal
    - (d) Ramp Signal.
  - (ii) The lower cut off frequency of a low pass RC circuit is \_\_\_\_\_.
  - (iii) the rise time of the output of a low pass RC circuit is given by \_\_\_\_\_.
  - (iv) If two stages with rise times  $tr_1$  and  $tr_2$  respectively, are connected in cascade the resultant rise time  $tr$  is given by:
    - (a)  $tr = tr_1 + tr_2$
    - (b)  $tr = tr_1 \times tr_2$
    - (c)  $tr = 1.05$
    - (d)  $tr = 2 \sqrt{tr_1^2 + tr_2^2}$
  - (v) The condition for perfect compensation of an alternator is \_\_\_\_\_.

- (vi) RL circuits are used when a large time constant is required (T/F)
  - (vii) In a clamping circuit the average level of the input does not play any part in determining the steady state o/p wave form (T/F)
  - (viii) Clipping circuits require nonlinear elements (T/F)
  - (ix) In a clamping circuit, the tilts in the forward ( $D_f$ ) and reverse ( $D_r$ ) are related by
  - (x) In a clamping circuit, when there is distortion the relation  $A_f/A_r = R_f/R_r$  is not valid. (T/F)
- (b) Derive an equation of percentage tilt for high pass RC network. 5
- (c) Explain the concept of an attenuator with its applications. 5

2 Attempt any two : 16

- (i) The periodic ramp voltage shown in figure (1) is applied to a low pass RC circuit.
  - (a) Find the equations from which to determine the steady state output wave form.
  - (b) If  $T_1 = T_2 = RC$ , find the maximum and minimum values of the output voltage and plot the waveform.

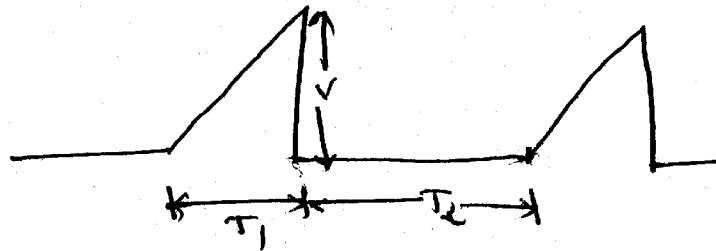


Fig. 1

- (ii) For the clipping circuit shown in figure 2 make a plot of  $V_o$  versus  $V_{in}$  for the range of  $V_{in}$  from 0 to 50 V. Indicate all slopes and voltage levels. Also, indicate for each region, the diodes which conduct

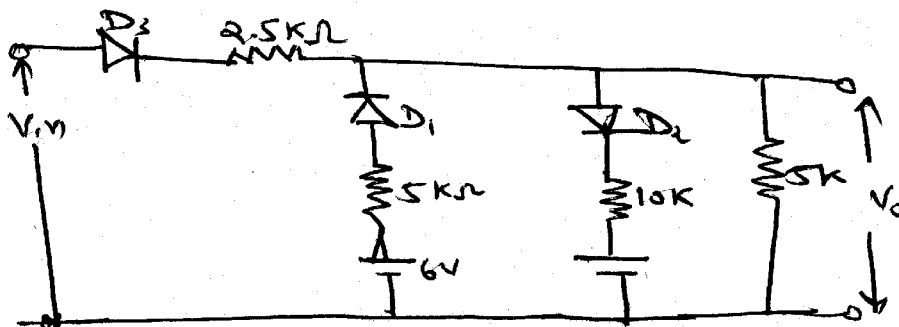



Fig. 2

- (c) Explain the operation of transistor as a clipper and derive the necessary equation for the same.

3 Attempt any two :

14

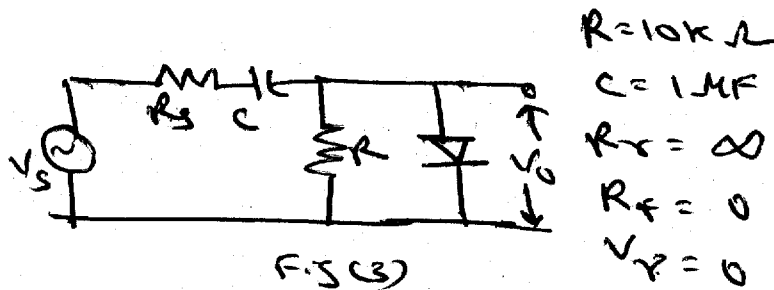- (i) Explain the concept of differentiation and double differentiation.
- (ii) A symmetrical 10 kHz square wave whose peak-to-peak excursions are  $\pm 10V$  with respect to ground is applied to the clamping circuit of figure (3) for the same
- (a) Sketch the output wave form
- (b) If the diode forward resistance is  $1 K\Omega$  sketch the output waveform
- (c) Repeat part (b) if the source impedance is  $1 K\Omega$



- (3) An unsymmetrical square wave with  $T_1 = 1 ms$  and  $T_2 = 1 \mu s$  has an amplitude of 20 V. This signal is applied to the clamping circuit of fig 3 in which  $R_F = 100 \Omega$ ,  $R = 100 K\Omega$  and  $R_s = 0$ . Assume that capacitor is arbitrarily large so that the output is a square wave without tilt. For the same
- (a) Find where the zero level location on the waveform is located
- (b) If the waveform is inverted so that  $T_1 = 1 \mu s$  and  $T_2 = 1 ms$  find location of the zero level.

## SECTION - II

4 (a) Answer the following :

10

- (i) During a transition, the loop gain is \_\_\_\_\_.
- (ii) The loop gain will be \_\_\_\_\_ if either of the two devices is below cut off or if either device is in saturation.
- (iii) \_\_\_\_\_ multivibrator is used as a delay circuit and as a gating circuit.
- (iv) Synchronization may be on a \_\_\_\_\_ basis or maybe with \_\_\_\_\_.

- (v) The \_\_\_\_\_ multivibrator is used as a master oscillator.
- (vi) For a Schmitt trigger \_\_\_\_\_ is defined as the i/p voltage at which Q1 starts conducting.
- (vii) \_\_\_\_\_ reduces o/p swing
- (viii) The interval during which conduction transfer from one transistor to another is called the \_\_\_\_\_.
- (ix) A circuit which has got one permanent stable state and one quasi stable state is called a \_\_\_\_\_.
- (x) \_\_\_\_\_ multivibrator can be used as a voltage to frequency converter.
- (b) Explain non-saturating binary. 5
- (c) Explain triggering symmetrically through unilateral diode. 5
- 5** (a) Explain the emitter coupled binary with the use of waveform for different loop gain and also explain hysteresis. 8
- (b) Calculate the component values of a monostable multivibrator developing an output pulse of 500  $\mu$ s duration. Assume  $h_{FE}(\text{min}) = 25$ ,  $I_{CE}(\text{sat}) = 5\text{mA}$ ,  $V_{CC} = 10\text{V}$  and  $V_{BB} = -4\text{V}$ . 7
- OR**
- 5** (a) Derive the expression for UTP and LTP for emitter coupled binary. 8
- (b) Silicon NPN transistors with  $h_{FE}(\text{min}) = 50$  are available. Design an astable multivibrator to generate a square wave of 2 KHz frequency with a duty cycle of 25%. 7
- 6** Write short notes on following (any **three**) 15
- (i) Schmitt trigger as a squaring circuit
- (ii) Fixed bias bistable multivibrator
- (iii) Types of triggering in a binary
- (iv) Miller sweep generator circuit
- (v) Commutating capacitors.
-