



RN-7385

**B. E. - IV (Sem. - VII) (ECC) Examination**  
**May / June - 2010**  
**Electronics System Design**

Time : 3 Hours]

[Total Marks : 100

**Instructions :**

(1)

नीचे दशांश देव निशानीवाणी विगतो उत्तरवडी पर अवश्य दधवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
B. E. - 4 (SEM. - 7) (ECC)

Name of the Subject :  
ELECTRONICS SYSTEM DESIGN

Subject Code No. : 7 3 8 5 Section No. (1, 2.....) : 1&2

Seat No. :

Student's Signature

- (2) Attempt all questions.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data whenever necessary and specify your assumptions clearly.
- (5) Use of scientific non-programmable calculator CASIO FX 82, 83, 100 or equivalent of other makes is allowed.

**SECTION - I**

- 1 Do as directed, Attempt questions of total 14 marks.
- 1.1 Value of capacitor as a filter will be more if ripple factor needed is more. True or false? 2  
Justify.
  - 1.2 Explain unit associated with  $K_I$  (integral mode controller constant) and it's significance? 2
  - 1.3 A controller outputs 4 to 20mA signal to control motor from 300 to 500 rpm with linear dependence. Find current corresponding to 400 rpm. 2
  - 1.4 Justify: Curve of output voltage versus output current is not perfect parallel to current axis, for voltage supply. 2
  - 1.5 Define following in context of process and control characteristics. 6
    - 1) Self regulation
    - 2) Process Load
    - 3) offset error
  - 1.6 What are limitations of series pass voltage regulators? 2
  - 1.7 Integral mode controller is natural extensions of Floating type controllers; True or false? 2  
Justify.
- 2 A Describe technique of designing function (arbitrary waveform) using Microcontroller. Draw connection/block diagram and flow chart of program for generating triangular waveform. 6
- 2 B Give steps of designing buck type switching regulator. Determine the filter circuit parameters for buck type SMPS for the following specifications; Input voltage  $V_{in}$  varies form 30V to 40V , Output volts  $V_o = 10V$ ; Output current  $I_o = 10A$ , Output voltage ripple = 80mV, Switching frequency = 50KHz. 8
- 2 C List and explain criteria for switching frequency selection in case of switch mode power supply. 4


OR

RN-7385]

1

[Contd...

- 2 A Describe design steps for Linear voltage regulators. 4
- 2 B With the help of waveforms and diagram explain operation of boost type switching regulators; derive design equations, and subsequently give design steps for filter circuit. 8
- 2 C What is significance of PWM waveforms in regulators? Explain techniques to generate PWM waveforms. 6
- 3 A Explain basic principle of proportional mode controller. Describe steps for design. 4
- 3 B Design two level controller for following specifications 6  
 For upper value of voltage:  
 Switch off relay at 40 V and switch on 25V  
 For Lower value of voltage:  
 Switch off relay at 15 V and switch on 20V  
 Assume suitable scale factor for sensing voltage. Explain each design steps and derive expressions you use.
- 3 C Derive controller output for following error profile, if controller is of PI type and having parameters  $K_I=0.2 \text{ s}^{-1}$ ,  $K_p=1$  and  $P_o=21\%$ . Draw graph of controller output based on values of controller output. 8  
 Design and draw circuit for above controller.

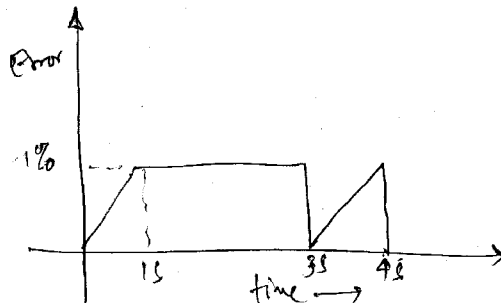

## SECTION - II

4. (a) Answer the followings: 12
- (i) The minimum number of machine cycle required to execute an 8051 instruction is \_\_\_\_\_ and maximum number of machine cycles required are \_\_\_\_\_.
- (ii) The ACALL target address is limited to \_\_\_\_\_ bytes from the present PC and LCALL target address is limited to \_\_\_\_\_ bytes from the present PC.
- (iii) The instruction ADD A,#255H is \_\_\_\_\_ and instruction DIV A,R1 is \_\_\_\_\_. (Legal/ Illegal).
- (iv) ADC 0809 is \_\_\_ bit ADC with \_\_\_ analog input channels.
- (v) \_\_\_\_\_ Interrupt has highest priority and \_\_\_\_\_ interrupt has lowest priority in 8051 upon reset.
- (vi) \_\_\_\_\_ and \_\_\_\_\_ registers are used to control and program the timer operations.
- (b) State criteria for selecting a micro-controller for any task. 04
- (c) Explain stack addressing modes in 8051 w.r.t. PUSH and POP instructions. 04
5. (a) Write a program to see whether D0 and D1 bits of register R1 are high. If so then divide register R1 by 4. 05
- (b) Write a program to get the 'x' value in the range 0 to 15 from P1 and send  $x^2$  to P2 continuously. Use look up table stored in ROM at location named SQR\_TABLE. 06
- (c) Explain following 8051 instructions with suitable example. 04  
 (i) SWAP A (ii) MUL AB

OR

5. (a) Find the time delay produced by following 8051 delay routine if clock frequency is 16MHz. **05**

```
DELAY: MOV R5,#100
BACK:  MOV R2, #200
AGAIN: MOV R3, #250
HERE:  NOP
      NOP
      DJNZ R3, HERE
      DJNZ R2, AGAIN
      DJNZ R5, BACK
      RET
```

(b) Explain in brief the difference in reading of input port pins Vs. port latch in 8051. **06**

(c) With the help of block diagram show how to connect PC serial port with 8051. Also indicate standard baud rates supported by IBM PC. **04**

6. Attempt any three. **15**

(a) Write a program to generate a 2kHz square wave using timer 0. Take 11.0592MHz crystal frequency and neglect instruction overhead. Output square wave on pin P1.5.

(b) Write a program to receive data serially on 8051 and put them in P1. Set the baud rate at 4800, 8bit data and 1 stop bit.

(c) Explain role of IP and IE register in 8051 interrupt programming?

(d) Give the interfacing of DAC 0808 with microcontroller 8051. Also write a program to generate a saw-tooth waveform using this scheme.

(e) Explain interfacing of LCD display unit with 8051 considering data and control signals of LCD.

---