



RN-8065

B. E. II (Sem. III) (EC/CO/IT/IC) Examination

May / June - 2010

Digital Logic Design

Time : 3 Hours]

[Total Marks : 100

Instruction :

(1)

नीचे दशांशविल निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. 2 (Sem. 3) (EC/CO/IT/IC)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Digital Logic Design"/>	<input type="text"/>
Subject Code No. : <input type="text" value="8"/> <input type="text" value="0"/> <input type="text" value="6"/> <input type="text" value="5"/>	Section No. (1, 2,...): <input type="text" value="1&2"/>
Student's Signature	

- (2) Attempt **all** questions.
(3) Assume suitable data whenever **necessary**.
(4) Figures to the **right** indicate full marks.

SECTION - I

- 1 (a) Answer following questions : 10
- (i) Convert $(0.6234)_{10}$ into its equivalent octal number.
- (ii) Subtract $(9)_{10}$ from $(4)_{10}$ using 1's complement method.
- (iii) Find the excess-3 code and its 9's complement for $(592)_{10}$.
- (iv) Prove $A + \bar{A}B = A+B$
- (v) Define an integrated circuit. Also give classification of digital ICs.
- (b) (i) Obtain an 8:1 MUX using two 4:1 MUX. 5
- (ii) Simplify the following equation using K-map 5
- $f(A, B, C, D, E) = \sum m(0, 2, 5, 7, 13, 15, 18, 20, 21, 23, 28, 29, 31)$
- 2 (a) Simplify the following using tabulation method. 8
- $Y(w, x, y, z) = \sum m(1, 2, 3, 5, 9, 12, 14, 15) + \sum d(4, 8, 11)$
- (b) Explain parity checker with truth table, K-map simplification and logic diagram. 7

OR

- 2 (a) A combinational circuit is defined by the functions : 8
- $F_1 = \sum m(3, 5, 7)$
- $F_2 = \sum m(4, 5, 7)$
- Implement the circuit with a PLA having 3 inputs, 3 product terms and two outputs.

- (b) Realize the following expression using only NOR gates. 4
 $Y = (ABC + \bar{B}\bar{C}) C$
- (c) Draw and explain timing diagrams and pin configuration of IC 7402. 3
- 3 Write short notes on any **three** : 15
 (i) BCD to 7 segment code converter
 (ii) ROM
 (iii) Internal block diagram of a digital computer
 (iv) 4-bit magnitude comparator.

SECTION - II

- 4 (a) Give answer in short : 10
 (i) Give the definition of the propagation delay and setup time.
 (ii) Give characteristics table and excitation table for D flip flop.
 (iii) For edge trigger T flipflop, as given in figure 1, draw output wave form.

 


Fig. 1

- (iv) Explain race condition and solution on it.
 (v) Draw o/p wave for Fig. 2 flipflop used here negative edge trigger D flipflop.

 
 


Fig. 2

- (b) Convert JK to D flip flop and JK to T flip flop. 5
- (c) Explain positive edge trigger D flip flop. 5

- 5 (a) Using JK flip flop design sequential circuit for following state diagram : 8

 


Fig. 4

- (b) Explain serial - in serial - out shift register. Draw the diagram for serial - in parallel - out shift register. 7

OR

- 5 (a) Reduce the state diagram and give state table for reduced state diagram. 8

 


Fig. 5

- (b) Design type I synchronous (synchronous counter using T flip flop) that goes through states 0,3,5,6,0.....is the counter self starting. 7

- 6 Attempt any **three** : 15

- (a) Explain ring counter and Johnson counter.
- (b) Explain in brief ALU with simple example.
- (c) Short note on microprogram control for control organization.
- (d) Short note on Magnetic core memory.
- (e) BCD synchronous counter.