



RN-8079

B. E. - II (Sem. III) (EL/ECC) Examination
May / June - 2010
Circuit & Network

Time : Hours]

[Total Marks :

Instructions :

(1)

नीचे दर्शाविए निशानीवाणी विगतो उत्तरवडी पर अवश्य लखवी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. 2 (Sem. 3) (EL/ECC)

Name of the Subject :
Circuit & Network

Subject Code No. : 8 0 7 9 Section No. (1, 2,.....): 1&2


Seat No. :

Student's Signature

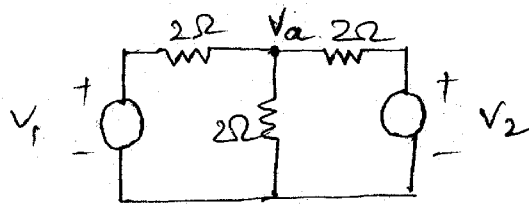- (2) Attempt all questions.
- (3) Answer to the two sections must be written in separate answer books.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data wherever required.
- (6) Scientific calculator upto casio-super fx 100D, 100W, 100MS series and equivalent are permitted.


SECTION - I

- 1 (a) Do as directed :
 - (i) Dual of independent loop is _____ 1
 - (ii) Reciprocity theorem is applicable to network containing both dependent and independent sources (true/false). 1
 - (iii) Define active network and passive network. 2
 - (iv) According to linearity theorem for given circuit $V_a = V_1 + V_2$ 1




(v) Match the following for given graph.

3

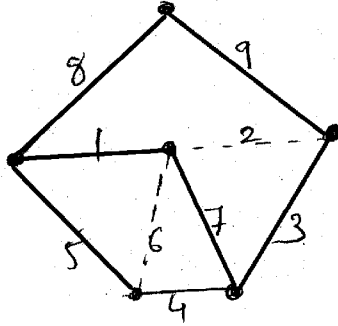


- | | |
|---------------|------------------------|
| (a) 1,7,4,5 | (i) Twigs |
| (b) 2,5,6,9 | (ii) Links |
| (c) 1,3,4,7,8 | (iii) Fundamental loop |
- (vi) Write down the statement of Norton's theorem. 2
- (b) (i) Using Norton's theorem find V_{in} across terminal M-N. 4

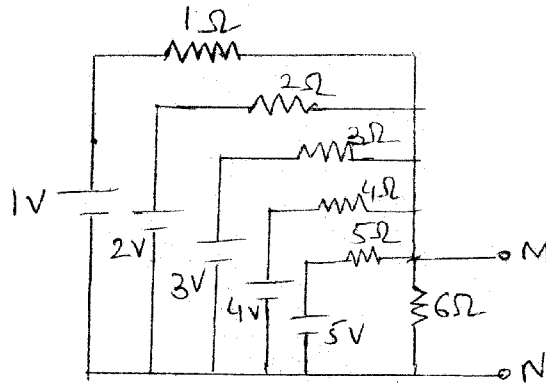


(ii) Derive Z-parameters in terms of Y parameters. 6

2 Attempt any two : 15

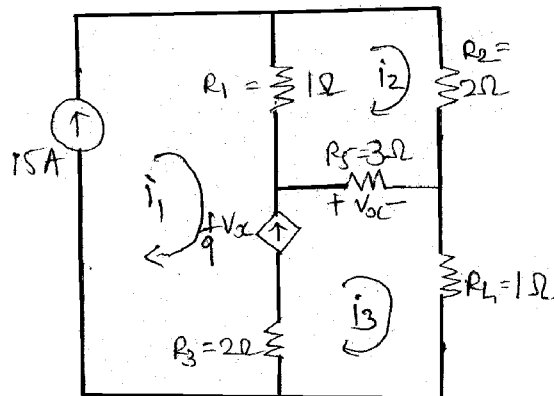
(i) Determine the voltage drop across $R_3 = 2\Omega$ resistor using mesh analysis.



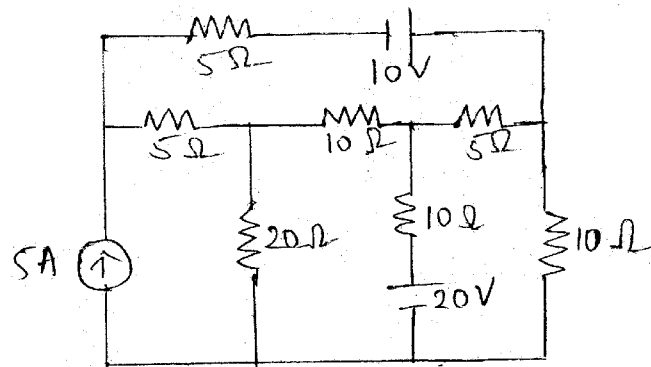
- (ii) Find out current passing through $20\ \Omega$ resistance for given circuit using Norton's theorem.



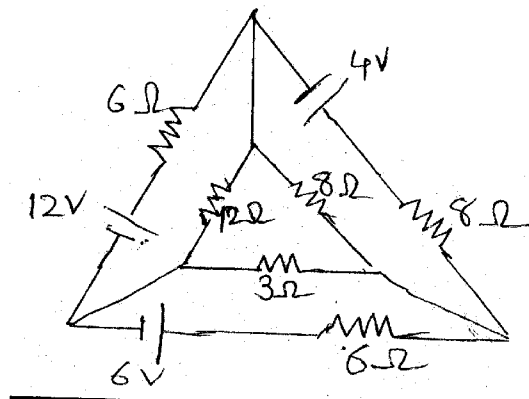- (iii) Determine the current in the $3\ \Omega$ resistor in the given circuit using Thvenin's theorem.




- (iv) Find V_a , V_b , V_c using nodal analysis.

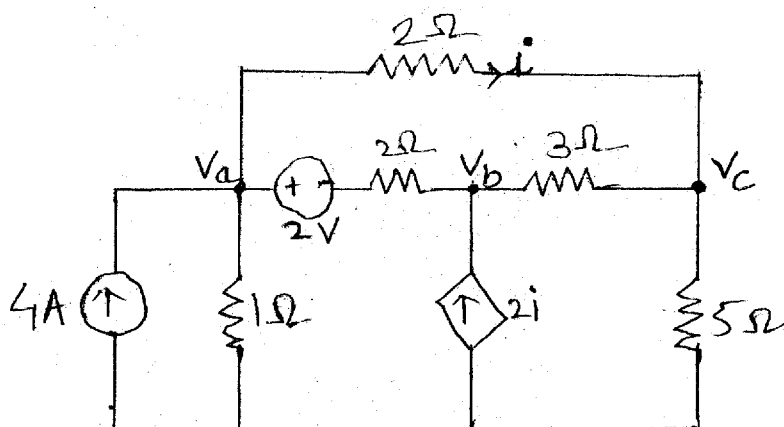


3 Attempt any three :

15

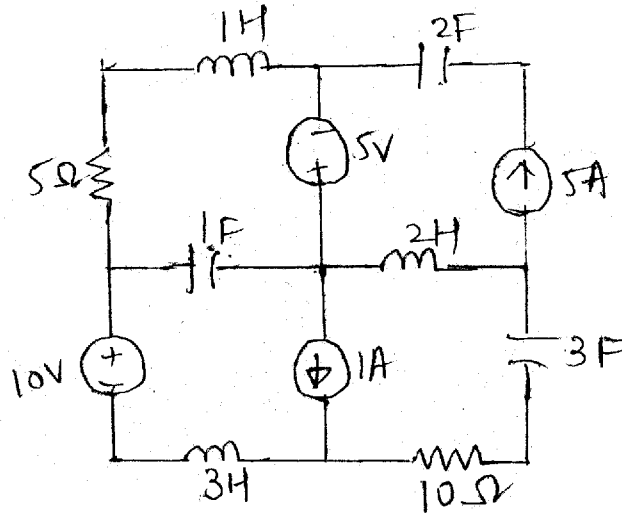
- (i) What do you mean by 'Duality'?
Derive the dual of given circuit.



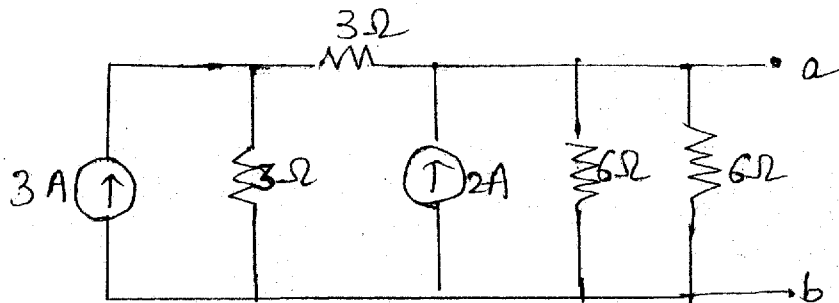
- (ii) (a) Using source conversion, reduce the given circuit into single voltage source in series with single resistance.



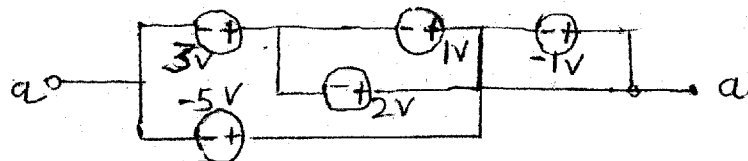
- (b) Replace the network of sources shown in figure with $V_{aa'}$.



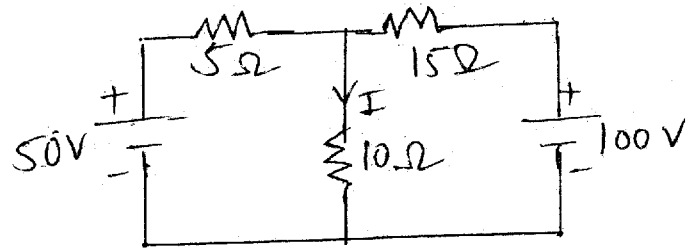
- (iii) Calculate current I using Milliman's theorem for the given network.



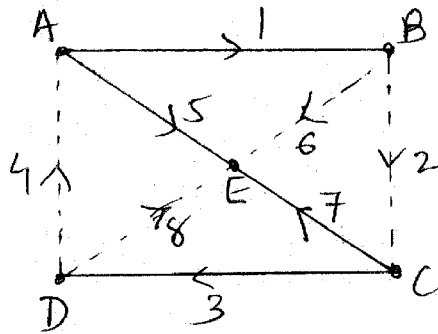- (iv) For the given graph obtain
 (a) Incidence matrix
 (b) Fundamental cutset matrix
 (c) Fundamental tieset matrix.




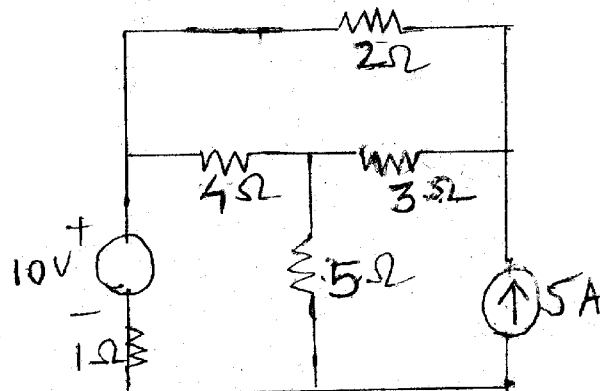- (v) For the given network find out current passing through $2\ \Omega$ resistance using super position theorem.




SECTION - II


- 4 (a) Do as directed 10
- (i) Match the following : 4
- | f(t) | f(s) |
|------------------------------|---------------------------------------|
| (i) t | (a) $1/S + a$ |
| (ii) e^{-at} | (b) $S/S^2 + \omega^2$ |
| (iii) $\cos \omega t$ | (c) $\omega / [(s + a)^2 + \omega^2]$ |
| (iv) $e^{-at} \sin \omega t$ | (d) $1/S^2$ |
- (ii) Define Delay time (td) 2
- (iii) State final value theorem. 2
- (iv) Find the circuit equivalent for following fig at $t = 0^+$ after switch is closed at $t = 0$. 2

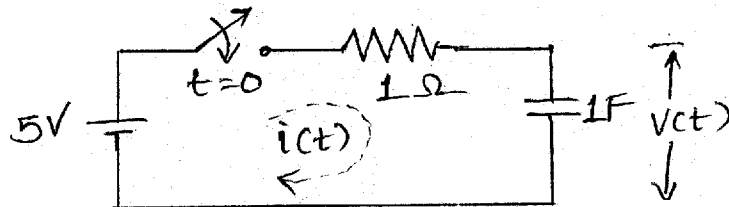

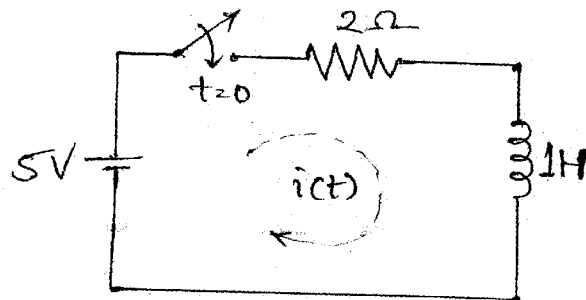- (b) (i) Find out the solution for DC or step response of 1st order R-C circuit. 4
- (ii) Find $i(0^+)$, $\frac{di}{dt}(0^+)$, $\frac{d^2i}{dt^2}(0^+)$ for following fig. 6
- switch is closed at $t=0$.



- 5 (a) Find out the general solution to second order differential equation if the roots are real and equal. Which type of response does the system has? 7
- (b) Following figure shows a parallel RLC circuit with initial conditions zero. The value of input source current is 1A, at $t=0$ and maintains constant current excitation for all time. Find the inductor current $i_L(t)$ for $t \geq 0$ for $R = 25 \Omega$. 8

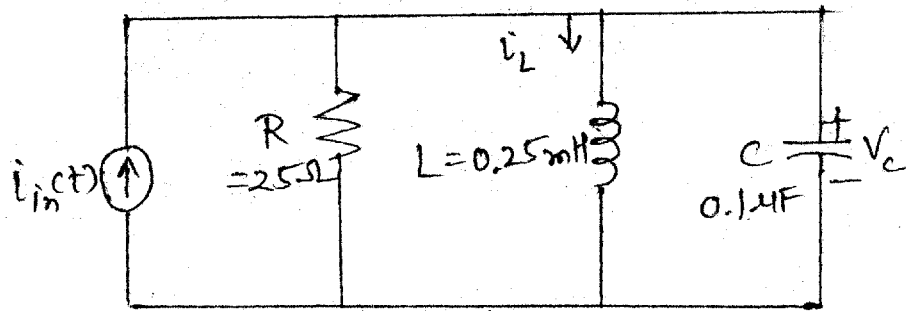


OR

- 5 (a) Draw time response of a system corresponding to following poles and discuss stability at these poles. 6
- (i) $F(s) = 1/s^2$
- (ii) $F(s) = 1/(s^2 + \omega^2)$
- (b) Determine frequency response in terms of resonant, peak and corresponding frequency of system having closed loop transfer function $(Cs) = 1/s^2 + s + 1$, also find out phase angle θ_r . 9


- 6 Attempt any **three** : 15
- (i) Obtain inverse laplace transform of

function $F(s) = \frac{1}{s(s+1)(s^2+1)}$ using convolution theorem.

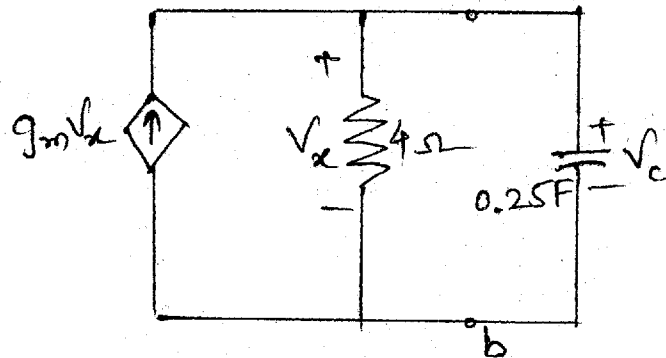- (ii) Assuming $g_m = 0.75 \text{ S}$ and $V_c(0) = 10\text{V}$, find $V_c(t)$ for the circuit shown in figure.



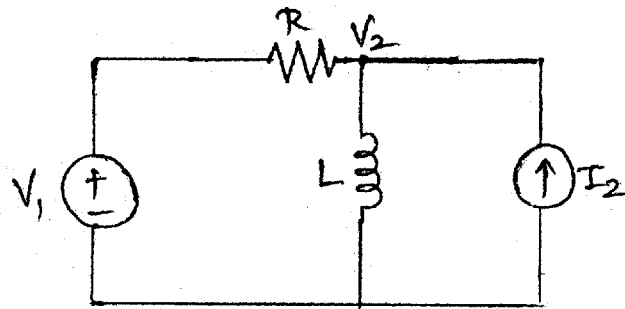- (iii) Derive the general expression for second order source free parallel RLC circuit.
- (iv) Find $V_2(s)$ in the circuit shown in figure use superposition theorem and laplace transform method.



- (v) For the circuit shown in figure find $V_c(+)$. The switch 's' is closed at $t=0$ with zero initial conditions. Use laplace transformation.

