



RN-8203

**B. E. - II (Sem. IV) (Electronics) Examination**  
**May / June - 2010**  
**Advance Electronics**  
**(GTU)**

Time : Hours]

[Total Marks :

**Instructions :**

(1)

नीचे दशावेक निशानीवाणी विगतो उत्तरवडी पर अवश्य वजवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<b>B. E. - 2 (Sem. 4) (Electronics)</b>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<b>Advance Electronics (GTU)</b>	<input type="text"/>
Subject Code No. : <input type="text"/> 8 <input type="text"/> 2 <input type="text"/> 0 <input type="text"/> 3	<input type="text"/>
Section No. (1, 2,.....) : <input type="text"/> 1&2	<input type="text"/>
	Student's Signature

- (2) Figures to the right indicate full marks.
- (3) Assume suitable data if necessary.
- (4) Write each section in different answer book.
- (5) Attempt all questions.

**SECTION - I**

- 1 Answer the following questions : 20
  - (i) Give names of various types of logic families.
  - (ii) What is band-width modulation?
  - (iii) What is the significance of hybrid parameters?
  - (iv) What is the purpose of bypass capacitor in an amplifier?
  - (v) Give applications of oscillators.
  - (vi) What is the use of Bode Plot?
  - (vii) Give names of different types of compensations used in operational amplifiers.
  - (viii) Draw circuit diagram of TTL family.
  - (ix) Write the truth table for EX-NOR gate.
  - (x) What is the value of CMRR in an ideal operational amplifier.
  
- 2 (a) Describe Hybrid -pi CE Transistor Model. 8  
(b) Explain low Frequency Response of an RC coupled stage and effect of an Emitter Bypass Capacitor on Low-frequency Response. 7

**OR**

- 2 (a) Give comparison of current shunt feedback and voltage shunt feedback. 8  
 (b) Explain the method of analysis of a feedback amplifier. 7  
 3 (a) Explain three-pole transfer function with feedback. 8  
 (b) Write short note on Resonant Circuit Oscillators. 7
- OR**
- 3 (a) Write short note on Phase-Shift Oscillator. 7  
 (b) Explain single-stage CE transistor amplifier response. 8

## SECTION - II

- 4 (a) Define the following : 10  
 (i) Slew rate  
 (ii) Sensitivity  
 (iii) Fan in  
 (iv) Noise margin  
 (v) Propagation delay  
 (vi) Power dissipation  
 (vii) i/p offset voltage  
 (viii) Advantages of -ve feedback  
 (ix) Figure of merit  
 (x) O/P offset voltage  
 (b) Explain pole-zero compensation. 2  
 (c) Prove  $Densitivity = 1 + AB$  3

**OR**

- (c) Find the o/p impedance equation for voltage series -ve feedback amplifier. 3  
 (d) True/False : 5  
 (i) Equation of sensitivity is  $1/1+AB$ .  
 (ii) -ve feedback will increase the bandwidth.  
 (iii) DCTL is more useful than RTL.  
 (iv) For voltage series -ve feedback amplifier the feedback signal is voltage.  
 (v) R/Zr ladder type is faster than binary weighted resistor type.


- 5 (a) For the transistor feedback amplifier stage shown, 12  
 $h_{fe}=100$ ,  $h_{ie} = 1k$  while  $h_{re}$  and  $h_{oe}$  are negligible.  
 Determine with  $R_e = 0$ .

(a)  $R_{Mf} = \frac{V_o}{I_s}$  where  $I_s = \frac{V_s}{R_s}$

(b)  $A_{Vf} = \frac{V_o}{V_s}$


(c)  $R_{if}$

(d)  $R'_{of}$

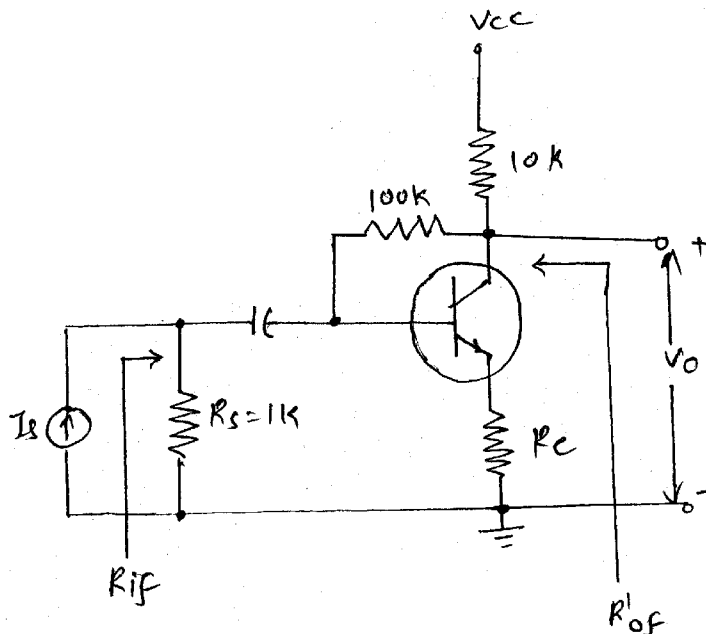

OR

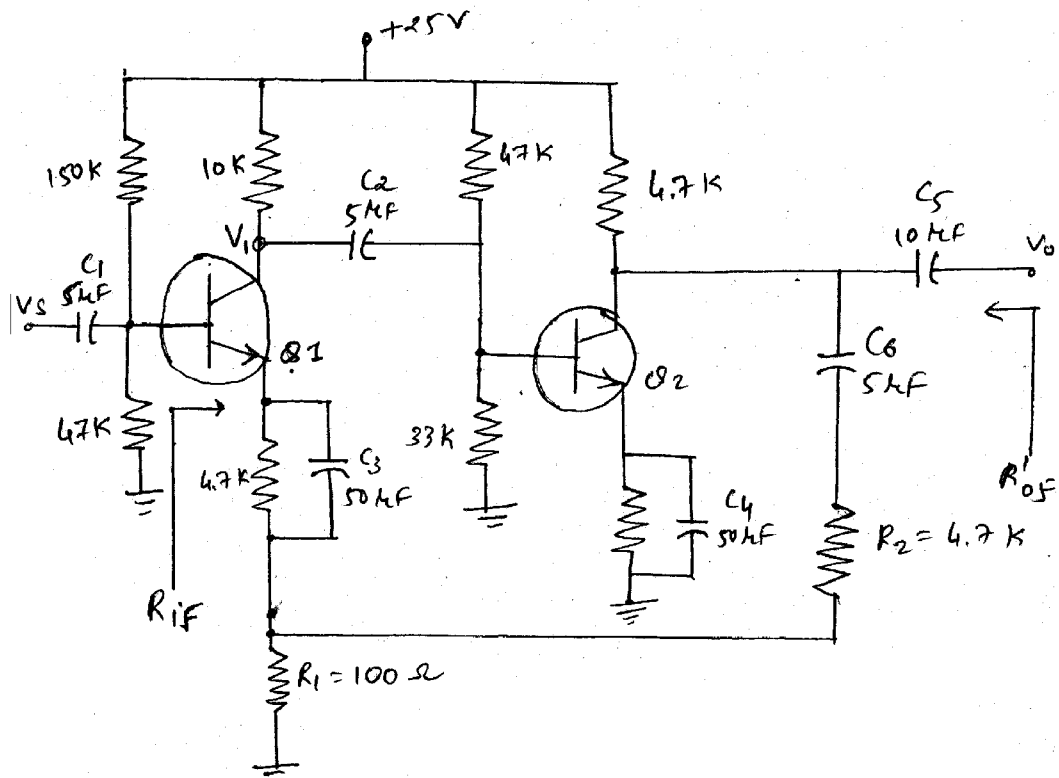Calculate  $A_{vf}$ ,  $R_{of}$  and  $R_{if}$  for the amplifier of below fig.  
 Assume  $R_s = 0$ ,  $H_{fe} = 50$ ,  $h_{ie} = 1.1 k$ ,  $h_{re} = h_{oe} = 0$  and identical transistors.



(b) Derive the i/p impedance equation for voltage series -ve feedback. 3

6 Attempt any **three** : 15

- (i) Explain R/2R ladder type
- (ii) Explain TTL gate in detail
- (iii) Block diagram of -ve feedback amplifier and explain each block in detail.
- (iv) The op-amp is used in the inverting and non-inverting mode with  $R_1 = 1 \text{ k}\Omega$  and  $R_f = 100 \text{ k}\Omega$  if  $V_{ce} = \pm 15 \text{ V}$  and rms input voltage  $V_i = 20 \text{ mv}$ . Calculate the o/p voltage in each case.