



RM-6467

B. E. - II (Sem. IV) (Comp) Examination

May / June - 2010

Linear Electronics - II

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दृशावेव निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. - 2 (Sem. 4) (Comp)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Linear Electronics - 2"/>	<input type="text"/>
Subject Code No. : <input type="text" value="6"/> <input type="text" value="4"/> <input type="text" value="6"/> <input type="text" value="7"/>	<input type="text"/>
Section No. (1, 2,.....) : <input type="text" value="1&2"/>	<input type="text"/>
	Student's Signature

- (2) Attempt **all** the questions.
- (3) Assume suitable data whenever necessary.
- (4) Figures to right indicate full marks.
- (5) Use of scientific calculator casio fx 82, 83, 100 or equivalent of any compulsory.
- (6) Answers to the two section must be written in separate answer books.


SECTION - I

- 1 (a) Attempt all questions: 10
- (i) The threshold voltage of an n-channel MOSFET can be increased by :
 - (a) increasing channel dopant concentration
 - (b) reducing the channel dopant concentration
 - (c) None of above
 - (ii) The main factor, which differentiates a D-MOSFET from E-MOSFET is the absence of :
 - (a) PN junction
 - (b) electrons
 - (c) insulated gate
 - (d) Channel
 - (iii) For a junction FET in the pinch off region, as the drain voltage is increased, the drain current
 - (a) becomes zero
 - (b) abruptly decrease
 - (c) remains constant
 - (iv) _____ amplifier is used for radio frequency transmission.
 - (a) Class A
 - (b) Class B
 - (c) Class C

- (v) Which power amplifier doesn't require output transformer in its working?
- (vi) In low frequency band which capacitors are important?
- (vii) For voltage sampling what is the value of V_o to draw input circuit in any feedback amplifier.
- (viii) The feedback signal is transmitted to input from the output through Block.
 - (a) True
 - (b) False
- (ix) Efficiency of Class C amplifier is 33%.
 - (a) True
 - (b) False
- (x) In a feedback amplifier desensitivity equals :
 - (a) $A\beta$
 - (b) $1/A\beta$
 - (c) $1+A\beta$

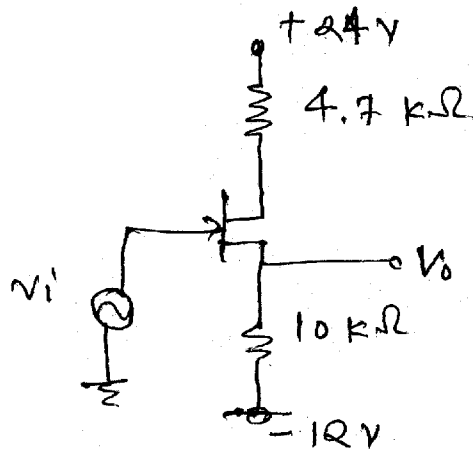- (b) Mention general characteristics of negative feedback amplifier. 2
- (c) What are the limitations of basic amplifier compared to negative feedback amplifier? 2
- (d) "F.E.T. is symmetrical". Justify the statement. State the advantages of FET over BJT. 6

- 2 (a) The JFET shown in figure has $I_{po} = 5.6 \text{ mA}$ 7
 $V_{po} = -4 \text{ V}$.
 (i) Find V_o if $V_i = 0 \text{ V}$
 (ii) Find V_i if $V_o = 0 \text{ V}$




- (b) For transistor coupled class A power amplifier. max power of 5W is to deliver to the load with $R_L = 4 \Omega$. The Q point is adjusted for Max. symmetrical swing and $V_{CC} = 20 \text{ V}$. Find the turns ratio N, peak collector I_{cm} , efficiency η . 8

OR

- 2 (a) Obtain expression for all power calculation of transformer coupled class A amplifier. 8
 (b) Justify, negative feedback increases the stability of amplifier. 7
- 3 Attempt any **three** : 15
 (i) Explain the operation of Metal-oxide semiconductor FET and hence draw its characteristics.
 (ii) Explain effect of an emitter bypass capacitor on low-frequency response of RC-coupled amplifier.
 (iii) Draw the equivalent circuit for a voltage amplifier what are the values of R_i and R_o .
 (iv) Advantages and disadvantages of negative feedback amplifier.
 (v) Explain working of class C amplifier.

SECTION - II

- 4 (a) Attempt following : 10
 (i) The amount of output offset voltage due to input bias current can be significantly reduced by _____.
 (ii) The CMRR is ratio of _____.
 (iii) The input resistance of op-amp 741 C is _____.
 (iv) The ideal op-amp have _____ slew rate.
 (v) To reset the 555 timer we require _____ pulse on pin no. _____.
 (vi) Astable multivibrator often called _____.
 (vii) Peak-detector measure _____ of the square wave input.
 (viii) Linear power supply having _____ power factor.
 (ix) A typical value for input offset current for an op.amp is _____.
 (x) Calculate the output voltage of a non-inverting amp for value of $V_1 = 2$ volt, $R_f = 500\text{ k}\Omega$ and $R_1 = 100\text{ k}\Omega$.
- (b) Explain 555 as an Astable Multivibrator. 6
 (c) Calculate the output voltage and zener current in circuit given below for $R_L = 1\text{ k}\Omega$. 4

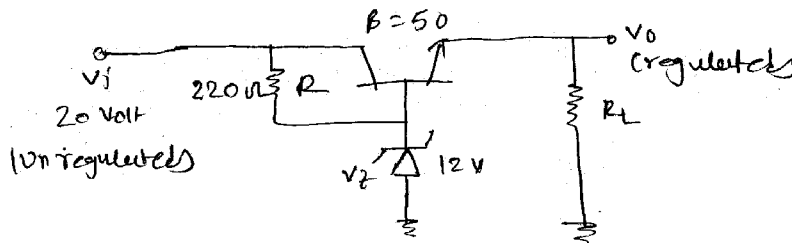


- 5 (a) Design off-set voltage compensating network. 8
 (b) Design the phase-shift oscillator such that $F_o = 200\text{ Hz}$. 4

- (c) In the circuit of differentiator given below 3

$R_1 = R_2 = 1\text{ k}\Omega$, $R_F = R_3 = 10\text{ k}\Omega$ and op-amp is 741 C.

(i) What are the gain and input resistance of the amplifier.

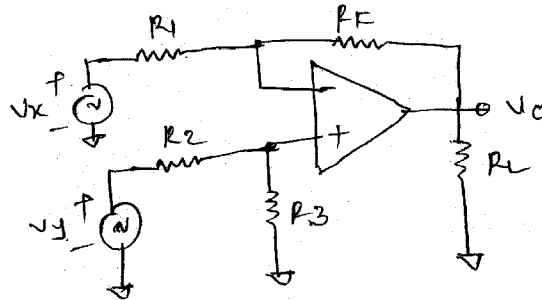(ii) Calculate the output voltage V_o if $V_x = 2.7\text{ V}_{pp}$ and $V_y = 3\text{ V}_{pp}$ sine wave at 100 Hz.




$$R_1 = R_2$$


$$R_F = R_3$$

OR

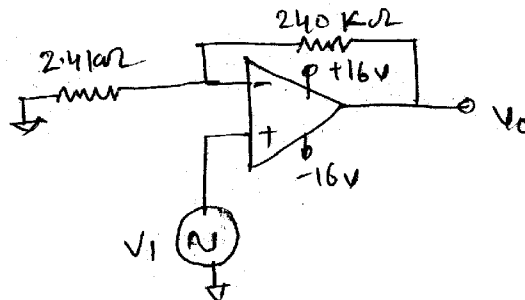- 5 (a) Write short note on differentiator; also draw the frequency response and effect of differentiator on different waves like sine, square. 8
- (b) Calculate the output voltage from the circuit of fig. below for an input of $120\text{ }\mu\text{ volt}$. 3



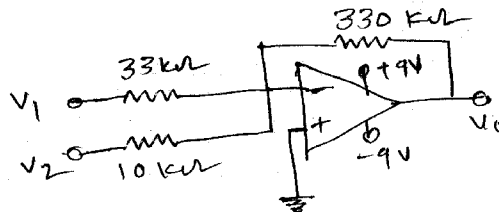- (c) Calculate the output voltage for the circuit of fig. below. The inputs are $V_1 = 50\text{ mV sin}(1000\text{ t})$ and $V_2 = 10\text{ mV sin}(3000\text{ t})$. 4



- 6 Attempt following (any three) 15
- (a) Design op-amp as an integrator
- (b) Write short note on phase-shift oscillator
- (c) Design first-order low-pass butterworth filter.
- (d) Explain series voltage regulation.