



RM-6487

B. E. - II (Sem. IV) (ECC) Examination
May / June - 2010
Electronic Circuits

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दृशावेव निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. - 2 (Sem. 4) (ECC)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Electronic Circuits"/>	<input type="text"/>
Subject Code No. : <input type="text" value="6"/> <input type="text" value="4"/> <input type="text" value="8"/> <input type="text" value="7"/>	<input type="text"/>
Section No. (1, 2,.....) : <input type="text" value="1&2"/>	
Student's Signature	

- (2) Figures on right side indicate full marks.
- (3) Support your answer with neat sketches.
- (4) Assume necessary data, if required.
- (5) Write both sections in separate answer books.


SECTION - I

- 1 (a) Answer the short questions : 10
- (i) Why the channel of a JFET is never completely closed at drain end?
 - (ii) What is pinch off voltage of JFET?
 - (iii) How does FET behave for small value of V_{DS} and for large value of V_{DS} ?
 - (iv) Why input impedance of FET is very high?
 - (v) Why are R-C coupled amplifier widely used as a voltage amplifier?
 - (vi) What is the effect of removal of emitter bypass capacitor in CE amplifier circuit?
 - (vii) What is miller effect?
 - (viii) Define F_T in context of high frequency model of a transistor.
 - (ix) What do you mean by alpha cut off frequency?
 - (x) Why source and drain are reversible in FET?

- (b) As shown in figure 1, two FETs are connected in parallel. Show that the equivalent FET has 6

$$\frac{1}{r_{ds}} = \frac{1}{r_{ds1}} + \frac{1}{r_{ds2}} \quad \text{and} \quad \mu = \frac{\mu_1 r_{ds2} + \mu_2 r_{ds1}}{r_{ds1} + r_{ds2}}$$

Show that effective gm is doubled and rds is halved and μ remain same if both FETs are identical.

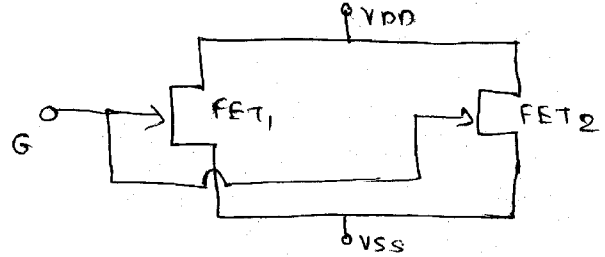


(Figure 1)

- (c) Mention different biasing techniques for FET and explain self bias technique in brief. 4


2 Attempt any two : 16

- (a) Derive the equation for gain in the case of common emitter configuration while considering the effect of emitter bypass capacitor.
- (b) For the source follower circuit shown in figure 2, sketch asymptotic voltage gain for low frequency. Also find lower 3-dB frequency $g_m = 2\text{mS}$, $r_{ds} = 15\text{ k}\Omega$.

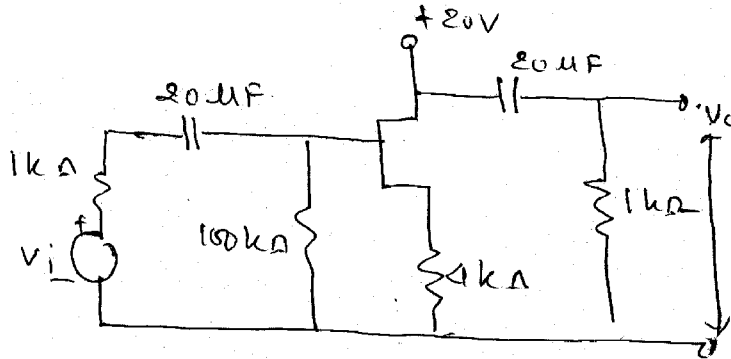

(Figure 2)


- (c) Find and plot transfer function v_o/i_s for amplifier shown in figure 3. Also find C_q such that lower 3dB frequency is at 10 rad/sec.

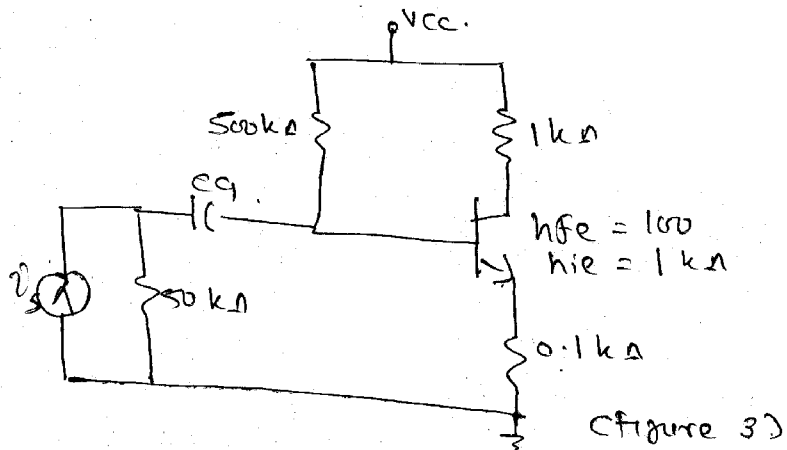

3 Attempt any two :


14

- (a) Explain emitter follower at high frequency. Derive the expression for voltage gain and high frequency.
- (b) The source follower shown in figure 4. The JFET of shown figure 4 has following parameters $g_m = 3\text{mA/V}$, $C_{gd} = 0.2\text{PF}$, $C_{gs} = 20\text{PF}$, $R_i = 10\text{K}\Omega$, $R_s = 2\text{k}\Omega$. Find the upper 3dB frequency and plot asymptotes for voltage gain $|v_o/v_{in}|$.

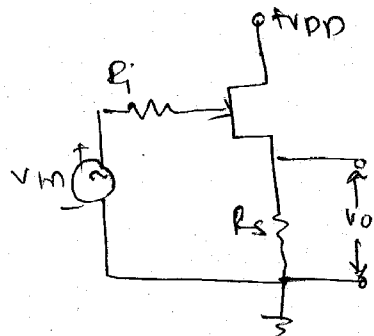

(Figure 4)

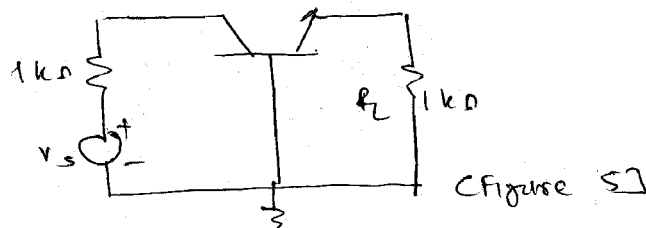- (c) For common base amplifier shown in figure 5, plot asymptotic magnitude plot for (v_o/v_i) and indicate upper 3-dB cut off frequency with $h_{fe} = 50$, $r_{b'e} = 1\text{k}\Omega$, $c_{b'e} = 40\text{PF}$, $c_{b'c} = 1\text{PF}$.



SECTION - II

- 4 (a) Answer following questions :
- (i) Enlist advantages of negative feedback. **3**
 - (ii) Determine the voltage gain, input and output impedance with feedback for voltage series feedback having **3**
 $A = -100$, $R_i = 10 \text{ k}\Omega$, $R_o = 20 \text{ k}\Omega$ for feedback of $\beta = -0.1$
 - (iii) Define : Gain margin and Phase margin. **4**
- (b) (i) Explain RC phase shift oscillator. **5**
- (ii) Find the Gain Bandwidth (GBW) product of a JFET amplifier having the parameters : **5**
 $g_m = 3 \text{ mS}$, $C_{gs} = 6 \text{ PF}$, $C_{gd} = 2 \text{ PF}$,
 $r_{ds} = 70 \text{ k}\Omega$ and $R_d = 10 \text{ k}\Omega$.
- 5 (a) Explain : Synchronously tuned amplifier. **8**
- (b) Draw and explain current shunt feedback circuit with necessary equations. **7**
- OR**
- 5 (a) What is Barkhausen criterion for oscillation? Explain in detail. **7**
- (b) What is the effect of feedback connection on input and output impedance for voltage series and current series connections. Explain with derivations. **8**
- 6 Write short notes on any **three** : **15**
- (i) Colpitt oscillator
 - (ii) Single tuned amplifier
 - (iii) Nyquist criteria
 - (iv) Effect of negative feedback on gain and bandwidth.
-