



RM-6547

**B. E. - II (Sem. IV) (IT) Examination**  
**May / June - 2010**  
**Digital Circuits**

Time : 3 Hours]

[Total Marks : 100

**Instructions :**

(1)

नीचे दृष्टावेव निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. - 2 (Sem. 4) (IT)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Digital Circuits"/>	<input type="text"/>
Subject Code No. : <input type="text" value="6"/> <input type="text" value="5"/> <input type="text" value="4"/> <input type="text" value="7"/>	<input type="text"/>
Section No. (1, 2,.....) : <input type="text" value="1&amp;2"/>	<input type="text"/>
	Student's Signature

- (2) Attempt all questions.
- (3) Answers to the **two** sections must be written in **separate** answer books.
- (4) Figures to the extreme right indicate marks.
- (5) Assume necessary data.
- (6) Draw logic circuit for design problem.

**SECTION - I**

- 1 (a) Answer the following : 10
- (i) What are SOP and POS forms of Boolean Expression?
  - (ii) What is the difference between weighted and non-weighted code? Explain with illustrations.
  - (iii) Write the difference between truth table and excitation table.
  - (iv) What are the advantages of digital systems over analog systems?
  - (v) Write first 10 decimal digits in base 5.

(b) Do as directed : (any **five**) 10

(i) Convert  $(5C7)_{16}$  and  $(756.603)_8$  to decimal.

(ii) Convert decimal 250.5 to base 3, base 4, base 7, base 8 and base 16.

(iii) Show that

$$A\bar{B}C + B + B\bar{D} + AB\bar{D} + \bar{A}C = B + C$$

(iv) Multiply  $(10110)_2$  with  $(10.1)_2$

(v) Reduce using mapping the expression

$\sum m(0, 1, 2, 3, 5, 7, 8, 9, 10, 12, 13)$  and implement it in universal logic.

(vi) Simplify following functions and implement them with NAND logic :

$$F = (B'+D') (A'+C'+D)(A+B'+C'+D)(A' + B+C'+D')$$

2 (a) What is K-map? Explain the use of it with example. 8

(b) What is a PLA? Explain it with example. 7

**OR**

(b) What is magnitude comparator? Draw logic diagram of a 4-bit comparator. 7

3 Do as directed : (any **three**) 15

(i) Implement the following function with a MUX :

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$

(ii) Explain Half/Full adder circuits. Also show their NAND gate implementation.

(iii) A circuit receives a 4-bit 5211 BCD code. Design the minimum SOP circuit to detect the decimal numbers 0, 2, 4, 6 and 8.

(iv) A logic equation is given as

$$F = AB'C + B'CD' + ABC + A'B'CD$$

(a) Prepare a truth table

(b) Simplify using K-map

(c) Realize using NAND gates.

## SECTION - II

- 4 (a) Answer the following : 10
- (i) What are asynchronous inputs in FFs?
  - (ii) A circuit with  $m$  flip-flops would have \_\_\_\_\_ states.
  - (iii) State True/False :  $A + A = 1$
  - (iv) State True/False : The SET input can use to make  $Q$  as 0.
  - (v) What is State table?
  - (vi) State True/False The circuit for a DEMUX is basically same as that for a decoder.
  - (vii)  $4 \times 1$  multiplexer has \_\_\_\_\_ input, \_\_\_\_\_ output and \_\_\_\_\_ select lines.
  - (viii) State True/False : "Binary Ripple counter is Asynchronous Counter."
  - (ix) State True/False : The SET input can use to make  $Q$  as 0.
  - (x) A group of flip-flop sensitive to pulse duration is called\_\_\_\_\_.
- (b) Answer in short : (any **five**) 10
- (i) Write difference between synchronous and asynchronous counter.
  - (ii) Explain Ripple Counter.
  - (iii) Explain Master-slave flip-flop.
  - (iv) Realize X-OR function using NAND logic.
  - (v) What is a Race condition?
  - (vi) What is Lock-Out?

- 5 (a) What is Flip/Flop? Discuss characteristics of various Flip-Flop. 8
- (b) Design and implement a synchronous 3-bit up/down counter using JK FFs. 7

**OR**

- (b) Write a short note on 4-bit bidirectional shift register. 7
- 6 Do as directed : (any three) 15
- (i) Design 3-bit Parity Generator and 4-bit Parity Checker.
- (ii) Design and implement a mod-6 asynchronous counter using T FFs.
- (iii) Design a D counter that goes through states 0,1,2,4,0.....
- (iv) Write about Johnson Counter.

---