

- 2 (a) Using the ac equivalent circuit, derive the expression 8
for the voltage gain A_d and differential input
resistance of a dual input, unbalanced output
differential amplifier.
- (b) Design a Zener constant current bias circuit according 6
to the following specifications :
- Emitter current $I_{E3} = 6 \text{ mA}$,
IN3825 Zener diode with $V_Z = 4.7 \text{ V}$ and $I_{zt} = 53 \text{ mA}$
CA 3086 transistor with $\beta_{ac} = \beta_{dc} = 100$ and $V_{BF} = 0.715 \text{ V}$
Supply voltage : $-V_{EE} = -9\text{V}$

OR

- 2 (a) Derive the voltage gain and input resistance of a 7
differential amplifier with three op-amps. Write
down its advantages.
- (b) Get the expression for voltage gain and input 7
resistance for a voltage shunt feedback amplifier.
- 3 (a) Obtain the expression for the output voltage of a 4
basic integrator from its diagram.
- (b) Why do we need a practical integrator ? Give its 5
frequency response and applications.
- (c) Design a peaking amplifier circuit to provide a gain 5
of 5 at a peak frequency of 10 kHz.

OR

- 3 (a) Illustrate the circuit operation of a triangular wave 7
generator using op-amp.
- (b) Explain phase correctors and its applications. 7
- 4 (a) What is the need of higher order active filters ? 7
Explain a second order low-pass Butterworth filter
and its design principles.
- (b) Design a second order low-pass filter at a high 7
cutoff frequency of 2 kHz. And draw the frequency
response of it.

OR

- 4 (a) Define A/D and D/A converters. What are the disadvantages of D/A converter with binary weighted resistors ? 4
- (b) Explain another D/A converter, which will overcome this difficulty. 5
- (c) Determine the size of each step if $R_F = 1.2 \text{ k}\Omega$ in a D/A converter (4-bit) with binary - weighted resistors. What is the output voltage when inputs b_0 through b_3 are at 5 V ? $R = 10 \text{ k}\Omega$. 5
- 5 (a) Explain sample and hold circuit and its applications. 6
- (b) Discuss the working principle of absolute-value output circuit with necessary diagram and derivation. 8

OR

- 5 (a) Using the internal block diagram of timer IC explain its action as a monostable multivibrator and give its applications. 8
- (b) Design a monostable multivibrator to be used as a divide-by-2 network. The frequency of the input trigger signal is 2 kHz. 6
