



RA-0715

Second Year B. Sc. Examination

March / April – 2010

Electronics : Paper - III

(Electronics Circuit Design & Application)

Time : Hours]

[Total Marks :

Instructions :

(1)

नीचे दृशायेक निशानीवाणी विगतो उत्तरवही पर अवश्य कपवी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
S. Y. B. Sc.

Name of the Subject :
Electronics : Paper - 3

Subject Code No. : 0 7 1 5 Section No. (1, 2,.....): Nil

Seat No. :

Student's Signature

- (2) Figures on the **right** indicate full marks.
- (3) All symbols and abbreviations have their usual meaning.
- (4) Non-programmable calculator is allowed.
- (5) Draw neat diagram/figures to support your answer.
- (6) Assume data if necessary.

1 Answer in brief :

14

- (a) What do you understand by stabilization of operating point? Why it is necessary in amplifier circuit?
- (b) Why is the voltage gain of an amplifier with negative feedback smaller than no feedback?
- (c) What is the basic condition for oscillation?
- (d) Distinguish between an amplifier and an oscillator.
- (e) Define h-parameters of a transistor in CE configuration.
- (f) Why is it that the total voltage gain of a cascaded amplifier is the product of the stage gains, but the total current gain is not the product of the stage current gains.
- (g) What is cross-over distortion? How is it overcome?

- 2 (a) How we can get operating point stability with the help of bias compensation method? Explain any one compensation method in detail.
- (b) What do you mean by "Thermal resistance"?

10

OR

- 2 (a) Explain why the gain drops at low and high frequency in a frequency response curve of an amplifier. Derive the expression for mid frequency gain in the case of RC coupled amplifier. 8
- (b) Design a voltage divider bias circuit for the following data : 6
 $I_{CQ} = 12 \text{ mA}$, $\beta = 100$, $V_{CCQ} = 9\text{V}$, $V_{CC} = 22\text{V}$
- 3 (a) Using a neat diagram of a transistorised Bistable multivibrator explain its working principle. Derive necessary equations. 8
- (b) Calculate the component values of a monostable multivibrator developing an output pulse of $140 \mu\text{S}$ duration. Assume $h_{femin} = 20$, $I_{sat} = 6 \text{ mA}$, $V_{CC} = 6\text{V}$, $V_{BB} = -1.5\text{V}$. 6
- OR**
- 3 (a) Draw the circuit of a class-B push-pull amplifier and explain its operation. Derive an expression for its maximum conversion efficiency. 9
- (b) An amplifier has mid band gain of 125 and a bandwidth of 250 kHz. If 4% negative feedback is introduced. Find the new bandwidth and gain. 5
- 4 (a) Draw the circuit diagram of phase shift oscillator and explain its operation by deriving expression for frequency of oscillation. 8
- (b) The frequency of oscillation of a three section RC phase shift oscillator with $R=5 \text{ k}\Omega$ is 5 kHz. Find the value of capacitors to be used in it. What range of resistors could be used to obtain a frequency range of 1 kHz to 20 kHz, for this oscillator? Use the same value of capacitor. 6
- OR**
- 4 (a) Discuss the effect of bypass and coupling capacitor on the low frequency response of a CE amplifier. 7
- (b) Explain "Heat Sink Theory." 7
- 5 Write short notes : (any two) 14
- (a) R-C Ramp generator
- (b) Monostable Multivibrator
- (c) FET as a V.V.R.
- (d) Transformer coupled amplifier
- (e) Negative resistance oscillators
- (f) Hartley Oscillator
- (g) Single tuned amplifier.