



RA-0716

Second Year B. Sc. Examination

March / April – 2010

Electronics : Paper - IV

(Digital Electronics & Microprocessor)

Time : Hours]

[Total Marks : 70

Instruction :

नीचे दृशायेक निशानीवाणी विगतो उत्तरवही पर अवश्य कपवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
S. Y. B. Sc.

Name of the Subject :  
Electronics : Paper - 4

Subject Code No. : 0 7 1 6 Section No. (1, 2,.....): Nil

Seat No. :  
[ ] [ ] [ ] [ ] [ ] [ ]

Student's Signature

- 1 Answer in brief : 14
- (i) What is an active low preset input?
- (ii) Add in BCD 415 and 279.
- (iii) Define :
- (a) Noise margin
- (b) Propagation delay
- (iv) What is a flag?
- (v) Give the names of different forms of number system.
- (vi) What do you mean by a controlled inverter?
- (vii) Give the full form of :
- (a) ASCII code
- (b) EBCDIC code.
- 2 (a) Design a 4-bit parallel adder/subtractor circuit. 6
- (b) Write a note on applications of X-OR and X-NOR gate. 8
- OR
- 2 (a) Draw the circuit diagram of two input TTL NAND gate and explain its working. 6
- (b) Draw a logic circuit for implementing the function 8  
 $F = AB + A(B+C) + B(B+C)$  and simplifying the function and draw logic circuit for the simplified function.

- 3 (a) Using K-maps design a full adder circuit. **6**  
 (b) Simplify  
 (i)  $F = (A+B) (\bar{A}+C) (B+C)$   
 (ii)  $F = \overline{AB} + \bar{A} + AB.$
- OR**
- 3 (a) Explain 8 to 1 multiplexer with the help of logic diagram. **6**  
 (b) Explain the working of serial in-parallel out and parallel in-parallel out registers. **8**
- 4 (a) Design and discuss the operation of decade counter. **6**  
 (b) Explain the instructions used for arithmetic and logical operations in the 8085 microprocessor. **8**
- OR**
- 4 (a) Draw the circuit diagram of J.K. flip-flop and explain the working of J-K flip.flop. **6**  
 (b) Draw the circuit diagram of R-S flip-flop and explain its working. Extend your discussion for clocked Rs flip/flop. **8**
- 5 Write short notes on : (any two) **14**  
 (a) Ripple counter  
 (b) Types of semiconductor memories  
 (c) Similarities and differences : CALL-RET and PUSH-POP instructions  
 (d) Error detecting and correcting codes.
-