



RA-0717

Second Year B. Sc. Examination

March / April – 2010

Electronics : Paper - V

Time : 2 Hours]

[Total Marks : 70

Instruction :

नीचे दशांश देव निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
S. Y. B. Sc.

Name of the Subject :  
Electronics : Paper - 5

Subject Code No. : 0 7 1 7 Section No. (1, 2,.....): Nil

Seat No. :

Student's Signature

- 1 Write very short answers :
- Draw the block diagram of a power supply and label each block.
  - What is need for regulation?
  - What component values are measured by an AC bridge?
  - Explain the electrochemical action in battery.
  - Compare relative and absolute error.
  - Discuss advantages and limitations of SMPS.
  - What is a solar cell?

- 2 (a) Discuss the full wave bridge rectifier and explain the action of C filter. Show that the DC output voltage in C filter is dependent on the current drawn from the circuit. 10
- (b) Show how the ripple factor in c filters increases with load current. 4

OR

- 2 (a) Discuss the zener regulator. 6
- (b) Draw a neat block diagram of feedback regulator and explain the process of regulation in this regulator. 8
- 3 (a) Discuss the application of fixed three terminal regulator. 8
- (b) Design a dual regulated power supply using the three terminal fixed regulator giving 12-0-12 volts output voltage. 6

OR

<b>3</b>	(a) What are converters? Discuss the forward type converter and fly-back converter.	<b>10</b>
	(b) Explain how would you make selection of transformer for SMPS.	<b>4</b>
<b>4</b>	(a) What are rechargeable batteries? Discuss the Ni-Cd types of rechargeable batteries?	<b>10</b>
	(b) Discuss the solar cells as a source of power.	<b>4</b>
<b>OR</b>		
<b>4</b>	(a) Discuss the Kelvin Bridge for measurement of resistance.	<b>8</b>
	(b) Discuss any <b>two</b> transducers you know.	<b>6</b>
<b>5</b>	Write short notes : (any <b>two</b> )	<b>14</b>
	(i) Types of errors	
	(ii) UPS	
	(iii) Adjustable regulator	
	(iv) Block diagram of a power supply	
	(v) Battery charger.	

---