



RR-0610
First Year B. Sc. Examination
March / April – 2010
Electronics : Paper - I
(Computer Science) (Basic Electronics)

Time : 3 Hours]

[Total Marks : 70

Instructions :

(1)

<p>નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination : F. Y. B. Sc.</p> <p>Name of the Subject : Electronics - 1</p> <p>Subject Code No. : 0 6 1 0 Section No. (1, 2,.....): Nil</p>	<p>Seat No. : □ □ □ □ □ □</p> <div style="border: 1px solid black; border-radius: 15px; height: 60px; display: flex; align-items: center; justify-content: center; margin-top: 10px;">Student's Signature</div>
--	---

- (2) All questions are **compulsory**.
- (3) Assume data if necessary.
- (4) Symbols and abbreviations have their usual meaning.
- (5) Figures to the right indicate full marks.

1 Answer in brief :

7×2=14

- (a) Write full form of
 - (i) JFET
 - (ii) MOSFET
 - (iii) LED
 - (iv) LDR
- (b) Enlist the types of memory
- (c) Define tolerance of resistor
- (d) What is the basic difference between P-type and N-type semiconductor ?
- (e) Enlist the types of number system.
- (f) What do you mean by break down in diode?
- (g) Draw the symbol of NAND and XOR gate.

- 2 (a) What is resistor? Explain various types of resistor in detail. 8
- (b) Give the colour codes of following resistor : 6
- (i) 3.9 k Ω (ii) 4.7 k Ω
- (iii) 1 M Ω .

OR

- 2 (a) Distinguish between metal, semiconductor and insulator. 8
- (b) Convert the following binary numbers to decimal : 6
- (i) 1011 (ii) 1101101
- (iii) 1110111

- 3 (a) Explain construction, working and characteristics of diode. 8
- (b) Write the truth table of 6
- (i) AND gate (ii) OR gate
- (iii) NOR gate.

OR

- 3 (a) Explain construction and working of transistor in detail. 8
- (b) Design the logic circuit representing boolean expression : 6
- (i) $X = A + \bar{B} \cdot C$ (ii) $X = (A + B) (\bar{A} + C) (B + D)$.

- 4 (a) Why NAND and NOR gate are called universal gates? Explain NAND and NOR gate in detail. 8
- (b) Prove the following boolean identity : 6
- $A + (B \cdot C) = (A + B) \cdot (A + C)$.

OR

- 4 (a) Explain half adder and full adder in detail. 8
- (b) State and prove De-Morgan's first and second theorem. 6
- 5 Write short notes : (any two) 7 \times 2=14
- (i) R-S Flip-Flop (ii) Binary Counter
- (iii) ROM (iv) Types of capacitor.