



RR-0613

First Year B. Sc. Examination

March / April – 2010

Electronics : Paper - II

(Network Analysis of Synthesis)

Time : 3 Hours]

[Total Marks : 70

Instructions :

(1)

नीचे दर्शावेल निशानीवाणी विगतो उत्तरवडी पर अवश्य लभवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
F. Y. B. Sc.

Name of the Subject :  
Electronics - 2

Subject Code No. : 0 6 1 3 Section No. (1, 2,.....): Nil

Seat No. :

Student's Signature

- (2) Figures on the right indicate marks.  
(3) All symbols and abbreviations have their usual meaning.  
(4) Use of non-programmable calculator is allowed.  
(5) Assume data if necessary.

1 Answer in brief :

14

- (i) What are linear and bilateral impedances?  
(ii) Find the Laplace transform of unit step function.  
(iii) What is the average of the sinusoidal function for one complete cycle?  
(iv) Define : "Resonance."  
(v) State the Norton's theorem.  
(vi) What do you mean by quality factor Q?  
(vii) What is an electronic filter?

2 (a) State and explain the Thevenin's theorem.

8

(b) Find the inverse Laplace transform for the following

6

$$\text{function : } F(s) = \frac{s+5}{s^2+6s+8}$$

OR

RR-0613]

1

[Contd...

- 2 (a) Discuss fully step current response of an R-L-C circuit. What is the time constant of R-L-C circuit? Draw the graphical representation of above response. **10**
- (b) In a series R-L-C circuit damping ratio is 20 and natural frequency of oscillation is 100 Hz. Find the time constant of the circuit. **4**
- 3 (a) Define Fourier Series. Deduce the constant coefficients as  $a_0$ ,  $a_1$ ,  $b_1$ ,  $a_n$  and  $b_n$ . **8**
- (b) State and explain Ohm's law, Kirchoff's voltage law and Kirchoff's current law. **6**
- OR**
- 3 (a) Evaluate instantaneous power. **8**
- $$P(t) = \frac{V_m I_m}{2} \cos \theta - \frac{V_m I_m}{2} \cos (2\omega t - \theta)$$
- (b) A voltage  $v(t) = 170 \sin (377 + 10^\circ)$  is applied to a circuit. It causes a steady state current to flow, which is described by  $i(t) = 14.4 \sin (377 - 20^\circ)$ . Determine the power factor and average power delivered to the circuit. **6**
- 4 (a) Define series resonance and prove that for an R-L-C series circuit the  $Q$  factor is : **10**
- $$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$
- (b) A series resonance circuit uses an inductor of  $10 \mu\text{H}$  and if the resonance frequency is 1 kHz then find the value of the capacitor used in the circuit. **2**
- (c) Distinguish between series and parallel resonance. **2**
- OR**
- 4 (a) Explain the constant-K low pass filter and find the expression for cut-off frequency. **10**
- (b) Name the various type of filter you have studied. **2**
- (c) Discuss the applications of filter circuits. **2**
- 5 Write short notes : (any two) **14**
- (a) Maximum power transfer theorem
- (b) Tellegen's theorem
- (c)  $N^{\text{th}}$  order Laplace transform
- (d) Balanced three phase system
- (e) One Port and two port network.