



**RR-0857**

**Third Year B. Sc. Examination**

**March / April – 2010**

**Electronics (ID)**

*(Can Course)*

*(New Course)*

Time : 3 Hours]

[Total Marks :

**Instructions :**

(1)

नीचे दशावलि निशानीवाणी विगतो उत्तरवडी पर अवश्य लभवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="T. Y. B. Sc."/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Electronics (ID) (Can) [NEW]"/>	<input type="text"/>
Subject Code No. : <input type="text" value="0"/> <input type="text" value="8"/> <input type="text" value="5"/> <input type="text" value="7"/>	<input type="text"/>
Section No. (1, 2,.....) : <input type="text" value="Nil"/>	
	Student's Signature

- (2) Draw neat diagram wherever necessary.
- (3) Symbols used in the question paper have their usual meaning.
- (4) Figures to the right indicate full marks of the question.
- (5) Scientific calculator may be used.

1 Answer the following questions in short : 14

- (i) Calculate the efficiency of transformer coupled class A amplifier for a supply of 12V and output voltage  $V_P(L) = 12V$ .
- (ii) Define CMRR and slew rate.
- (iii) State three application of a thermistor.
- (iv) Draw the circuit diagram of colpits oscillator.
- (v) What are the different characteristic of op-amp.
- (vi) Voltage shunt feedback having  $z_i = 20k\Omega$ , and  $z_{if} = 5k\Omega$ .  
Calculate output impedance with feedback if output impedance with feedback if output impedance is  $30k\Omega$ .
- (vii) What is maximum closed loop gain for an op-amp having slew rate  $2.4V/\mu s$  when input signal varies by  $0.3V$  in  $10\mu s$ .

- 2 (a) Explain class B amplifier operation. Obtain an equation for its efficiency and show that maximum efficiency is 78.5%. 7
- (b) Calculate the efficiency of a class B amplifier for a supply voltage of  $V_{cc} = 24V$ , with peak to peak output load voltage of (i) 44 volts and (ii) 12 volts. 4

**OR**

- 2 (a) Explain the method used to categorize amplifier on the basis of class. 7
- Draw the diagram of series fed class A amplifier and explain its DC and AC operation.
- (b) Calculate the efficiency of a transformer coupled class A amplifier for a supply 12V and outputs of 4
- (i)  $V_{L(PP)} = 24V$  and
- (ii)  $V_{LP} = 6V$
- 3 (a) Explain how the stability of a feedback amplifier can be investigated using Nyquist method. 7
- State advantage and disadvantage of negative feedback.
- (b) Determine the feedback gain, gain with feedback and output resistance for the voltage series feedback if 4
- $R_i = 1k\Omega$ ,  $A = -50$ ,  $R_{if} = 6k\Omega$  and  $R_{of} = 6.67k\Omega$ .


**OR**

- 3 (a) Explain the Wein-bridge oscillator with circuit diagram. Also explain FET phase shift oscillator with circuit diagram. 7
- (b) Calculate the frequency for FET colpits oscillator circuit having the component values  $L_{Rfc} = 0.5mH$ , 4
- $L = 100\mu H$ ,  $C_1 = 0.005\mu F$ ,  $C_2 = 0.01\mu F$  and  $C_c = 10\mu F$ .

- 4 (a) What is op-amp ? What is open loop gain in op-amp. 7  
 Explain the use of op-amp as
- (i) Inverting amplifier and
  - (ii) Summing amplifier.
- (b) Calculate the CMRR in dB for the circuit 4  
 measurements of  $v_d = 1mV$ ;  $v_o = 120mV$  and  
 $V_c = 1mV$ ;  $V_o = 20\mu V$ .

OR

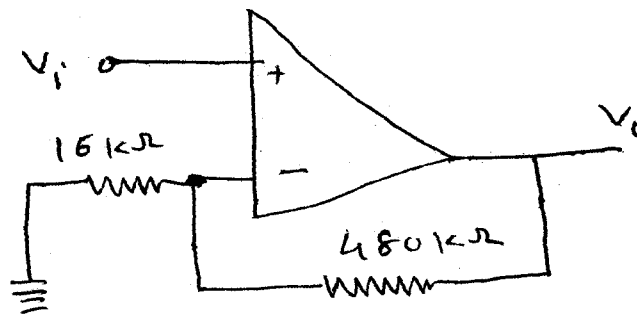- 4 (a) Draw the basic block diagram of op-amp and explain 7  
 the function of each block.
- (b) What input ( $V_i$ ) must be applied to input of given 4  
 circuit to result an output of  $-9.3V$  ? State the polarity  
 of applied voltage.



- 5 (a) Explain amplitude modulation in detail. What is 7  
 modulation factor ? Explain following case of modulation.
- (i) 00 %
  - (ii) 50 %
  - (iii) 100 %
  - (iv) 150 %

- (b) A carrier of 150V and 200 kHz is modulated by 70V, 4 200Hz sinewave signal. Calculate frequency components of modulated wave along their amplitude.

**OR**

- 5** (a) What are the functions of radio receiver ? Give detail **6** notes on straight radio receiver and supper-heterodyne receiver with proper diagram.
- (b) Describe the construction of UJT with its symbol. **5**  
Draw and explain UJT emitter characteristic.
- 6** Answer any **two** of the following : **14**
- (a) Describe the construction and basic operation of SCR giving necessary diagram the operation of SCR on the basis of two transistor analog.
- (b) Explain the use of diac in proximity detector.
- (c) Write a short note on varactor diode.
- (d) Describe how the construction and application of hot carrier diode are significantly different from those of conventional semiconductor diode.