



SE-6181

B. E. - II (Sem - III) (Common With EL & ECC)

Examination

April / May - 2011

Electrical Network - I

Time : Hours]

[Total Marks : 100

Instructions :

(1)


नीचे दृशावेव निशानीवाणी विगतो उत्तरवही पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. - 2 (SEM - 3) (COMMON WITH EL & ECC)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="ELECTRICAL NETWORK - 1"/>	<input type="text"/>
Subject Code No. : <input type="text" value="6"/> <input type="text" value="1"/> <input type="text" value="8"/> <input type="text" value="1"/>	<input type="text" value="Student's Signature"/>
Section No. (1, 2,.....): <input type="text" value="Nil"/>	

- (2) Attempt **all** questions.
- (3) Figures to **right** indicate full marks.
- (4) Assume suitable data wherever necessary.
- (5) Scientific calculator upto *fx100D,100W,100MS* series and equivalent are permitted


1 (a) Answer the following questions :

- (i) The maximum value of coefficient of coupling is _____. 1
- (ii) In an electrical circuit, the dual of capacitor is _____. 1
- (iii) The current in the neutral wire of a balanced three-phase, four wire star connected load is _____. 1
- (iv) While calculating the Thevenin's equivalent impedance of an electrical network, 1
 - (a) the terminal of interest are short circuited
 - (b) the terminal of interest are open circuited
 - (c) voltage source is replaced by its short circuit equivalent.
 - (d) the terminal of interest are open circuited and voltage source is replaced by its short circuit equivalent.

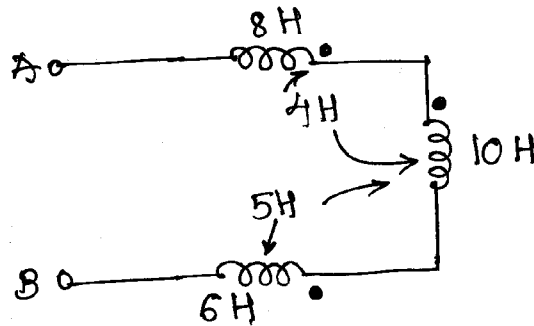- (v) The principle of superposition does not hold good 1
while calculating.
- the current through a resistor
 - the voltage across an impedance
 - the current and voltage across a resistor
 - the instantaneous power
- (vi) The equivalent inductance across terminals A 2
and B for the given coupled circuit is _____.




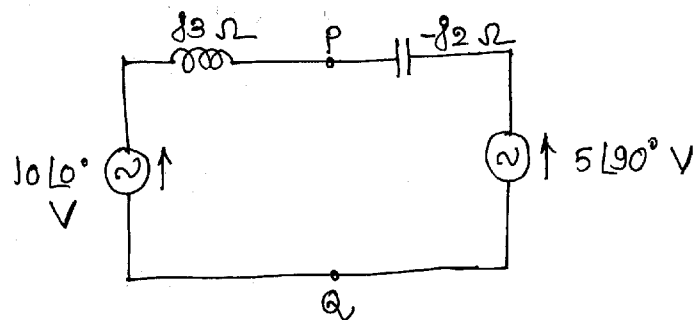- (vii) For the network shown in Fig. below, the 3
Thevenin's equivalent voltage between terminals P
and Q is _____.




- Explain the concept of duality with a suitable 5
example.
- State the explain dot rule. 5

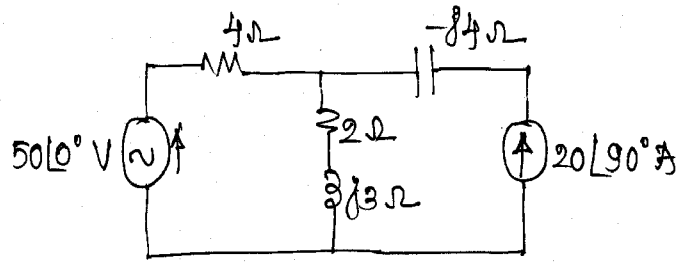- 2 (a) For the circuit shown in Fig. below, determine the current in $(2+j3)$ ohm, using superposition theorem. 7




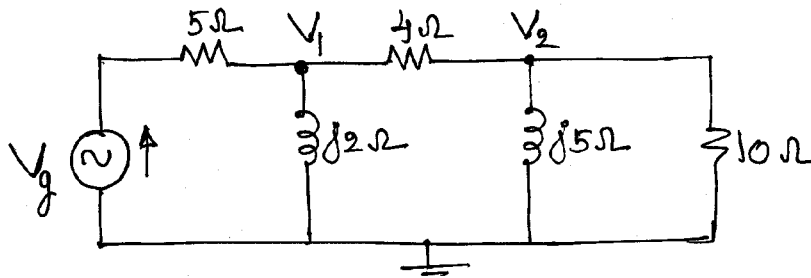- (b) Find the ratio of node voltages V_1/V_2 for the network given below. 8




OR

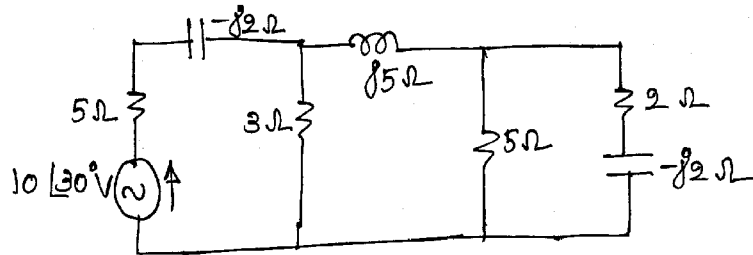- 2 (a) Determine the current through impedance $(2-j2)\Omega$ using Thevenin's theorem. 7




- (b) Obtain Norton's equivalent circuit at open terminals A-B. 8

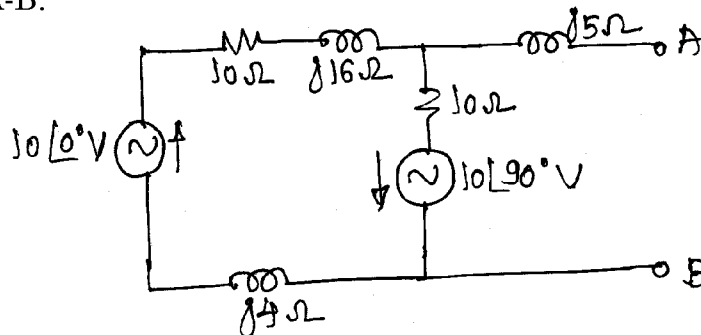


3 Attempt any three :

15

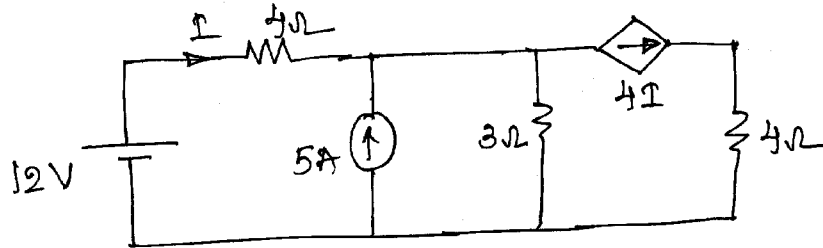
- (i) Find current I through $4\ \Omega$ resistor using Thevenin's theorem in the given figure.



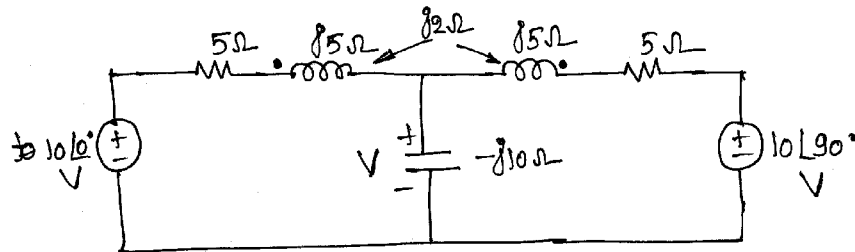- (ii) For the given dotted equivalent circuit, determine voltage V across $10\ \Omega$ capacitive reactance.



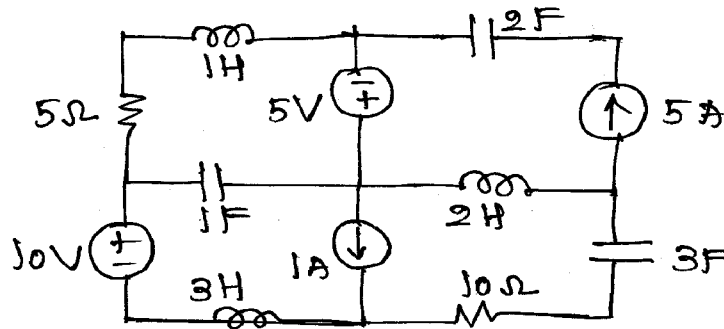- (iii) Obtain the dual of the following network.



- (iv) A three phase, 3-wire, 100 V, ABC system supplies a delta connected three equal impedances of $5\angle 45^\circ\ \Omega$. Determine the line currents I_A , I_B , I_C . Also draw phasor diagram.
- (v) Explain displaced neutral method for 3-phase, 3-wire unbalanced star connected load. Derive expression for displaced neutral voltage.

4 (a) (i) Match the following :


04

- | | |
|-------------------------|--|
| (a) $\sin wt$ | (i) $\frac{1}{s+a}$ |
| (b) $\sinh wt$ | (ii) $\frac{s \cos \theta - w \sin \theta}{s^2 + w^2}$ |
| (c) $\cos(wt + \theta)$ | (iii) $\frac{w}{s^2 - w^2}$ |
| (d) e^{-at} | (iv) $\frac{w}{s^2 + w^2}$ |

(ii) Fill in the blanks :

6

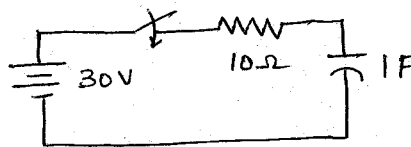
- (i) Given $f(s) = \frac{s+2}{s(s+1)}$ the initial value of the function will be _____.
- (ii) Time constant for a series R-C circuit is _____.
- (iii) for the circuit shown current through the circuit at $t = \infty$ is _____



- (iv) Laplace transform of impulse function is _____.
- (v) When $f(t) = -f(-t)$ then function is said to have _____ symmetry.
- (vi) The z-parameter equation of a 'T'-network is
 $V_1 = 24I_1 + 8I_2$
 $V_2 = 8I_1 + 32I_2$
 z_{22} for the network is _____.

(b) Obtain y parameter for the network shown.

05

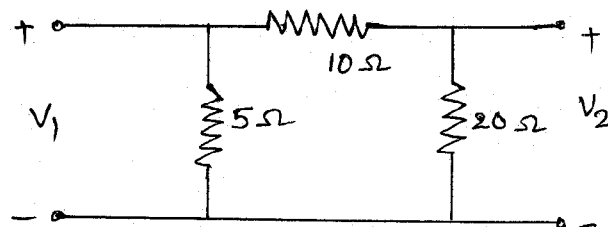



(c) State and prove final value theorem.

03

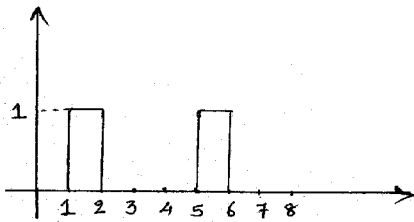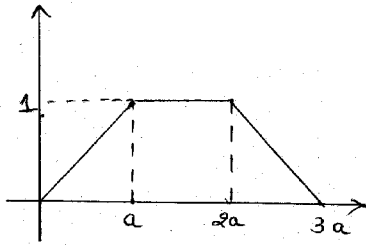
(d) If $f_1(t) = f_2(t) = e^{at}$ determine convolution between $f_1(t)$ and $f_2(t)$.

02

- 5 (a) Obtain Laplace transform of the following waveforms. 5



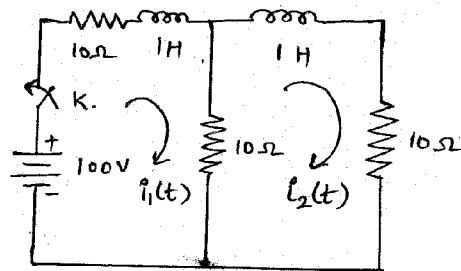- (b) Find current $i_2(t)$ using Laplace transformation for the circuit shown. Assume initial condition to be zero. 10




OR


- 5 (a) Find inverse Laplace for the following function. 05

$$F(s) = \frac{3s^2 + 4}{s(s^2 + 4)}$$

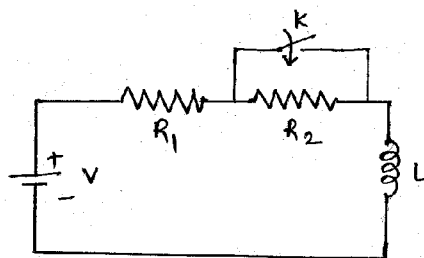- (b) In the figure the battery voltage is applied for a steady state condition. Obtain complete expression for current after closing the switch 'K'. Assume $R_1 = 1\Omega$, $R_2 = 2\Omega$, $L = 1H$ and $V = 10v$. 10



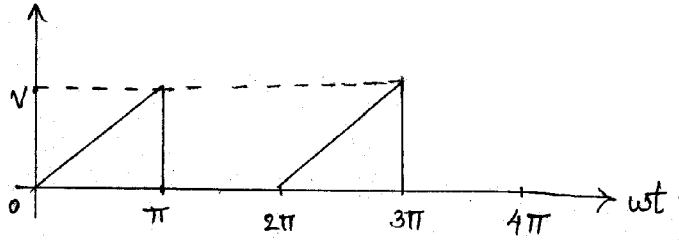- 6 (a) Evaluate fourier coefficient a_n for the fourier series. 5
 (b) Find trigonometric fourier series for the waveform shown. 10



OR

- 6 (a) Find Laplace transform for the following functions. 05
 (i) $f(t) = \cos \omega t$
 (ii) $f(t) = e^{at}$
 (b) Find trigonometric fourier series for the waveform shown and plot line spectrum. 10

