



SE-6227

**B. E. - II (IC) (Sem. III) Examination**  
**April / May - 2011**  
**Digital Circuits**

Time : 3 Hours]

[Total Marks : 100

**Instructions :**

नीचे दशावेक निशानीवाणी विगतो उत्तरवही पर अवश्य दखवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :

Name of the Subject :

Subject Code No. :     Section No. (1, 2,.....) :

Seat No. :

Student's Signature

- 1 Attempt all questions
- 2 Assume suitable data wherever required
- 3 Figure to the right indicate full marks.

- 1 (A) Answer the following questions 10
- (1) 1's complement of 10101010 is \_\_\_\_\_
  - (2) Draw the symbol and truth table of NOR gate
  - (3) Simplification of  $x + xy$  is \_\_\_\_\_
  - (4) \_\_\_\_\_ is the gray code of 1011.
  - (5) \_\_\_\_\_ is the binary equivalent of decimal number 111.
  - (6) What is the full form of ASCII ?
  - (7) What is the dual of  $A + AB$  ?
  - (8) Implement  $Y = AB + CD + E$  with the help of logic gates.
  - (9) 4 X 1 multiplexer has \_\_\_\_\_ selection lines.
  - (10) \_\_\_\_\_ and \_\_\_\_\_ are called universal gates.
- 1 (B) Explain Full adder circuit diagram and truth table. 6
- (C) Realize Ex- OR gate with NAND gates only. 4
- 2 (A) Design binary to gray code converter circuit. 8
- (B) Simplify following boolean functions using K-map 7
- (1)  $F(a,b,c,d) = \sum m (1,5,7,9,11,13,15)$
  - (2)  $F(w,x,y,z) = \sum m (1,3,4,5,7,9,11,13,15)$
- OR
- 2 (A) Simplify the following Boolean function using tabulation method 8
- $F(A,B,C,D) = \sum m (0,1,3,7,8,9,11,15)$
- (B) Design a combinational logic circuit whose out put is high only when majority of inputs (A,B,C,D) are low. 7
- 3 Attempt any three. 15
- (1) Explain 3 to 8 line decoder with truth table and circuit diagram
  - (2) Implement following boolean function using 8 : 1 multiplexer  
 $F(A,B,C,D) = \sum m (2,4,5,7,10,14)$
  - (3) Design 2 bit multiplier circuit.
  - (4) Explain BCD adder circuit.
  - (5) Design 3 bit parity generator and checker circuit.

**Q4.**

**A) Attempt All.**

1. Explain difference between 'Combination Circuit' and 'Sequential Circuit'. [3]
2. What do you mean by Race around condition? [2]
3. For J-K Flip-flop output is toggle when  $J = \underline{\quad}$ ,  $K = \underline{\quad}$ . [2]
4. Differentiate Synchronous and asynchronous circuits. [3]

**B) Explain 4-bit Ring Counter with necessary Wave forms. [10]**

**Q5. Attempt Any two. [16]**

- A) Explain Universal Shift register in detail.
- B) Draw SR Latch circuit with Truth table, Excitation table and Char. Equation.
- C) Convert SR flipflop to JK Flipflop.

**Q6. Attempt Any Two. [14]**

- A) Explain JK flipflop with Asynchronous inputs.
- B) Explain ROM in Detail.
- C) Design BCD Counter with JK flip flop. Draw necessary waveform.

---