

- (b) Find the complement of the functions 4
 $F_1 = x'yz' + x'y'z$ and $F_2 = x(y'z' + yz)$.
- (c) Express the Boolean function $F = A+B'C$ in sum of 6
 minterms. Also draw logic diagram.
- 2** (a) Simplify the following Boolean function. 8
 (1) $F = A'B'C' + B'CD' + A'BCD' + AB'C'$
 (2) $F = (A,B,C,D,E) = \sum (0,2,4,6,9,11,13,15,17,21,25,27,29,31)$
- (b) Explain BCD to excess-3 code conversion with 7
 necessary diagram.

OR

- 2** (a) Simplify following Boolean function using tabulation 8
 method
 $F(w,x,y,z) = \sum (1,4,6,7,8,9,10,11,15)$
- (b) Explain carry generator and checker. 7
- 3** (a) Explain BCD adder. 8
- (b) Implement a full-adder circuit with a decoder and 7
 two or gates.

OR

- 3** (a) Implement function $F(A,B,C,D) = \sum (0,1,3,4,8,9,15)$ 8
 using multiplexer.
- (b) Write short note on types of ROM 3. 7

SECTION - II

- Instructions :** (1) Figures to the right indicate full marks.
(2) Programmable calculators are not allowed.
(3) Justify your answer with proper explanation.
(4) Draw logic circuit for design problem.

- 4 (a) Attempt all : 10
(1) Draw characteristic table and excitation table for JK flipflop.
(2) List applications of counter.
(3) Explain terms : Edge trigger flipflop
(4) Draw basic block diagram of master slave flipflop.
(5) Explain term : Asynchronous Input
(b) List types of shift register and explain any one of them. 10
- 5 (a) Design a type T-counter that goes through 8
states 0-3-5-6-0...
(b) Explain 4 bit Johnson counter in detail. 8

OR

- (b) Explain 4 bit binary counter with parallel load. 8
- 6 Attempt any **two** : 14
(a) Explain clocked 'D' flipflop with NAND gates.
(b) Convert D flipflop to J K flipflop.
(c) A combination circuit is defined as the function :

$$F_1(A, B, C) = \Sigma (3, 5, 6, 7)$$

$$F_2(A, B, C) = \Sigma (0, 2, 4, 7)$$

Implement the circuit with a PLA having 3 inputs, 4 product terms and 2 outputs.