



SE-6827

B. E. III (Sem. V) (IC) Examination

April / May – 2011

Linear Integrated Circuits

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दृष्टावेक निशानीवाणी विगतो उत्तरवही पर अवश्य लभवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. III (Sem. V) (IC)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Linear Integrated Circuits"/>	<input type="text"/>
Subject Code No. : <input type="text" value="6"/> <input type="text" value="8"/> <input type="text" value="2"/> <input type="text" value="7"/>	<input type="text"/>
Section No. (1, 2,.....) : <input type="text" value="1&2"/>	
Student's Signature	

- (2) Attempt all questions.
(3) Figure to the **right** indicates marks.
(4) Answers to the **two** sections must be written in same answer book.

SECTION-I

- 1 (a) Answer the following question briefly. 10
- (i) Draw the pin diagram of IC 741 op-amp. 2
- (ii) Give any two non-linear applications of op-map. 2
- (iii) Define the terms 'offset voltage' and 'input impedance' with respect to op-amp. 2
- (iv) State barkheusen criteria ? 2
- (v) Give two disadvantages of R-2R ladder type DAC. 2
- (b) Explain the operation of op-amp as non-inverting amplifier. 8
- 2 (a) Explain the working of astable multivibrator using op-amp. 8
- (b) Explain the working of full wave precision rectifier. 8

OR

- 2 (a) What is frequency compensation in op-amp ? How is it achieved ? 8

(b) How can we use op-amp as a constant current source ? 8

3 Explain any **two** of the following : **8×2=16**

- (a) Differentiator
- (b) Wein bridge oscillatro
- (c) Schmitt trigger.

SECTION : II

4 (a) Answer the following question in brief. **10**

- (i) Classify ADCs and DACs. **2**
- (ii) Draw the frequency responses of high pass, low pass and band reject filters. **2**
- (iii) What is a multivibrator ? Define monostable multivibrator. **2**
- (iv) What do 78xx and 79xx series signify ? **2**
- (v) What is resolution of ADC ? It depends on which factors ? **2**

(b) Explain the working of monostable multivibrator using IC 555. **10**

5 (a) Explain first order high pass butterworth filter using op-amp. **8**

(b) Draw the circuit diagram of band pass filter and explain. **8**

OR

5 (a) Explain second order high pass butterworth filter using op-amp. **8**

(b) With the help of block diagram, explain voltage regulator using IC. **8**

6 Explain any **two** of the following : **8×2=16**

- (a) Sample and hold circuit
- (b) Design of voltage regulator
- (c) Dual slope type ADC.