



SE-7429

B. E. IV (Sem. VII) (IC) Examination
April / May – 2011
Industrial Drives & Control

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दृशावेक निशानीवाणी विगतो उत्तरवही पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. IV (Sem. VII) (IC)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Industrial Drives & Control"/>	<input type="text"/>
Subject Code No. : <input type="text" value="7"/> <input type="text" value="4"/> <input type="text" value="2"/> <input type="text" value="9"/>	<input type="text"/>
Section No. (1, 2,.....) : <input type="text" value="Nil"/>	<input type="text"/>
	Student's Signature

- (2) Attempt all questions.
(3) Figure to the right indicates marks.
(4) Answer of two section must be written in separate answer books.

- 1 (a) Give the answers in brief : 10
- (1) What is the electrical time constant of a D.C. drive ? 2
- (2) What are the disadvantages of the open loop control of D.C. drives ? 2
- (3) What are the different operating modes of DC motor ? 3
- (4) What is the range of output voltage of a class A chopper if the input voltage is 'V' ? 2
- (5) What are the different breaking modes of the dc drive ? 2
- (b) The chopper used for on-off control of DC separately excited motor has a supply voltage of 230 VDC, an on-time of 10 msec. and off-time of 15 msec. Assuming continuous conduction of motor current, calculate the average load current when the motor speed is 1500 rpm and has a voltage constant of $K_v = 0.5$ V/rad per sec. The armature resistance is 3Ω . 8

- 2 (a) Explain the chopper controlled DC motor set up with diagram. 8
 (b) Give two methods of speed control for DC motors. 8

OR

- 2 (a) Explain three-phase full converter DC drive. Write necessary equations. 8
 (b) Sketch the characteristics of a separately excited DC motor. Indicate clearly the constant torque and constant power drive regions. 8

3 Answer any **two** : 16

- (1) What is rheostatic break control ? Explain in detail by diagrams and mathematical expression.
 (2) Explain three-phase semi converter dc drive. Write necessary equations.
 (3) Explain the basic characteristics of dc motor with necessary diagram and equation.

- 4 (1) Name a few techniques for speed control of AC motors. 10
 (2) State the disadvantages of AC drives.
 (3) Write a few applications of AC drives.
 (4) What do you mean by slip in induction motor ?
 (5) State the two types of induction motors.
 (b) Explain series inverter. 8

- 5 (a) Explain the constant power mode of induction motor. 8
 A, 3 phase 400V, 15kW, 1440 rpm, 50 Hz., star connected induction.
 (b) Motor has rotor leakage impedance of $0.4+j.1.6 \Omega$. 8
 Calculate the motor torque for full load and the motor slip.

OR

- 5 (a) Explain the speed-torque curve of an induction motor. 8
 (b) A 400, 50 Hz, 3 phase SCIM develops full load torque remaining constant, calculate the motor speed. 8
 Assume speed torque characteristics of motor to be linear in stable region. Neglect stator resistance.

6 Write a short note on any **two** : 16

- (a) Stator frequency control
 (b) PWM inverter
 (c) Stator voltage control.