



SE-8290

**B. E. - III (Sem. V) (Instrumentation & Control)
Examination**

May / June - 2011

Sensors & Signal Conditioning

Time : 3 Hours]

[Total Marks : 100

Instructions : (1)

नीचे दशावेक निशानीवाणी विगतो उत्तरवही पर अवश्य लिखनी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. - 3 (SEM. 5) (INSTRUMENTATION & CONTROL)

Name of the Subject :
Sensors & Signal Conditioning

Subject Code No. : **8 2 9 0** Section No. (1, 2,.....) : **1&2**

Seat No. :

Student's Signature

Instructions:

- (1) Attempt all Questions.
- (2) Figure to the right indicates marks.
- (3) Answer of two sections must be written in separate answer books.

Section I

- Q-1 (a) Answer the Following questions. (10)
- 1 Define transducer? 2
 - 2 Differentiate between accuracy and precision. 4
 - 3 Define bandwidth 2
 - 4 Why dummy strain gauges are used? 2

Q-1(b) What are the different types of static errors? Explain each of them. 8

Q-2(a) With a neat sketch, explain the construction and working of inductive methods of thickness measurement. 8

Q-2(b) Define the term pH. Explain the working principle of pH measurement. 8

OR

Q-2(a) Explain the operating principle of strain gauge? And also define its gauge factor. 8

Q-2(b) Name different types of photo-electric transducer. Explain any one in detail. 8

- Q-3 Explain any two 16
- 1 Phase angle measurement
 - 2 Piezoelectric transducer
 - 3 Capacitive transducer

Section II

Q-4 (a)	Answer the Following questions.	
1	What is comparator?	2
2	Bandwidth of high pass filter is _____	1
3	Slew rate of high frequency op-amp is _____	1
4	A high pass filter has a time constant of τ . Its gain at a frequency ω is _____	2
5	Give ideal characteristics of an op-amp?	4
Q-4(b)	What are the important types of active filters? Give a brief note on each	8
Q-5(a)	Give basic circuit diagram of function generator and derive the expression of frequency for the same along with its waveforms.	8
Q-5(b)	Explain second order low pass butterworth filter. Derive necessary expression.	8
OR		
Q-5(a)	Draw the scheme of sample and hold circuit and explain its operation and application	8
Q-5(b)	What is data logger and what is its role in field of instrumentation?	8
Q-6	Explain any two	
1	Voltage to frequency converter	8
2	Wien-bridge oscillator	8
3	Amplitude modulators	8