



SF-6469

B. E. - II (Sem. IV) (Comp.) Examination

May / June - 2011

Digital Electronics

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दर्शाविए निशानीवाणी विगतो उत्तरवही पर अवश्य कभवी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. - 2 (SEM. 4) (COMP.)

Name of the Subject :
DIGITAL ELECTRONICS

Subject Code No. : 6 4 6 9 Section No. (1, 2,.....): NIL

Seat No. :

Student's Signature

- (2) Attempt all questions.
(3) Assume data if necessary.

- 1 (a) Do as directed : 10
- (i) Convert $(10101)_2$ to decimal.
(ii) Multiply $(1011.101)_2$ by $(101.01)_2$.
(iii) Define : Combinational circuit.
(iv) Convert binary to gray code 1001.
(v) Implement X-OR using NAND gate.
- (b) Design 5×32 decoder using four 3×8 decoder and one 2×4 decoder. 8
- 2 Any two : 14
- (i) Design BCD adder.
(ii) Implement universal gates
(iii) Explain decoder, demux, encoder, mux.
- 3 Any three : 18
- (i) Design and implement a 4 bit gray to binary converter.
(ii) Draw 4 bit magnitude comparator
(iii) Implement a full adder circuit with a decoder and two or gates.
(iv) Implement the following function with a multiplexer
 $F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$

4 (a) Answer the following :

10

- (i) a sequential circuit is one, whose output depends on _____.
- (a) Present inputs
 - (b) present states
 - (c) both
 - (d) none
- (ii) The characteristics equation of JK flip-flop is
- (a) $J\bar{Q} + K\bar{Q}$
 - (b) $J\bar{Q} + \bar{K}Q$
 - (c) $\bar{J}Q + K\bar{Q}$
 - (d) $\bar{J}Q + K\bar{Q}$
- (iii) How many number of flip-flops are used in master slave flip-flop ?
- (a) Two
 - (b) Three
 - (c) One
 - (d) Four
- (iv) If the value of R and S are 0,1 respectively then the present state and next states are
- (a) 1,1
 - (b) 0,0
 - (c) 0,1
 - (d) 1,0
- (v) A counter with 6 flip-flop can have the maximum number of states are :
- (a) 6
 - (b) 256
 - (c) 64
 - (d) 8
- (vi) If $J = X$ and $K = 1$ what are the present state and next states ?
- (a) 0, 1
 - (b) 1, 0
 - (c) 0,0
 - (d) 1,1
- (vii) Which of the following is an example of a sequential circuit _____ ?
- (a) Parallel adder
 - (b) Serial adder
 - (c) BCD adder
 - (d) Look ahead adder


- (viii) In _____ type of register we have access only to left most and right most flip-flops
- Serial in serial out
 - Serial in - parallel out
 - parallel in - serial out
 - Parallel in - serial out
- (ix) A digital circuit used for counting pulses is known as
- Counter
 - FF
 - Register
- (x) Johnson's counter is also called as _____ ring counter.

(b) Convert SR flip-flop to J K Flip-flop. 5

(c) Write down difference between combinational circuits and sequential circuits with example.

5 (a) What is race around condition ? How it solve ? 7
Explain with master slave JK flip/flop ?

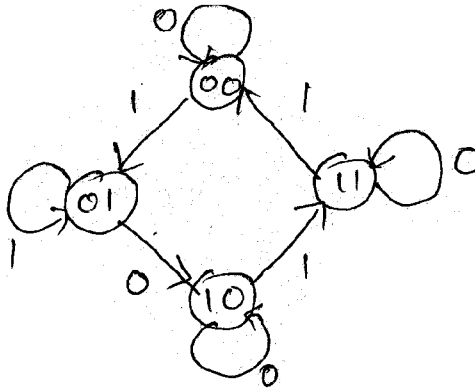(b) Write state table derive state equation and design sequential circuits using J K Flip-flop for following state diagram. 8



OR

5 (a) Explain state reduction and state assignment using example. 7

(b) Explain edge-triggered flip-flop. 8

6 (a) Explain Bidirectional shift register with parallel load. 8

(b) Design a synchronous BCD counter using T-flip.flop. 7

OR

6 (a) Design a 4-bit BCD ripple counter. 8

(b) Explain serial transfer using shift register. 8