



SF-6481

**B. E. - II (Sem. IV) (EL) (Common with EC & C)
Examination
May / June - 2011
Electrical Network - II
(Old)**

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दशांश के निशानीवाणी विगतो उत्तरवही पर अवश्य लिखनी.
Fillup strictly the details of signs on your answer book.

Seat No. :

Name of the Examination :

Name of the Subject :

Subject Code No. : Section No. (1, 2,.....) :

Student's Signature

- (2) Attempt all questions.
- (3) Assume appropriate data and give neat sketches wherever necessary.
- (4) Numerical figures to the right indicate full marks.
- (5) Scientific calculator upto casio-super fx100D, 100W, 100MS series and equivalent are permitted.

- 1 (a) Explain the following terms : 4
 - (i) Graph
 - (ii) Co-tree
 - (iii) Path
 - (iv) Fundamental tie set
- (b) Match list I and list II for fig. 1 3

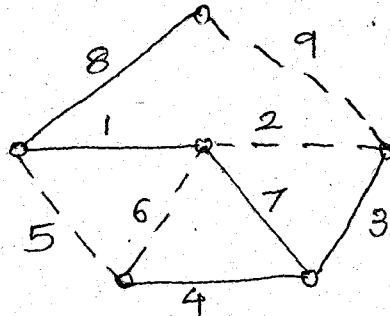


Fig. 1

- | | |
|-------------------|------------------------|
| List I | List II |
| (a) 1, 7, 4, 5 | (i) Twigs |
| (b) 2, 5, 6, 9 | (ii) Links |
| (c) 1, 3, 4, 7, 8 | (iii) Fundamental Loop |

(c) Do as directed (any three)

3

- (i) _____ sequence component of voltage is always absent in delta connection.
- (ii) For a two port network $Z_{11}Y_{11} =$ _____
- (iii) The steady state value of current in the circuit shown in fig 2 is _____.

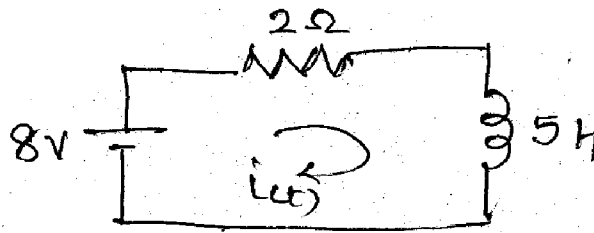


Fig. 2

- (iv) For the graph having N nodes there will be _____ fundamental cutsets.

(d) A balanced delta connected load as shown in fig. 3 10

is connected to a symmetrical 3- ϕ system. If the fuse in line C melts, determine the symmetrical components of the line currents. Under this condition current $I_a = 15 \angle 0^\circ A$

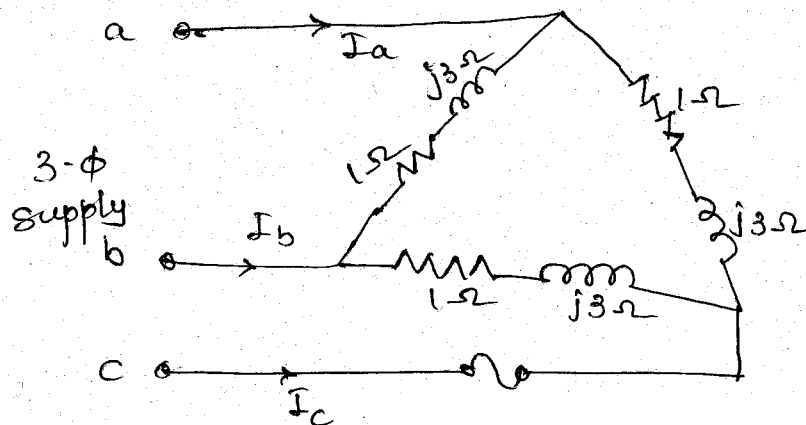


Fig. 3

- 2 (a) For the network shown in fig. 4
- (i) Draw the oriented graph 3
 - (ii) Write tie-set schedule. 3
 - (iii) Find the current through and voltage across each element. 6

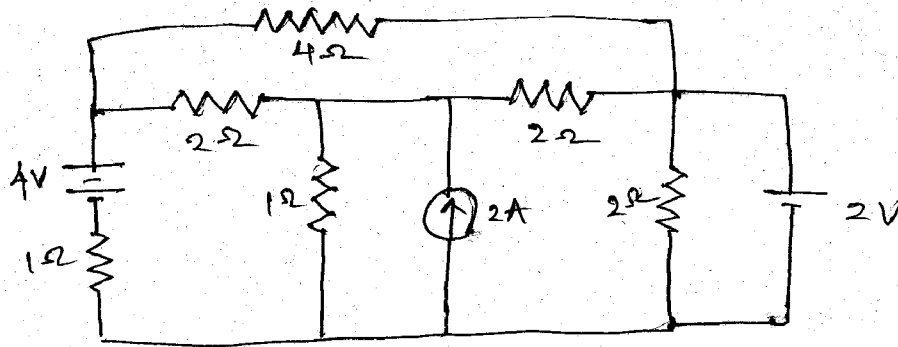


Fig. 4

OR

- 2 (a) For the network shown in fig. 4
- (i) Draw the graph 3
 - (ii) Write the cut-set schedule. 3
 - (iii) Find the current through and voltage across each branch. 6
- (b) For the network shown in fig. 5 calculate the Y parameter.

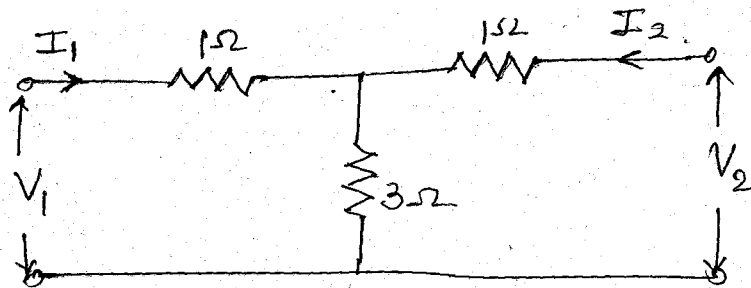


Fig. 5

- 3 (a) In the RC circuit shown in fig. 6 $R = 15\ \Omega$ and $C = 100\ \mu\text{F}$. Switch is closed at $\theta = 45^\circ$. Find current when $V(t) = 100 \sin(500t + \theta)$ is applied to the circuit at $\theta = 45^\circ$. 10

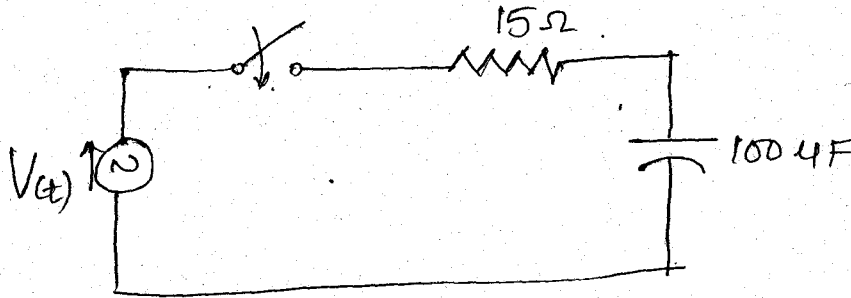


Fig. 6

OR

- 3 (a) For the circuit shown in fig. 7 S/W 'K' is opened at $t=0$. Obtain complete expression of voltage across resistance for time $t \geq 0$. Assume zero current through inductor and zero charge on capacitor before the switch 'k' is opened. 10

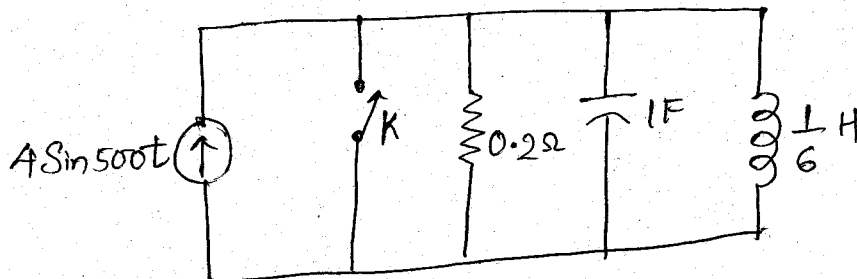


Fig. 7

- (b) Derive the expression which shows the relationship of ABCD parameters in terms of Hybrid parameters. 5

OR

- (b) Discuss the absence of zero sequence components [current and voltage] for particular cases. 5

- 4 (a) Define internal and external critical frequencies. 2
- (b) State the restrictions on the location of poles and zeros for driving point function. 4
- (c) Define image impedance. 2
- (d) State and prove separation property of one port L-C network. 5
- (e) State and explain Bartlett's bisection theorem. 4
- (f) Obtain Z_{ii} for the network shown in fig.8 3

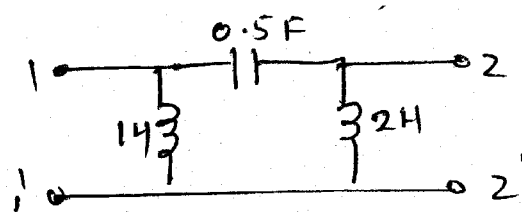


Fig. 8

- 5 Attempt any three : 15
- (a) A driving point impedance for L-C network is given by

$$z(s) = z \frac{(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

Obtain pole-zero location in S-plane and show variation of reactance w.r.t ω .

- (b) The frequency response test gives the following critical frequencies for one port loss-less n/w. Obtain all four canonical network configuration (do not determine element value).

- (c) Obtain Foster's first form of one port L-C n/w having

$$z(s) = \frac{3(s^2 + 4)(s^2 + 25)}{s(s^2 + 16)}$$

- (d) Write a note on constant K-filter
 (e) Explain Cauer's first form of reactive n/w.

- 6 (a) For symmetrical lattice network shown in fig-9, derive transfer function 8

$$\frac{v_2(s)}{v_1(s)} = \frac{R - z_a(s)}{R + 2z_a(s)}$$

where $Z_L = R$ and $Z_a Z_b = R^2$.

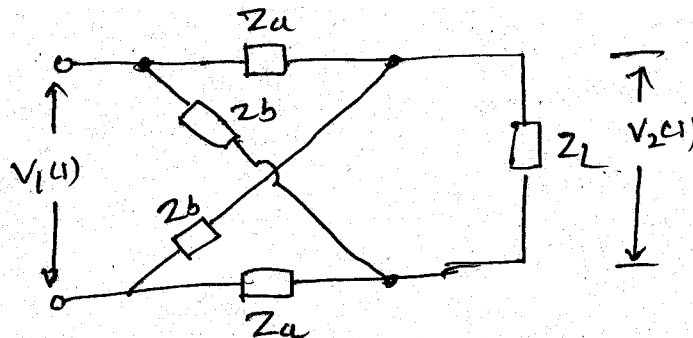


Fig. 9

- (b) Derive expression for image impedance of symmetrical T-network. 7

OR

- 6 (a) For a series R-L-C circuit $y(s) = \frac{s}{s^2 + 2s + 1.25}$ 8

Find (i) dumping ratio (ii) natural frequency of oscillation
 (iii) Quality factor (iv) Bandwidth (v) values of R,L,C
 (vi) Location of poles and zeros of Y(s).

- (b) For the network shown in fig. 10, determine pass band, 7 stop band and cutoff frequencies. Comment on the type of filter.

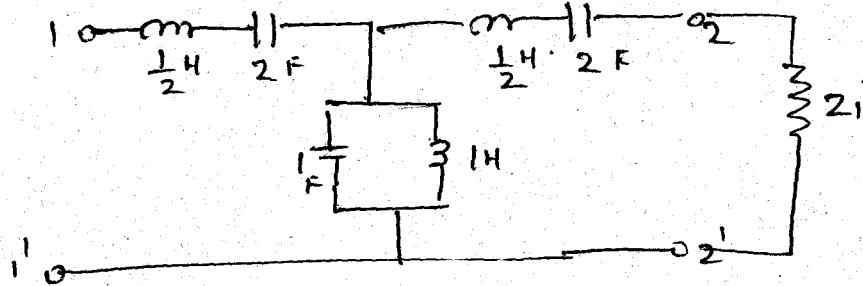


Fig. 10