



SF-6489

B. E. - II (Sem. IV) (EC / ECC) Examination

May / June - 2011

Digital Circuits

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दर्शाविए निशानीवाणी विगतो उत्तरवही पर अवश्य कभवी.  
 Fillup strictly the details of signs on your answer book.

Name of the Examination :

Name of the Subject :

Subject Code No. :     Section No. (1, 2,.....) :


Seat No. :

Student's Signature

- (2) Attempt all questions.
- (3) Assume suitable data whenever required.
- (4) Use of scientific calculator (82-fx, 82Ms, 100-fx and 100-Ms or equivalent) of other companies is allowed.

1 (a) Attempt following : 5

 
- (i) Which of the binary number is equivalent to decimal 10
  - (a) 1000                      (b) 1100
  - (c) 1010                      (d) 1001
- (ii)  $(101101)_2 - (100111)_2 = \underline{\hspace{2cm}}$
- (iii) The parity bit is
  - (a) always 1                  (b) always 0
  - (c) 1 or 0                      (d) none of above
- (iv) For the circuit shown in figure 1 the output equation is



- (a)  $Y = ABCD$               (b)  $Y = AB + \overline{CD}$
- (c)  $Y = A+BCD$             (d)  $Y = AB + \overline{CD}$

 - (v)  $\bar{A} \cdot \bar{B} \cdot \bar{C} = F$  represents a
- (a) NOR gate      (b) NAND gate  
(c) Ex-OR gate    (d) AND gate
- (b) Represent the decimal number 8620 4
- (i) In BCD  
(ii) In Excess-3 code  
(iii) In 2421 code  
(iv) As binary No
- (c) Design and implement a 4-bit binary to gray converter. 6
- (d) Explain the function of NAND gate and explain 5  
that why it is called universal gate.
- 2** Attempt any two : 16
- (a) Express the following functions in a sum of minterms  
and a product of max terms
- (i)  $F(A, B, C, D) = D(A' + B) + B'D$   
(ii)  $F(x, y, z) = 1$
- (b) Simplify the following Boolean function using K-map
- (i)  $f(w, x, y, z) = \sum (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$   
(ii)  $f = A'B'C' + B'CD' + A'BCD' + AB'C'$
- (c) Design an SOP circuit that will generate an odd parity  
bit for a 4-bit input.
- 3** Attempt any two : 14
- (a) Write short note on magnitude comparator and draw the  
ckt for the same.
- (b) Explain look ahead carry generator in detail.
- (c) Design full subtractor using half subtractor and gate.
- (d) Explain and draw the circuit for BCD adder using  
binary parallel adder IC.

- 4 (a) Answer the following questions (each of 1 mark) 10
- (i) If  $J=K=1$  in JK flip flop, what will be the next state output  $Q(t+1)$  if the previous state output was  $Q(t)=1$  ?
  - (ii) Define Sequential circuits.
  - (iii) What is the advantage of state reduction method ?
  - (iv) State true or false : “A Serial in Parallel out (SIPO) register can have all of its bits displayed at one time.”
  - (v) State atleast two application of MUX.
  - (vi) How many flip flops are required to construct mod-15 counter.
  - (vii) Give the definition of Encoder.
  - (viii) What is the difference between bidirectional shift register and unidirectional shift register ?
  - (ix) How many flip flops are required to construct 5 bit shift register ?
  - (x) A single flip flop may be used to divide the input frequency by\_\_\_\_\_.
- (b) Implement a full adder circuit with a decoder and two OR gates. 5
- (c) Explain in detail 4 to 1 line multiplexer. 5
- 5 (a) Explain in detail Master Slave flip flop. 7
- (b) Design a sequential circuit for the state diagram shown below. 8



OR

- 5 (a) Explain in detail clocked Rs flip flop. 7  
(b) Convert T flip flop into D flip flop. 8
- 6 (a) Explain bidirectional shift register with parallel load. 7  
(b) Design 3 bit binary up ripple counter using JK flip flop. 8

**OR**

- 6 (a) Explain Johnson counter in detail. 7  
(b) Draw and explain 4 bit shift register with parallel load. 8
-