



**SF-6525**

**B. E. - II (Sem. - IV) (I.C.) Examination**  
**May / June - 2011**  
**Pulse & Switching Circuit**

Time : Hours]

[Total Marks :

**Instructions :**

(1)

नीचे दृष्टावेक निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. - 2 (Sem. - 4) (I.C.)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Pulse &amp; Switching Circuit"/>	<input type="text"/>
Subject Code No. : <input type="text" value="6"/> <input type="text" value="5"/> <input type="text" value="2"/> <input type="text" value="5"/>	<input type="text"/>
Section No. (1, 2,.....): <input type="text" value="Nil"/>	<input type="text"/>
	<input type="text" value="Student's Signature"/>

- (2) Attempt all questions.  
(3) Figures to the right indicate full marks.  
(4) Assume suitable data, wherever necessary.

1 (a) Answer the following :

10

- (1) The process where by the form of a non-sinusoidal signal is altered by transmission through a linear network is called \_\_\_\_\_.
- (2) The frequency at which the gain is \_\_\_\_\_ of its maximum value is called the cut-off frequency.
- (3) The capacitor \_\_\_\_\_ the dc signal.
- (4) The process of converting pulses into pips by means of a circuit of very short time constant is called \_\_\_\_\_.
- (5) For a perfectly compensated attenuator,  $V_o(O^+)$  \_\_\_\_\_  $V_o(\infty)$ .
- (6) \_\_\_\_\_ is the process of cutting and removing a part of the waveform.
- (7) \_\_\_\_\_ circuits may be used as comparators.
- (8) In \_\_\_\_\_ clamping, the positive extremity of a waveform is fixed at the reference level and the entire waveform appears below the reference.

- (9) The clamping circuit theorem states that \_\_\_\_\_.
- (10) The low-pass RC circuit is called a \_\_\_\_\_ circuit.
- (b) Derive an expression for the rise time of the output of a RC low-pass circuit excited by a step input. 6
- (c) Distinguish between comparators and clipping circuits. 4

- 2 (a) The periodic waveform shown in Fig.1 is applied to an RC low-pass network whose time constant is  $10\ \mu\text{s}$ . sketch the output waveform. Calculate the maximum and minimum values of the output voltage with respect to ground under steady-state conditions. 10

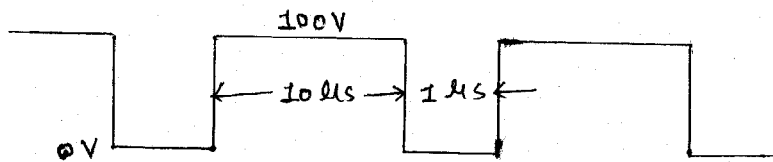


Fig.1

- (b) For sinewave input to the clipper circuit shown in Fig.2 and Fig.3. Plot output voltage waveform. 6

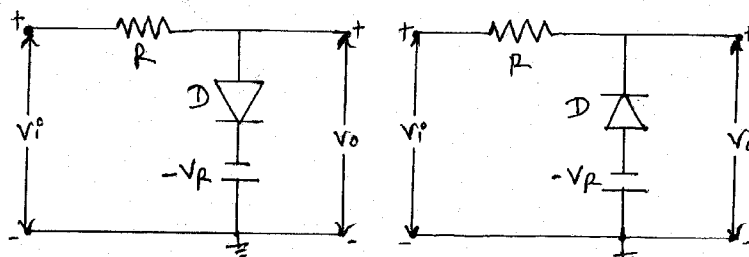


Fig.2

Fig.3

OR

- 2 (a) Compute and draw to scale the output waveform for (a)  $C_1 = 50\ \text{pF}$ , (b)  $C_1 = 75\ \text{pF}$  and (c)  $C_1 = 25\ \text{pF}$  respectively for the circuit shown in Fig. 4. The input is a 20V step. 8

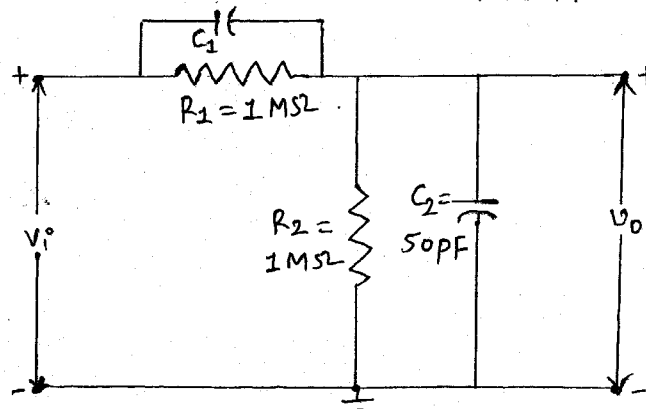


Fig.4

- (b) Derive an expression for the output of a RC low-pass circuit excited by a step input. 8

3 Attempt any two : 14

- (a) A 100V peak square wave with a period of 20ms shown in Fig. 5 is to be negatively clamped at 25V. Draw the circuit diagram necessary for this purpose. Draw the output waveform.

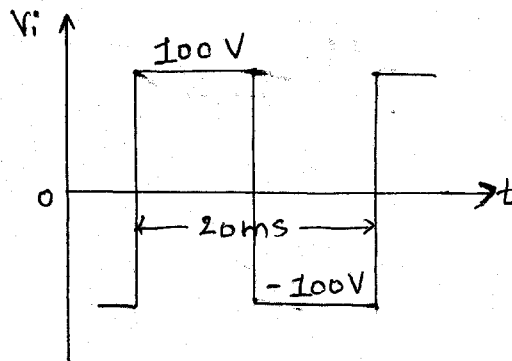


Fig.5

- (b) Derive an expression for the output of a RC high pass circuit excited by an exponential input.
- (c) For the circuit shown in Fig. 6,  $V_i$  is a sinusoidal voltage of 50 volts. Assuming ideal diodes, sketch one cycle of output voltage.

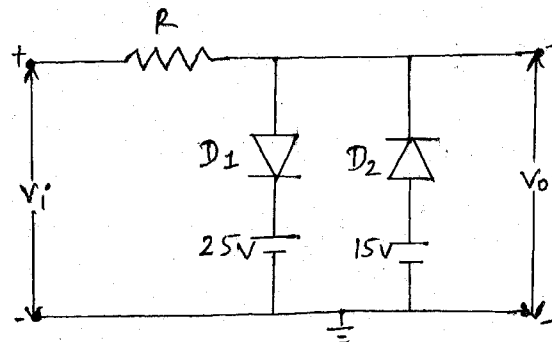


Fig. 6

- 4 (a) Give the answers : 10
- (1) \_\_\_\_\_ multivibrator is called as master oscillator.
  - (2) \_\_\_\_\_ capacitors are used to increase the speed of operation in multivibrator.
  - (3) When generators with equal frequencies run in synchronism, the synchronization is said to be on a \_\_\_\_\_.

- (4) Synchronization with pulse signals is possible only if \_\_\_\_\_.
- (5) The process of applying an external signal to induce a transition from one state to the other is called \_\_\_\_\_.
- (6) A circuit which can oscillate at a number of frequencies is called a \_\_\_\_\_.
- (7) Which are the types of multivibrator ?
- (8) The smallest allowable interval between triggers is called the \_\_\_\_\_ of the flip flop.
- (9) Storing of binary data can be done by \_\_\_\_\_ multivibrator.
- (10) Emitter coupled bistable multivibrator is commonly known as \_\_\_\_\_.
- (b) Describe a difference between a fixed bias and self bias transistor binary. 5
- (c) Describe a applications of schmitt trigger. 5
- 5 (a) Derive the expression for the gate-width T of a monostable multivibrator neglecting the reverse saturation current  $I_{CBO}$ . 7
- (b) Design an astable multivibrator to generate a square wave of 1 KHz with duty cycle of 25%. Using a transistor of  $h_{FE}=25$ ,  $I_{c(sat)}=5$  mA and  $V_{CC}=12V$ . 8
- OR**
- 5 (a) Explain a working of a emitter coupled astable multivibrator with the use of necessary waveforms and derivations. 7
- (b) The fixed bias bistable multivibrator uses n-p-n transistors with  $h_{FE}=20$ . The circuit parameters are  $V_{CC}=12V$ ,  $V_{BB}=3V$ ,  $R_C=1$  K $\Omega$ ,  $R_1=5$  K $\Omega$ ,  $R_2=10$  K $\Omega$ ,  $V_{ce(sat)}=0.4V$  and  $V_{be(sat)}=0.8V$ . Find the stable state voltages and currents. 8
- 6 Write a short note : (any three) 15
- (1) Direct connected binary
- (2) Commutating capacitors
- (3) Loading and elimination of it
- (4) Use of monostable multivibrator for frequency division
- (5) Method of improving resolution.