

- (b) Explain by load line and power calculation how inductor coupled class of power amplifier increases maximum efficiency to 50%. 5
- (c) The transistor used in inductor coupled amplifier has rating $P_{c_{max}} = 16 \text{ W}$, $BV_{CEO} = 60\text{V}$, $I_{c_{max}} = 4\text{A}$. Determine the maximum attainable swing and power dissipated to load. Assume $V_{CESAT} = 0\text{V}$ and load resistance $R_L = 8\Omega$. 5

2 Attempt any two of the following : 15

- (a) Explain the basic block diagram of feedback amplifier. Enlist the steps to recognize the type of topology of given feedback amplifier.

- (b) For the circuit shown in figure 1 the transistor parameters are $h_{fe} = 50$, $h_{ie} = 1 \text{ k}\Omega$ find

- (i) i_L/i_s
 (ii) V_o/V_s
 (iii) i_L/V_s
 (iv) V_o/i_s
 (v) R_{if}
 (vi) R_{of}

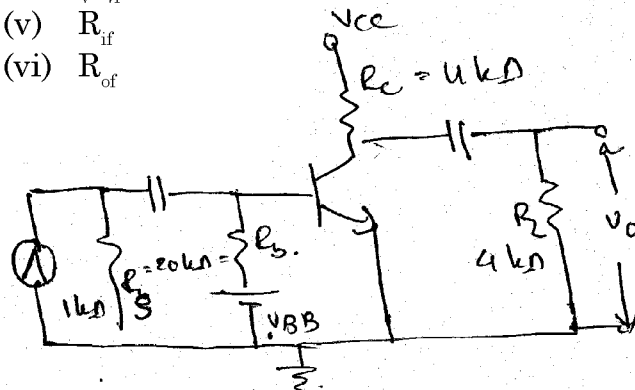


Fig.1

- (c) An amplifier with open loop voltage gain $A_v = 1000 \pm 100$ is available. Design the feedback amplifier whose voltage gain varies by no more than $\pm 0.1\%$

3 Attempt any three : 15

- (a) State different features of 78 XX series voltage regulators.
- (b) Explain different performance measurement of voltage regulators.
- (c) Explain design of low voltage using IC 723.
- (d) Draw neat and clean diagram of series and shunt voltage regulator. Write drawbacks in both regulators.

- 4 (a) Do as directed : 10
- (i) Define : Input Offset voltage
Input offset current
 - (ii) What are the limitations of open loop configurations.
 - (iii) Define : Load regulation.
 - (iv) Explain the basic principal of oscillators.
 - (v) Applications of 555 timer.
- (b) Draw and explain the ckt diagram for summing, scaling and averaging amplifier using op-amp. 8

OR

- (b) Draw the ckt diagram of Integrator and explain the same. 8
- 5 (a) Explain Wein bridge oscillator. 8

OR

- (a) Explain the first order high pass butterworth filter. 8
- (b) Explain the working of monostable multivibrator using op-amp and obtain the expression for the output pulse width and recovery time. 8
- 6 Attempt any two : 16
- (i) Explain the block diagram of basic voltage regulator.
 - (ii) Bistable multivibrator
 - (iii) Phase locked loop
 - (iv) SMPS