



**SF-8342**

**B. E. III (Sem. VI) (Electrical) Examination**

**May / June - 2011**

**Electrical & Electronic Measurement**

*(New Course)*

Time : Hours]

[Total Marks : 100

**Instructions :**

(1)

नीचे दशांशवैल निशानीवाणी विगतो उतरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<b>B. E. 3 (Sem. 6) (Electrical)</b>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<b>Electrical &amp; Electronic Measurement (New)</b>	<input type="text"/>
Subject Code No. : <input type="text" value="8"/> <input type="text" value="3"/> <input type="text" value="4"/> <input type="text" value="2"/>	<input type="text"/>
Section No. (1, 2,.....): <input type="text" value="NIL"/>	
Student's Signature	

(2) Attempt all questions.

(3) Figure to the right indicate full marks.

(4) Assume suitable data if necessary.

1 (a) Answer the following questions :

(i) List methods to measure high resistance. **2**

(ii) Wein bridge is used to measure frequency. **1**  
(State 'true' or 'false')

(iii) Megger is used to measure insulation resistance **1**  
(State 'true' or 'false')

(iv) List various types of errors. **2**

(v) Explain in brief the term : Precision. **2**

(vi) Explain in brief the term : Accuracy. **2**

(b) Derive general equation for bridge balance in case **10**  
of ac bridges. Explain how it is different from dc bridge.

2 (a) Discuss Maxwell's inductance - capacitance bridge to **10**  
measure self inductance. List its advantages and  
disadvantages.

(b) Discuss substitution method to measure medium **5**  
resistance.

**OR**

2 (a) List methods to measure capacitance and explain **10**  
schering's bridge.

- (b) A sheet of Bakelite 4.5 mm thick is tested at 50 Hz between electrodes 0.12 m in diameter. The Schering bridge employs a standard capacitor  $C_2 = 106 \text{ pF}$  capacitance, a non-reactive resistance  $R_4 = 1000/\pi \Omega$  in parallel with a variable capacitor  $C_4$ , and a non reactive variable resistance  $R_3$ . Balance is obtained with  $C_4 = 0.5 \text{ } \mu\text{F}$  and  $R_2 = 260 \Omega$ . Calculate the capacitance, power factor and relative permittivity of sheet. 5
- 3** Attempt any “three” : 15
- (i) Discuss Wheatstone bridge method to measure resistance
  - (ii) Explain measurement of resistance of earthing electrode
  - (iii) Explain : ammeter voltmeter method to measure medium resistance.
  - (iv) Discuss direct deflection method to measure high resistance.
- 4** (a) Answer the following questions (2 marks each) 10
- (i) List factors affecting CT error.
  - (ii) Define : Magnetizing force
  - (iii) List types of fault in Cable.
  - (iv) Why CT secondary must not be kept open ?
  - (v) Define : Nominal ratio, Transformation ratio in connection with instrument transformers.
- (b) Discuss fall of potential method to determine fault location in cables. 10
- 5** (a) Discuss Murray’s Loop test to localize cable faults. 8
- (b) Write a short note on : Flux meter. 8
- OR
- 5** (a) With neat sketch explain equivalent circuit of PT, phasor diagram of PT and derive expression for ratio error. 8
- (b) A CT has single turn primary and 400 secondary turns. The magnetizing current is 90 A while core loss current is 40 A. Secondary circuit phase angle is  $28^\circ$ . Calculate the actual primary current and ratio error when the secondary carries 5A current. 8
- 6** Attempt any “two” : 14
- (i) Discuss tests to find out open circuit faults in cables.
  - (ii) Discuss method to determine B-H curve of a magnetic material
  - (iii) Write a short note on : Differences between CT and PT.
  - (iv) Explain factors affecting errors of CT.