



**SB-0715**  
**Second Year B. Sc. Examination**  
**March / April – 2011**  
**Electronics : Paper - III**  
**(Electronics Circuit Design & Applications)**

Time : Hours]

[Total Marks :

**Instructions :**

(1)

<p>नीचे दृशावेक निशानीवाणी विगतो उतरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination : <b>S. Y. B. Sc.</b></p> <p>Name of the Subject : <b>Electronics : Paper - 3</b></p> <p>Subject Code No. : <b>0 7 1 5</b> Section No. (1, 2,.....): <b>Nil</b></p>	<p>Seat No. : <input type="text"/><input type="text"/><input type="text"/><input type="text"/><input type="text"/><input type="text"/></p> <div style="border: 1px solid black; border-radius: 15px; height: 80px; display: flex; align-items: center; justify-content: center; margin-top: 10px;">Student's Signature</div>
---	--

- (2) Question 1 is compulsory.
- (3) Symbols have their usual meaning.
- (4) Draw neat diagram to support your answer.
- (5) Figures at extreme right indicate full marks.

1 Answer in brief :

14

- (i) Why is collector current in transistor, slightly less than emitter current ?
- (ii) Why BJT is called current driven device where as JFET is called voltage driven device ?
- (iii) In RC coupled amplifiers, why does the gain fall-off at low and high frequencies ?
- (iv) State the merits and demerits of negative feedback in amplifiers.
- (v) What is the main purpose of using transformer coupling in a class A amplifier ?
- (vi) What do you mean by a tuned amplifier ? Where it is used ?
- (vii) Can a negative feedback amplifier works as an oscillator ? If yes, how ? If not, why ?

- 2 (a) Using approximate hybrid model analyse a CE configuration with Re bypassed and unbypassed. 7
- (b) Explain how the stabilization is obtained in potential divider bias circuit. 7

OR

- 2 (a) Draw the drain characteristics of N-channel FET. 7
- Explain :
- (1) Channel ohmic region
  - (2) Pinch-off voltage
  - (3) drain resistance
  - (4) trans conductance and
  - (5)  $I_{DSS}$ .
- (b) Determine the bias resistor  $R_B$  for fixed bias and collector to base bias and compare the stability factor S for both of them. 7

Given :

$$V_{CC} = 12V, R_L = 330 \text{ ohms}, I_B = 0.3 \text{ mA}$$

$$\beta = 100, V_{CEQ} = 6V.$$

- 3 (a) Prove that in a negative feedback voltage gain reduces and in positive feedback it increases. 8
- (b) The overall gain of a multistage amplifier is 100. 6
- When negative feedback is applied, the gain reduces to 10. Find the fraction of the output that is feedback to the input.

OR

- 3 (a) Derive expression for current gain, voltage gain, input resistance, output resistance and power gain of a transistor amplifier operating in the CE mode. Explain the significance of negative sign in the expression for the voltage gain. 8
- (b) In a transistor amplifier,  $R_C = 10 \text{ K}\Omega$ ,  $R_L = 30 \text{ K}\Omega$  and  $V_{CC} = 20V$ . The value of  $R_1$  and  $R_2$  are so as to fix the operating point at 10V, 1 mA. Draw the d.c. and a.c. load lines. Assume  $R_e$  is negligible. 6

- 4 (a) Explain the working principle of Hartley oscillator and derive its frequency of oscillator. 8
- (b) Find the operating frequency of a transistor Hartley oscillator if  $L_1 = 100 \mu\text{H}$ ,  $L_2 = 1\text{mH}$ , mutual inductance between the coils  $M = 20 \mu\text{H}$  and  $C = 20 \text{ pF}$ . 6

**OR**

- 4 (a) Explain a single tuned inductively coupled transistor amplifier. 8
- (b) Draw the circuit diagram for Bistable transistorised multivibrator. Explain its operation. What do you mean by symmetrical triggering ? 6
- 5 Write short notes on : (any two) 14
- (1) Bootstrap ramp generator.
  - (2) Heatsink theory
  - (3) JFET as VVR.
  - (4) R.C phaseshift oscillator.