



**SB-3438**

**M. Sc (Part - I) Examination**

**March / April - 2011**

**Physics : Paper - II**

**(Quantum Mechanics & General Electronics)**

Time : 3 Hours]

[Total Marks : 70

**Instructions :**

(1)

नीचे दशांश के निशानों वाली विगतो उत्तरवही पर अवश्य लिखनी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
M. Sc. (PART - 1)

Name of the Subject :  
PHYSICS : PAPER - 2

Subject Code No. : 3 4 3 8 Section No. (1, 2,.....) : 1&2

Seat No. :

Student's Signature

- (2) Use separate answer book for each section.  
(3) Symbols used have their usual meaning.  
(4) Figures to the **right** indicate full marks.

**SECTION - I**

- 1 (a) Explain Clebsh Gordan coefficients ? 3  
(b) Write down the limitations of the Klein Gordan equation. 3  
(c) Briefly discuss the admissibility condition on the wave function. 3  
(d) Find  $[x, P^n]$  2
- 2 (a) What do you mean by Normalize and Non-normalize wave function. Discuss probability interpretation and box normalization procedure in detail. 7  
(b) Prove that  $(x, p)^2 = x^2 p^2 - L^2 + i\hbar(x, p)$ . 5

**OR**


- 2 (a) Deduce and discuss the necessary equations for degenerate perturbation theory. 7
- (b) For Pauli's matrices prove that  $\sigma_x \sigma_y = -\sigma_y \sigma_x = -i\sigma_z$  5  
and  $\sigma_+ \sigma_- = 2(1 + \sigma_z)$
- 3 (a) Derive Fermi Golden Rule for transition probability per unit time for one transition to the other transition states. 7
- (b) Estimate the scattering amplitude and scattering cross section for screen coulomb potential using Born Approximation. 5

OR

- 3 (a) Using abstract operator method show that the energy eigenvalue of harmonic oscillator is 7  
 $(n + \frac{1}{2})\hbar\omega_c, n = 0, 1, 2, \dots$
- (b) Prove that linear momentum  $P_x$  is self adjoint operator. 5

SECTION - II

- 4 (a) List different types of networks. 2
- (b) Briefly explain drawbacks of fixed biasing circuit. 3
- (c) Using truth table, Show that 3  
 $\overline{A \cdot B} + A \cdot B = \overline{(A \cdot \bar{B} + \bar{A} \cdot B)}$
- (d) What is the difference between a comparator and an operational amplifier? Draw the transfer characteristics of a comparator. 3
- 5 (a) Giving example, explain Thevenin's theorem. 7
- (b) Compute  $R_{Th}$  and  $V_{Th}$  between point A and B in the following circuit. 5

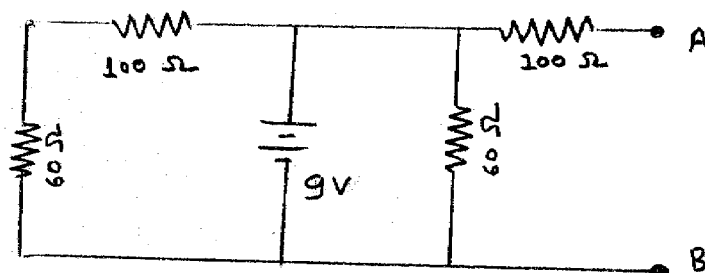

OR

- 5 (a) What is the difference between an active and a passive filter ? Draw the circuit diagram of an operational amplifier based first order band pass active filter. Draw and explain its frequency response. 7
- (b) Using operational amplifier design a circuit that finds the average of its three inputs  $V_a$ ,  $V_b$  and  $V_c$ . 5
- 6 (a) Draw the internal block diagram of an IC-555 and explain its operation as an astable multivibrator. 7
- (b) Using comparator, design a circuit that generate square wave of 1.5kHz frequency. 5

**OR**

- 6 (a) What is counter ? With waveform and truth table explain working of a three bit ripple counter. 7
- (b) Using Boolean relations simplify and implement following. 5
- (i)  $Y = \overline{A + (A \cdot B) \cdot C}$
- (ii)  $Y = (A + B) \cdot (A + C)$
-