



SB-3522

M. Sc. (Part - II) Examination
March / April - 2011
Electronics : Paper - II
(Integrated Circuit & Integrated Circuit Technology)

Time : 3 Hours]

[Total Marks : 52

Instructions :

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
M. Sc. (Part - 2)

Name of the Subject :
Electronics : Paper - 2

Subject Code No. : 3 5 2 2 Section No. (1, 2,.....) : 1&2

Seat No. :

Student's Signature

- (2) Use **separate** answer books for each sections.
- (3) Symbols used have their usual meaning.
- (4) Figures to the **right** indicate full marks.
- (5) Assume data if require.

SECTION - I

- 1 (a) For operational amplifier define following parameters : 3
(i) Input Offset voltage
(ii) Slew rate and
(iii) CMRR.
- (b) Explain the concept of virtual ground. 2
- (c) How many different output voltages can an 8 bit DAC produce ? 2
- (d) Write expressions for the Voltage gain, input and output resistances and Bandwidth for an inverting amplifier configuration. 3
- 2 (a) What is an instrumentation amplifier ? How is it useful in measurement of some physical quantities ? 4
- (b) Design a second order high pass filter to allow all frequencies above 700 Hz. Draw its expected frequency response. 4

OR

SB-3522]

1

[Contd...

- 2 (a) What is voltage to current converter ? With circuit diagram and formula, explain working of an operational amplifier based voltage to current converter circuit with floating load. 4
- (b) Design operational amplifier based differentiator circuit that converts 1 kHz triangular wave into square waveform. 4
- 3 (a) Explain the operating principle of a PLL. With necessary circuit diagram and formula, explain any one application of PLL. 4
- (b) Draw the circuit diagram of Sample and hold circuit and explain its working. 4

OR

- 3 (a) With the help of circuit diagram explain the working of a Successive Approximation ADC. 4
- (b) Assuming logic "1"=5.0 volt and logic "0"=0.0, volt, draw equivalent circuit and calculate output voltage of 4-bit R-2R DAC for the following inputs : 4
- (i) 1000_2
- (ii) 0100_2
- (iii) 0010_2
- (iv) 0001_2

SECTION - II

- 4 (a) With necessary chemical equations, explain process to produce electronic grade silicom from silica. 4
- (b) State the importance of ohmic contact fabricated by metallization in integrated circuits. 3
- (c) Explain integrated resister fabrication method. 3
- 5 (a) With schematic diagram and necessary chemical reactions, explain a float zone method of crystal growth. Compare float zone crystal growth method with Czochralski crystal growth method. 5
- (b) Determine the capacitance per unit area of the 400 \AA gate oxide of a MOSFET device. Relative permittivity of $\text{SiO}_2 = 3.9$. 3

OR

- 5 (a) What is sheet resistance ? Describe different techniques to fabricate integrated resistance. 5
(b) A base diffusion layer length is $100 \mu m$ and its width is $10 \mu m$. The sheet resistance of the layer is 100 ohm/cm^2 . Calculate its resistance. 3

- 6 (a) Explain optical lithography and compare its merits and demerits over the x-ray lithography. 5
(b) Explain Fick's one dimensional diffusion equation. 3

OR

- 6 (a) With the help of schematic diagrams, explain fabrication process sequence steps for the fabrication of NMOS devices. 5
(b) What is the stored charge and the number of electron on an MOS capacitor with an area of $4 \mu m^2$, a dielectric of 200 \AA thick SiO_2 and applied voltage of 5 Volt? 3
(Assume $\epsilon_o = 8.85 \times 10^{-14} \text{ F/cm}$ and $\epsilon_{Si}/\epsilon_o = 3.9$)
