



KD-6169

B. E. II (Sem. III) (Computer) Examination
December - 2012
Linear Electronics - I

Time : Hours]

[Total Marks :

Instructions :

(1)

नीचे दर्शावेक निशानीवाणी विगतो उत्तरवही पर अवश्य लपवी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. 2 (Sem. 3) (Computer)

Name of the Subject :
Linear Electronics - 1

Subject Code No. : 6 1 6 9 Section No. (1, 2,.....): Nil

Seat No. :

Student's Signature


- (2) Assume suitable data wherever required.
- (3) Figures on right indicate marks.
- (4) Use of scientific calculator CASIO fx-82/83 or fx-100 or equivalent of other companies is allowed.
- (5) Attempt all the questions.

1 (a) Answer the following : 10

- (1) Define Ripple factor
- (2) What is donor type semiconductor material ?
- (3) I_{CBO} is _____ current in _____ configuration.
- (4) Draw the symbol of zener diode and state where it is used.
- (5) For Si diode $V_D =$ _____
- (6) The output is taken from _____ terminal is case of an emitter follower circuit.
- (7) The voltage gain of common collector amplifier is _____.
- (8) The diode characteristic equation is _____ .
- (9) Define extrinsic semiconductor.
- (10) If both the junction of transistor are in forward biased, then transistor is in _____ region.

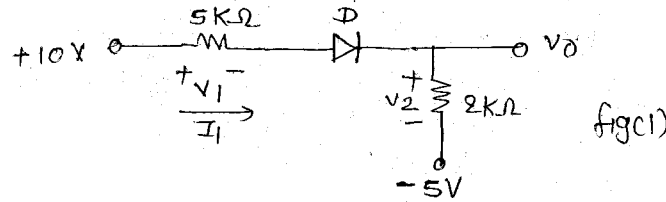- (b) (1) Draw and explain the V-I characteristics of Diode. 5
- (2) Explain the concept of diffusion capacitance. 5


- 2 (a) Draw the circuit of Half wave rectifier with capacitor filter and explain it in detail. 8
 (b) Find I_1 , V_1 , V_2 and X_0 for the given Ckt. 4



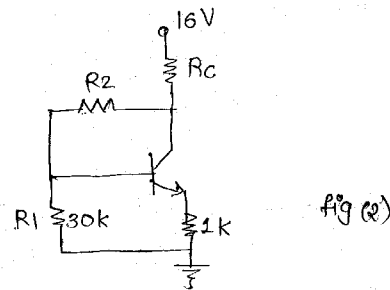- (c) Define efficiency and ripple factor of a rectifier. 3


OR

- 2 (a) Draw the Ckt of centre tap full wave rectifier and derive all the necessary equations. 10
 (b) Explain the current flow mechanism of a transistor using CB configuration. 5
- 3 (a) Explain how current amplification takes place in the transistor. 7
 (b) Calculate the value of R_2 and R_C to place Q point at $I_E = 2 \text{ mA}$ and $V_{CE} = 6V$ in the given Ckt. 8
 $V_{BE} = 0.2 \text{ V}$ and $\alpha = 0.985$ and $I_{CBO} = 4 \mu\text{A}$.



OR

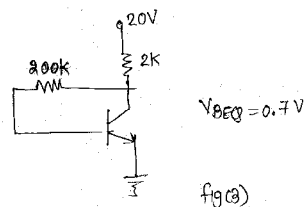- 3 (a) Calculate the minimum and maximum collector current in fig. (3). If β varies from 50 to 200. Also find variation in V_{CE} and show it on load line. Neglect I_{CBO} . 8



- (b) Why do we need transistor biasing methods ? List all of them. Explain DC bias with voltage feedback. 7

- 4 (a) Attempt the following : 10
- (1) Ic is generally made up of _____
 - (2) Define : Compensation techniques for stabilization.
 - (3) Define : Thermal resistance.
 - (4) Define : Thermal runaway.
 - (5) Classified Amplifier based on Q point.
 - (6) Darlington amplifier is sometimes also called _____
 - (7) Which semiconductors are used in fabrication of ICs ?
 - (8) What are the applications of CB, CC and CE configuration ?
 - (9) How many components are fabricated on VLSI model ?
 - (10) What happen with the gain if the number of transistor cascading transistors are increases ?
- (b) Attempt any two : 10
- (1) What do you mean by stabilization ?
Define stability factor. Derive the expression factors S_I , S_V , S_β , S_{VCE} and S_{RE} for transistor amplifier circuit.
 - (2) Explain Monolithic IC fabrication process.
 - (3) Explain Photolithography process for IC fabrication.
- 5 Write short notes : (any three) 15
- (1) Explain Phase splitter circuit.
 - (2) Explain the effect of β on Q point.
 - (3) Explain Boot Strapped emitter follower.
 - (4) Explain direct coupled amplifier circuit.
- 6 Attempt any two : 15
- (1) The idealized push pull class-B circuit has $V_{cc} = 20V$.
 $N = 1/2$, $R_1 = 20\Omega$, $h_{fe} = 20$. Determine the output signal power and collector dissipation in each transistor the circuit is designed for maximum swing.
 - (2) Darlington Amplifier
 - (3) Cascode Amplifier.
-