



KC-6185

B. E. - II (Sem. III) (EC / ECC / IC) Examination
November / December - 2012
Electronics Devices & Circuits

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. - 2 (SEM. 3) (EC / ECC / IC)

Name of the Subject :
ELECTRONICS DEVICES & CIRCUITS

Subject Code No. : 6 1 8 5 Section No. (1, 2,.....): NIL

Seat No. :

Student's Signature

- (2) Attempt all questions.
- (3) Figures to the right indicate full marks.
- (4) Programmable calculators are not allowed.
- (5) Assume suitable data wherever necessary.

1 (a) Answer the following questions : (any ten) **10**

- (1) The cut-in voltage for Ge PN junction diode is _____ volt.
(a) 0.7 (b) 0.6
(c) 0.3
- (2) The free electron is said to be in the _____ band.
(a) Conduction (b) Valence
(c) Forbidden
- (3) The peak-inverse voltage is the max reverse voltage that can be applied to a diode destruction.
True / False ?
- (4) The _____ diode can be used as light detector.
(a) LED (b) Photo
(3) Solar cell
- (5) The relation between α and β is _____.
(a) $\beta = \frac{1+\alpha}{\alpha}$ (b) $\beta = \frac{\alpha}{1-\alpha}$
(c) $\beta = \frac{\alpha}{1+\alpha}$

- (6) The transition capacitance is _____ proportional to the width of depletion region.
 (a) directly (b) inversely
- (7) The diode _____ shows a negative resistance characteristics.
 (a) Zener (b) Tunnel
 (c) PN - junction
- (8) In CB - configuration with emitter open the collector current is equal to _____.
 (a) I_B (b) I_{CEO}
 (c) I_{CBO}
- (9) For a transistor if $\alpha_{dc} = 0.99$ and $I_E = 7\text{ mA}$. Calculate I_C and I_B .
- (10) The _____ impurity is known as an acceptor impurity.
 (a) trivalent (b) tetravalent
 (c) Pentavalent
- (11) Peak inverse voltage of half wave rectifier is _____.
 (a) V_m (b) $2V_m$
 (c) $V_{m/2}$
- (12) For the switching diodes, the forward and reverse recovery times should be as _____ as possible.
 (a) Small (b) Large.
- (b) (i) Explain the forward and reverse characteristics of PN junction diode. **5**
 (ii) State the differences between Avlanche breakdown and zener break down. **5**

- 2** (a) Explain the full wave Bridge Rectifier and derive the following parameters : **8**
- (i) $I_{L, rms}$
 (ii) $V_{L, rms}$
 (iii) $P_{L, dc}$

OR

- (a) Explain the half wave rectifier and derive the following parameters : **8**
- (i) Ripple factor
 (ii) Rectifier efficiency
 (iii) TUF
- (b) Explain Rectifier with different filters. **7**

- 3 Write short notes : (any three) 15
- (1) Diode switching times.
 - (2) Shottkey diode.
 - (3) Base width modulation.
 - (4) Input and output characteristic of CE configuration.
 - (5) Light emitting diode.
- 4 (a) Attempt following questions 10
- (1) The Q point of class A Amplifier is located 1
_____.
 - (2) Explain impedance reflection in transistor. 4
 - (3) The current gain of darlington is $\beta =$ _____. 1
 - (4) Multistage amplifier are employed for having larger _____. 1
 - (5) All the _____ harmonics are automatically cancelled in the push pull amplifier 1
 - (6) What is the difference between voltage amplifier and power amplifier. 2
- (b) Discuss the characteristics of darlington amplifier. 5
- (c) Classify different power amplifier. 5
- 5 Attempt any two 12
- (i) For the Si transistor in figure $h_{fe} = 100$ and $h_{re} = h_{oe} = 0$. find h_{ie} , A_v , Z_i , Z_o . Also find A_i is the transistor amplifier is not used and load resistor of $1.5 K\Omega$ is connected directly to input.

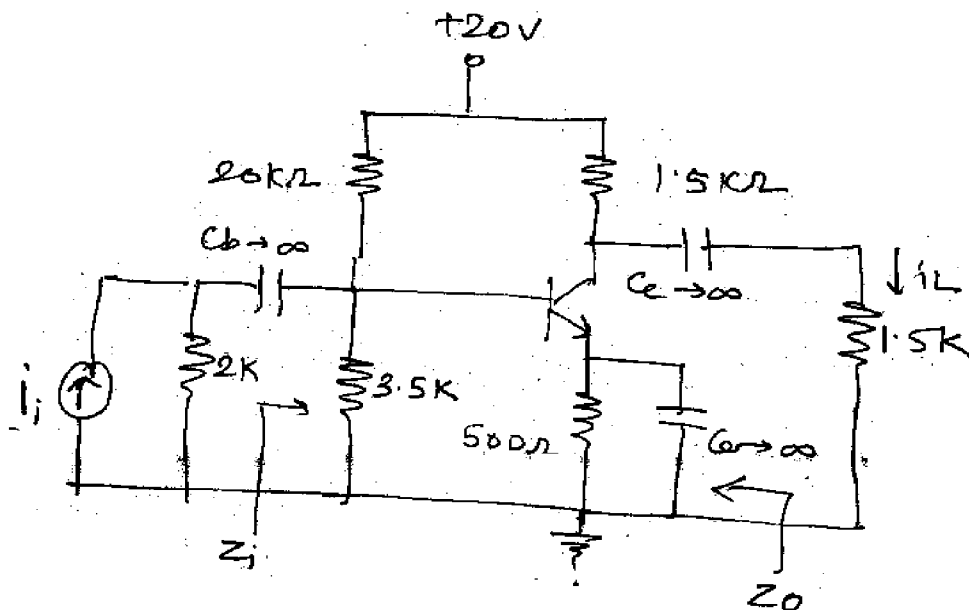


Fig.

- (ii) For the given circuit find A_v , Z_i , Z_o , $H_{fe} = 100$, $h_{re} = h_{oe} = 0$.

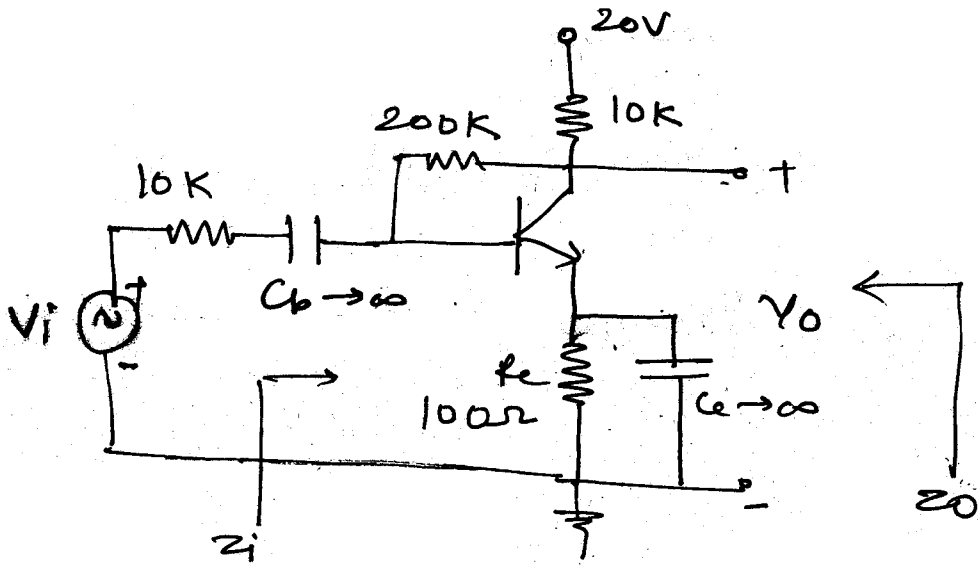


Fig.

- (iii) For transistor coupled class A power amplifier maximum power of 5 watt is to deliver to the load with $PL = 4\Omega$. The Q point is adjusted for maximum symmetrical swing and $V_{CC} = 20 V$. Find the turns ratio N , peak collector I_{cm} and efficiency.

6 Attempt any three :

18

- (1) Cascade amplifier its advantages and significance. Discuss in detail.
- (2) Write a short note on power calculations in CE amplifier
- (3) For common emitter amplifier draw circuit of an amplifier, its small signal equivalent circuit and derive expression for h parameters.
- (4) Discuss different types of power amplifier circuit in brief. Also discuss the location of Q point for various power amplifiers.