



KC-6223

**B. E. II (Sem. III) (IC) Examination**  
**November / December – 2012**  
**Electrical Circuit Theory**

Time : 3 Hours]

[Total Marks : 100

**Instructions :**

(1)

नीचे दर्शाविए निशानीवाणी विगतो उत्तरवही पर अवश्य कर्जवी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
B. E. 2 (Sem. 3) (IC)

Name of the Subject :  
Electrical Circuit Theory

Subject Code No. : 6 2 2 3 Section No. (1, 2,.....): Nil


Seat No. :

Student's Signature

- (2) Attempt all questions.
- (3) Assume necessary data whenever necessary.
- (4) Extreme right figures indicate full marks of question.
- (5) Scientific calculator FX - 100 W or equivalent students may use.

1 Do as directed :

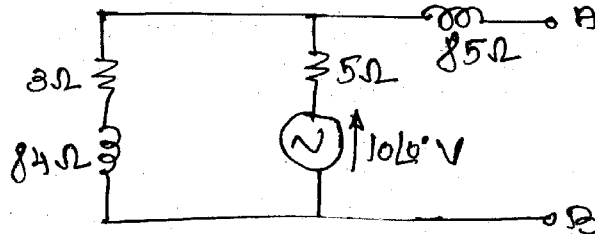
- (1) Distinguish between dependent and independent sources with suitable example. 4
- (2) State and explain superposition theorem. 4
- (3) State and explain dot rule for the coupled circuit. 4
- (4) The Thevenin equivalent impedance of the circuit in Fig is \_\_\_\_\_. 4




- (5) State whether the following statements are true or false : 4
  - (i) Superposition theorem is valid only for linear circuits.
  - (ii) Superposition theorem is not applicable to networks containing transformers.

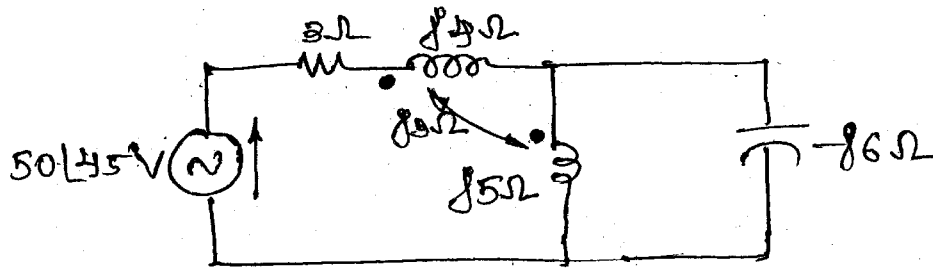- (iii) The maximum value of the coefficient of coupling is 100%.
- (iv) The value of the coefficient of coupling  $K$  is more for air cored coupled circuits compared to the iron core coupled circuits.

- 2 (a) Find the voltage drop across capacitor for the following network. 7




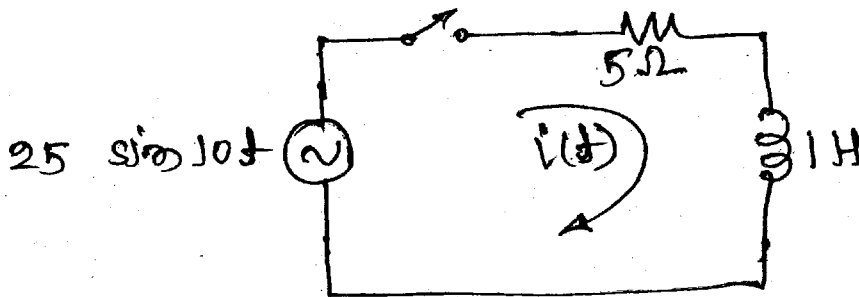- (b) For the circuit shown in Fig. a sinusoidal voltage is applied at time  $t = 0$  to a series R-L circuit. Determine the expression for current after closing the switch. 10




OR

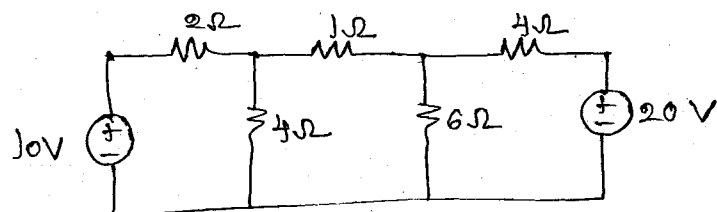- 2 (a) For the network shown in following Fig., find the power consumed in each resistor using mesh current analysis. 7




- (b) In fig, the battery voltage is applied till steady state is achieved with S/W-K open. Obtain the complete expression for current after closing S/W-K.

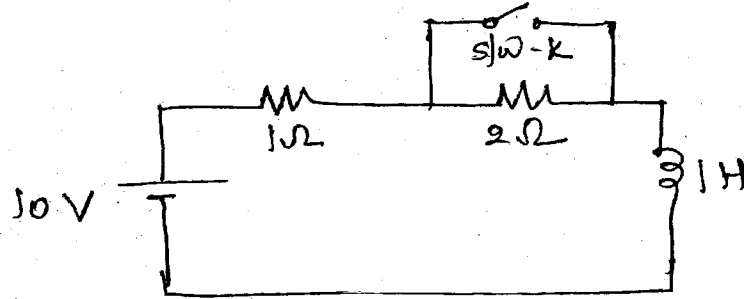


3 Attempt any **three** :

15

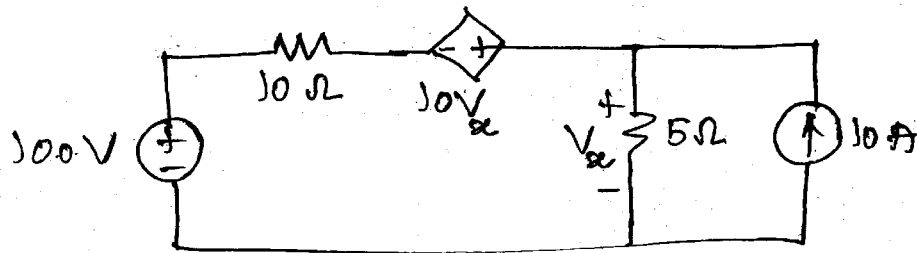
- (a) What is duality ? How can we obtain dual of the network ?  
 (b) Find the current through 10 Ω resistor for the given network.



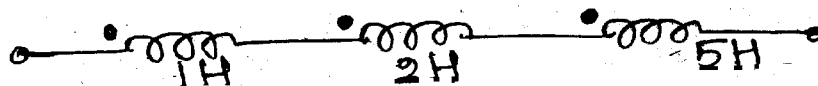- (c) For the mutually coupled coils, prove the mutual inductance  $M = K \sqrt{L_1 L_2}$   
 (d) Find the equivalent inductance of the three series connected coupled coils.




(e) Obtain dual for following N/W.

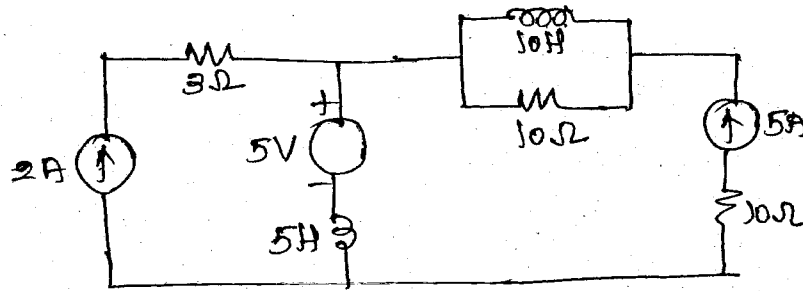


- 4 (a) Attempt all questions :  
 (each question carries **equal** marks)  
 (i) For given network, find  $R_{int}$


10

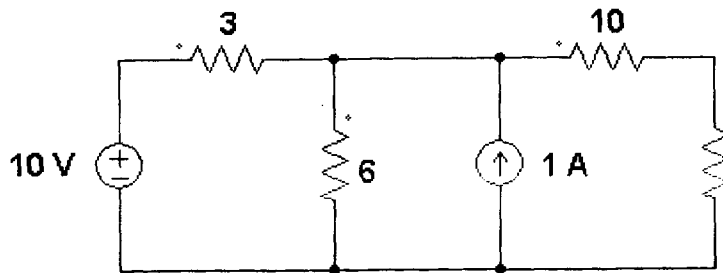

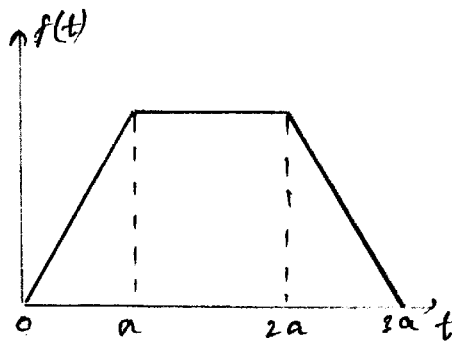- (ii) Define and explain initial value theorem.  
 (iii) Find the Laplace transformation of  $f(t) = t^n$ .  
 (iv) Find the Laplace transformation of  $f(t) = e^{-at}$   
 (v) Explain Dependent and Independent energy sources.  
 (b) Obtain the Laplace transform of the following waveform : 5  
 (i) Non-recurring wave-form



(ii) Recurring wave-form

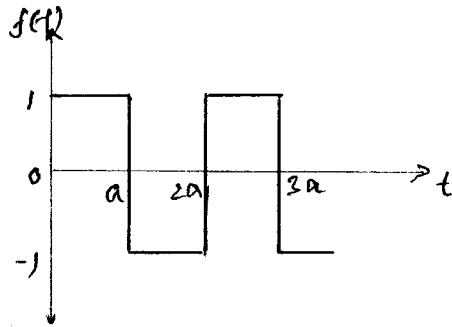

(c) Obtain inverse Laplace of the following functions : 5


(i) 
$$F(s) = \frac{s+5}{s(s^2+2s+5)}$$

(ii) 
$$F(s) = \frac{3s^2+4}{s(s^2+4)}$$

5 (a) For RLC circuit find : 7


- (i) Damping factor
- (ii) Damping ratio
- (iii) Actual frequency of oscillation
- (iv) Bandwidth
- (v) Q-factor
- (vi) Half power frequency
- (vii) Pole-zero location.

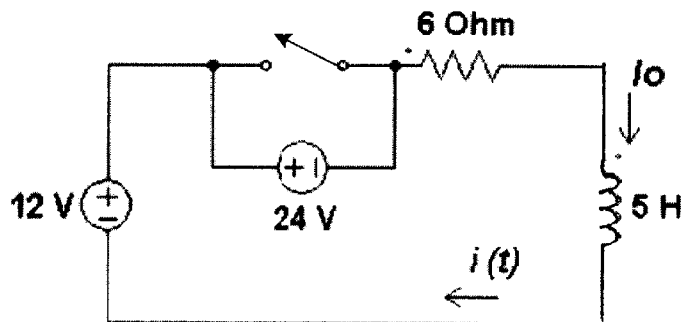(b) Find the current in the circuit shown in the figure below at an instant  $t$ , after opening the switch if a current of 0.5 A had been passing through the circuit at the instant of opening. 8




OR

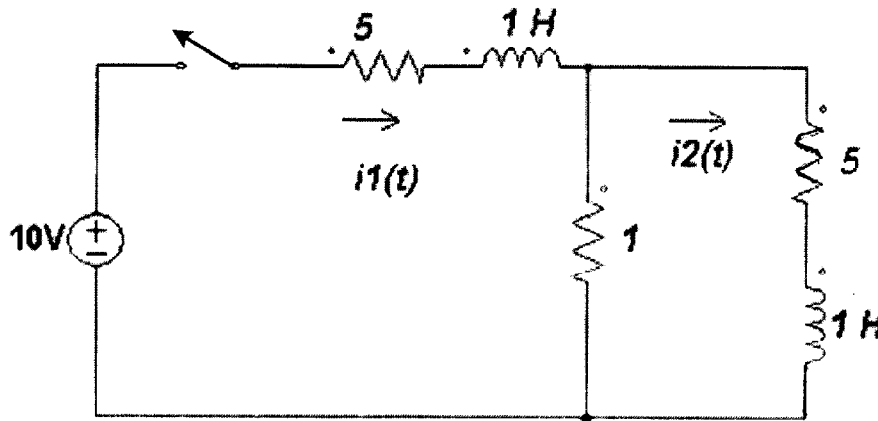- (b) Using Laplace Transform, find  $i_{2p}(t)$  at  $t = 0 +$  following closing at  $t = 0$  of switch  $k$ . Assume initial conditions to be zero. 8




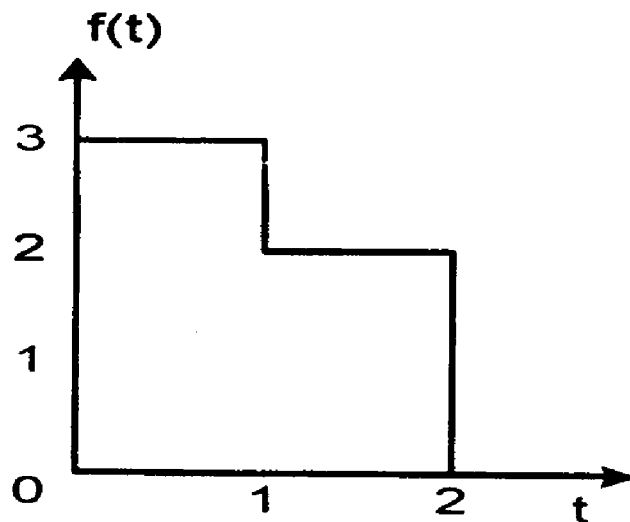- 6 Attempt any three : 15  
 (i) (a) Find the Laplace Transform of following waveform.




- (b) Draw the waveform from wave equation  
 (ii) Define following and obtain its Laplace transform :  
 (a) Unit step function  
 (b) Unit impulse function.

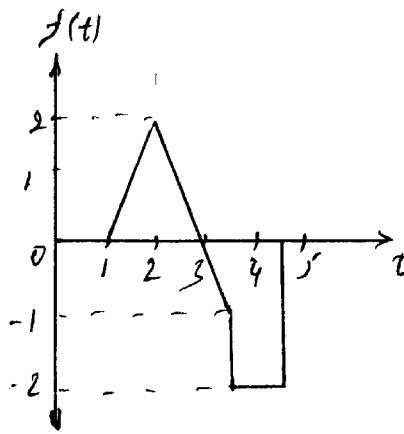(iii) Find the Laplace Transform of following waveform :




(a)

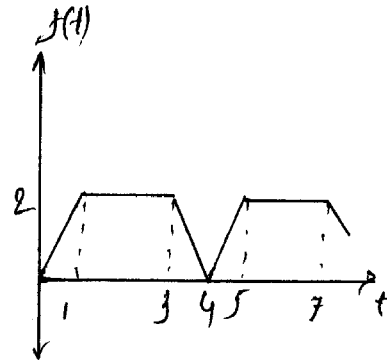

(b)

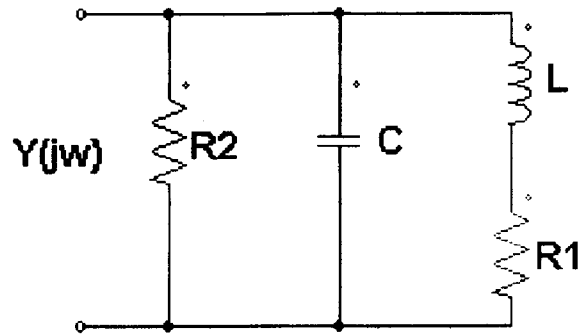(iv) Draw the polar plot of the following circuit.



(v) Prove convolution theorem to determine inverse Laplace transform.

---