



KC-6247

B. E. II (Sem. III) (IT) Examination
November/December – 2012
Electronics - I

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दर्शावेक निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. II (Sem. III) (IT)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Electronics - I"/>	<input type="text"/>
Subject Code No. : <input type="text" value="6"/> <input type="text" value="2"/> <input type="text" value="4"/> <input type="text" value="7"/>	<input type="text" value="Student's Signature"/>
Section No. (1, 2,.....) : <input type="text" value="Nil"/>	

- (2) Attempt all the questions.
- (3) Figures to the right indicate marks.
- (4) Assume necessary data whenever required.
- (5) Scientific calculators Casio FX 82/83 and equivalent are allowed.

- 1 (a) Do as directed : 10
- (i) Knee voltage for silicon diode is _____.
 - (ii) Ripple factor of a full wave rectifier is _____
and of a half wave rectifier is _____.
 - (iii) The majority carriers in N-type semiconductors are _____.
 - (iv) Zener diode is used as _____.
 - (v) Define : What is doping ?
 - (vi) Define : Forbidden Energy Gape.
 - (vii) When electron jumps from higher orbit to lower orbit, it _____.
 - (viii) In most transistors, the collector region is made physically _____ than the emitter region.
 - (ix) BJT stands for _____.
 - (x) The output resistance of a transistor is much _____ than its input resistance. (high, low)

- (b) Explain P-type Semiconductor material with diagram. 4
- (c) Explain Transition Capacitance and Storage Capacitance of diode. 6
- 2 (a) Draw and explain full wave rectifier with LC filter with suitable waveforms. Also derive the equation for ripple factor. 8
- (b) Explain effect of infinite coupling capacitor in transistor amplifier. 7
- OR**
- 2 (a) Explain concept of dynamic resistance in diode. 7
- (b) Explain working of half wave rectifier and derive expression of output voltage, efficiency and ripple factor. 8
- 3 Write short notes : (any three) 15
- (i) Explain Schottky Diode
- (ii) Explain Zener Diode
- (iii) Compare CE, CC, CB transistor configuration
- (iv) Explain N-type Semiconductor.
- 4 (a) Answer the following : 10
- (i) Define biasing. Why biasing is needed ?
- (ii) Define : Thermal run-away
Pinch off voltage
- (iii) For 102 coding on a capacitor, its value is _____ pF.
- (iv) Draw hybrid equivalent model of common emitter NPN-transistor.
- (v) The equation of pinch off voltage of NMOS is _____.
- (b) Explain the small signal analysis of CE configuration. 6
- (c) Differentiate enhancement and depletion type MOSFET. 4

- 5 (a) Explain construction and working of enhancement type MOSFET. 8
(b) Write difference between BJT and FET. 7
- OR**
- 5 (a) Explain effect of temperature on Q-point. 8
(b) Explain impedance reflection in h-parameters. 7
- 6 Write short notes on : (any three) 15
(i) Temperature compensation using two diodes.
(ii) Phase splitter circuit using BJT.
(iii) Various steps of making monolithic IC
(iv) N-channel JFET.
-