



U-6161

Second Year B. E. (Sem. III) (Computer)
Examination

June / July - 2012

Electrical Circuit Theory : Paper - II

Time : Hours]

[Total Marks :

Instructions :

(1)

नीचे दृश्यावलोकन निशानीवाणी विगतो उत्तरवही पर अवश्य लक्षणी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
S. Y. B. E. (Sem. 3) (Computer)

Name of the Subject :
Electrical Circuit Theory : Paper - 2

Subject Code No. : 6 1 6 1 Section No. (1, 2,.....): NIL


Seat No. :

Student's Signature

- (2) Attempt all questions.
- (3) Figure to the right indicate full marks.
- (4) Assume suitable data wherever required.
- (5) Scientific calculator up to Casio-super fx 100 D, 100 W, 100 MS series and equivalent are permitted.

1 (a) Do as directed : 10

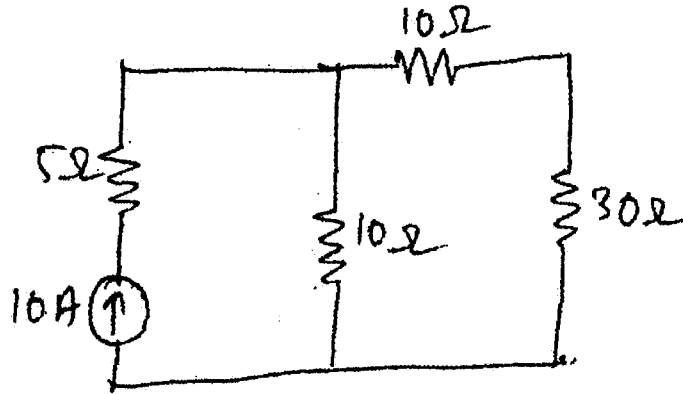- (1) The current through 30Ω branch in the given circuit is _____ . 2



(2) KCL is a consequence of law of _____ and conservation of _____ . 2

- (a) energy
- (b) charge
- (c) flux
- (d) all the above


(3) A network N with short circuit impedance matrix 2

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

is followed by an ideal transformer

with 1 : a ratio, find the overall admittance matrix.

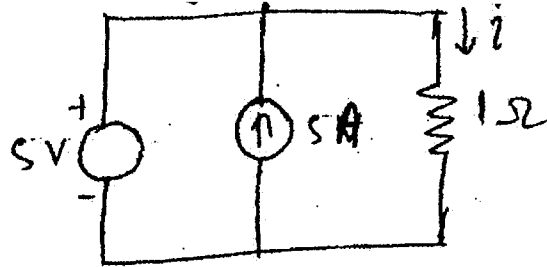(4) The value of the current I flowing in the 1Ω resistor in the circuit, shown in the fig is _____ . A. 1



(5) The current through the current coil of a 2

wattmeter is given by, $i = (1 + 2 \sin wt)$ A and voltage across the pressure coil is

$V = (2 + 3 \sin 3 at)$ v. What is wattmeter reading _____ ?


(6) What is node ?

(b) Explain Kirchoff's voltage and Kirchoff's current law in brief. 4

(c) For the mutually coupled coils circuit prove the 6


$$M = k \sqrt{L_1 L_2}$$

2 (a) Find the drop across R_L . 7

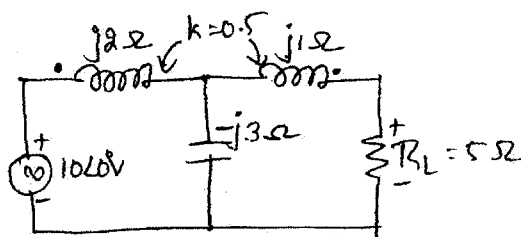

(b) Obtain the dual of the network.


5

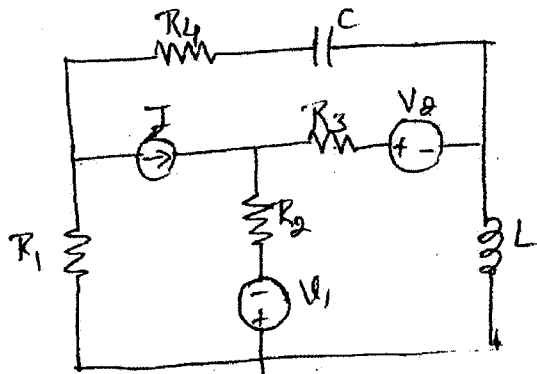

OR


2 (a) Find V_2 in the circuit, such that current in the loop-1 is zero.

7

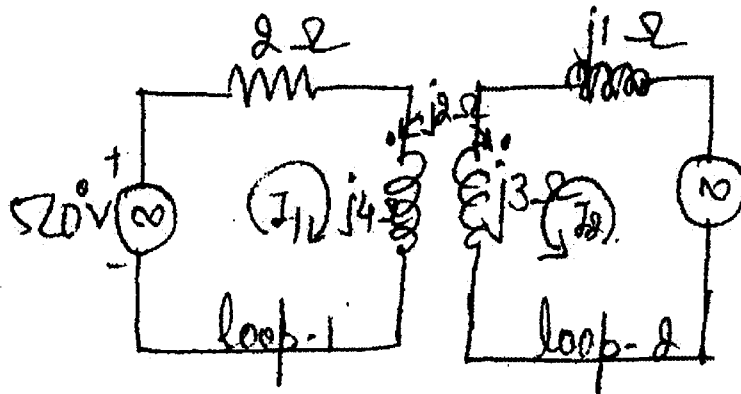

(b) Obtain the dual of the network.


5

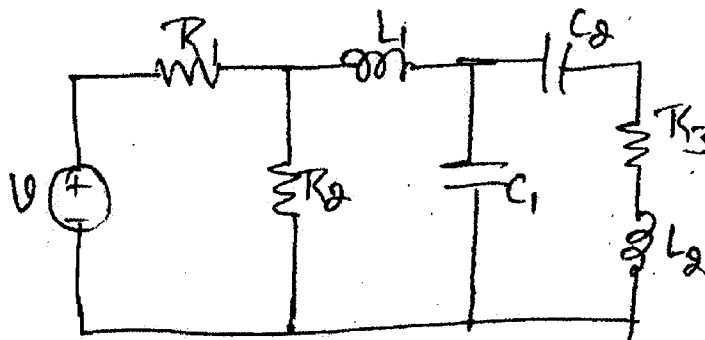


3 Attempt any three :

18

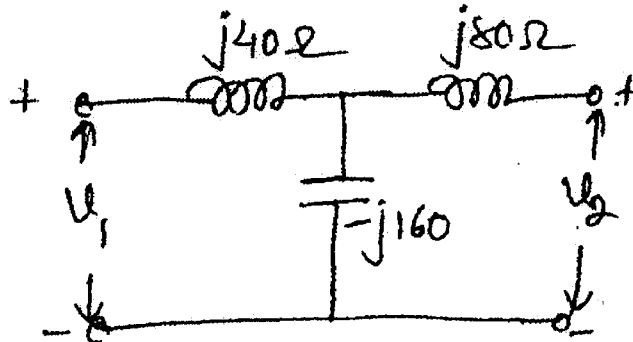
- (1) Obtain y-parameters in terms of z-parameters.
- (2) Find the open circuit parameter of given circuit.



- (3) Find v by superposition Theorem.

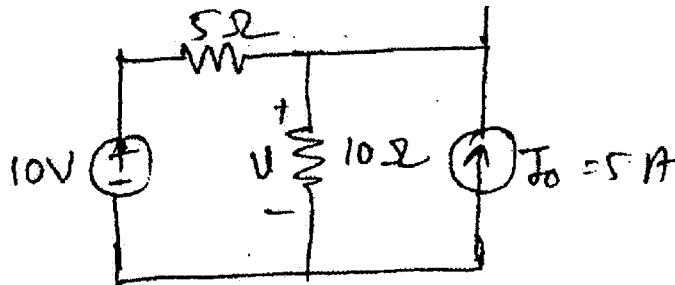

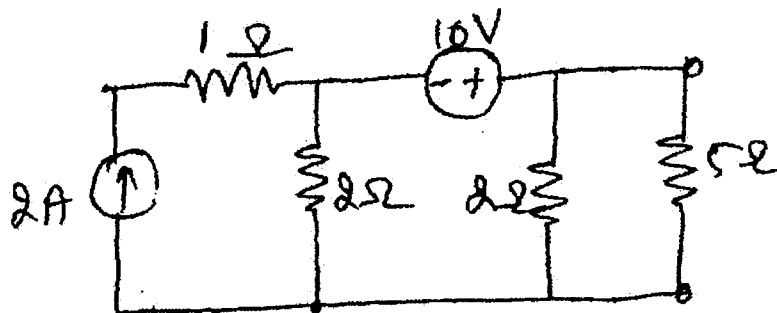
- (4) What is the current in 5Ω, resistor of the given ckt, Use Norton's theorem.



- (5) Write down the statement of Thevenin's theorem and maximum power transfer and explain it.

4 (a) Do as directed :

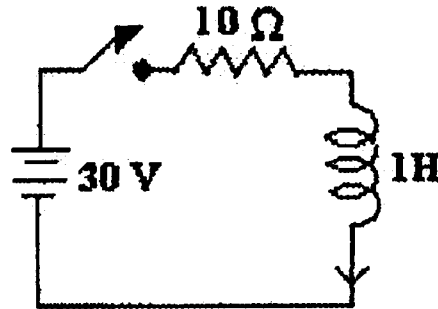- (1) For the circuit shown below current through the circuit at $t = \infty$ is _____ . 1



- (2) Write equation for voltage across capacitor in a series RC circuit. 1

- (3) Time constant for series RL circuit is _____ and for a series RC circuit is _____ . 2

- (4) Define unit ramp function and obtain its laplace transform. 2



- (5) $F(s) = S + 2/S(S+1)$, the initial value of the function is _____ and the final value of the function is _____ . 4

- (b) Match the following functions with their Laplace transformations : 5


<i>Function</i>	<i>Laplace Transform</i>
(1) $u(t)$	$1/s^2$
(2) ramp	1
(3) e^{-at}	$s/(s^2 + \omega^2)$
(4) $\cos \omega t$	$1/(s+a)$
(5) impulse	$1/s$

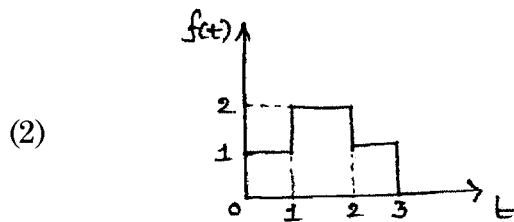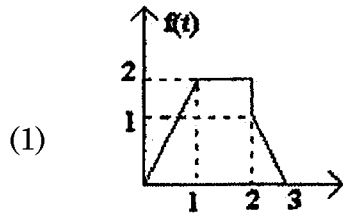- (c) State and prove final value theorem. 5

5 (a) Obtain Laplace transform of the following waveforms : 5



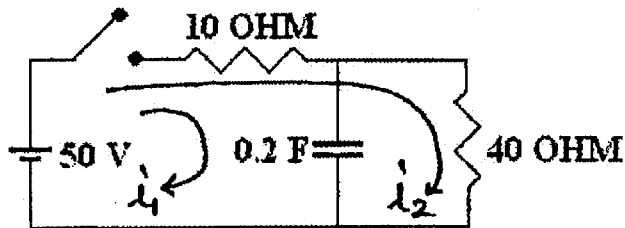(b) In two N/W shown; there is no initial charge on the capacitor. Find the loop currents i_1 and i_2 which result when the switch is closed at $t=0$, 10




OR

5 (a) Obtain inverse Laplace transformation for the following function. 5


(1) $F(s) = (2s^2 + 6s + 5)(s+1)^2(s+2)$

(2) $F(s) = 2s + 5 / (s^2 + 5s + 6)$

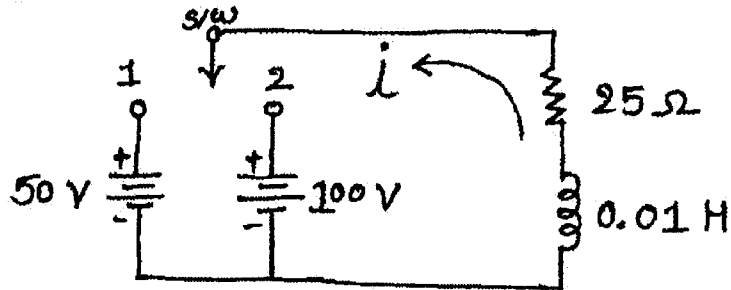- (b) In the RL circuit shown, the s/w is in position 1 for long time to establish steady state conditions and at $t=0$ it is switched to position 2, find resulting current. The direction of current is shown in fig. 10



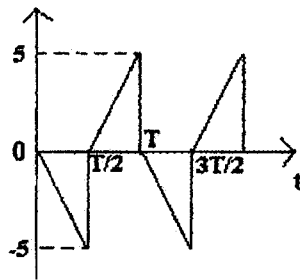- 6 (a) Evaluate the Fourier coefficient for the Fourier series. 5
 (b) Find trigonometric Fourier series for the periodic wave shown in fig. below. 10



OR

- (b) Find exponential of Fourier series for the periodic shown in fig. below. 10

