



UF-6225

**B. E. - II (Sem. - III) (Instrumentation & Control)  
Examination**

May/June – 2012

**Measurement & Instruments - IC 304 IC**

Time : 3 Hours]

[Total Marks : 100

**Instructions :**

(1)

नीचे दशांशवैध निशानीवाणी विगतो उत्तरवही पर अवश्य लपकी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/>
<input type="checkbox"/> B. E. - II (Sem. - III) (Instrumentation & Control)	<input type="text"/>
Name of the Subject :	
<input type="checkbox"/> Measurement & Instruments-IC (304 IC)	
<input type="checkbox"/> Subject Code No. : <input type="text" value="6"/> <input type="text" value="2"/> <input type="text" value="2"/> <input type="text" value="5"/> <input type="checkbox"/> Section No. (1, 2,.....): <input type="text" value="1"/> <input type="text" value="2"/>	

- (2) Attempt all questions.  
(3) Figures to the right indicate marks.  
(4) Answer of two sections must be written in separate answer books.

**SECTION - I**

- 1 (a) Give the answer in brief. 10
- (i) The high torque to weight ratio in an analog 1  
indicating instrument indicates
- (a) high friction loss  
(b) low friction loss  
(c) nothing as regards friction loss  
(d) none of these
- (ii) A reversed biased diode in addition to a forward 1  
biased diode is used in rectifier type voltmeter  
using half wave rectification. The use of reverse  
biased diode is :

- (a) It does not allow any current to flow through the meter during negative half cycle.
  - (b) It short circuits the meter during negative half cycle.
  - (c) It does not allow the reverse leakage current to flow through the meter during negative half cycle.
  - (d) all of above.
- (iii) In an electro-dynamometer type of wattmeter. 1
- (a) the current coil is made fixed
  - (b) the pressure coil is made fixed
  - (c) any of the two coils i.e. current or pressure coil can be made fixed.
  - (d) Both the coils should be movable.
- (iv) The power in a 3-phase 4-wire ckt can be 1  
measured by using
- (a) 2 watt meters
  - (b) 4 watt meters
  - (c) 3 watt meters
  - (d) 1 watt meters
- (v) A make break switch is provided to disconnect the 1  
battery when the meter is not in use in
- (a) both series and shunt type ohmmeters.
  - (b) only in series type ohmmeters.
  - (c) only in shunt type ohmmeters.
  - (d) none of the above.
- (vi) A d'Arsonval movement has a sensitivity of 1  
 $40,000 \Omega/V$  and its lateral resistance is  $4000 \Omega$ .  
The resistance of multiplier to convert it to 1 V  
voltmeter is :
- (a)  $44,000 \Omega$
  - (b)  $36,000 \Omega$
  - (c)  $3,600 \Omega$
  - (d) None of the above

- (vii) What is a d'Arsonval galvanometer ? 2
- (viii) Define 'actual transformation ratio' with respect to instrument transformer. 2
- (b) Explain different types of errors. How they can be minimized ? 8
- 2** (a) Describe the constructional detail and working of a moving iron attraction type meter. Derive its torque equation. 8
- (b) The inductance of a moving iron ammeter is given by the expression : 8
- $$L = (12 + 5\theta - 2\theta^2) \mu H,$$
- Where  $\theta$  is the angular deflection in radians from zero position.
- Determine (i) the spring constant (ii) the angular deflection in radians for a current of 10 A if the deflection for a current of 5A is  $30^\circ$ .
- OR**
- 2** (a) Describe the three ammeter method for measurement of power and power factor in a single phase circuit. Derive the expression for power and power factor. 8
- (b) A 50V range spring controlled electrodynamic voltmeter has an initial inductance of 0.25 H, the full scale deflection torque of  $0.4 \times 10^{-4}$  Nm and full scale deflection current of 50mA. 8
- Determine the difference d.c. and 50Hz a.c. readings at (i) 50V and (ii) 25V if the voltmeter inductance increases uniformly over the full scale of  $90^\circ$ .
- 3** Give answers of any two : 16
- (i) Explain the construction and principle of operation of a dynamometer type wattmeter. How it can be made to read dc as well as ac.
- (ii) Explain the principle of operation of the moving iron power factor meter.

- (iii) Explain clothier median method for testing potential transformers.

## SECTION - II

- 4 (a) Give the answers in brief : 10
- (i) The ratio of transformation in the case of 1  
potential transformers
- (a) increases with increase in power factor of secondary burden.
- (b) remain constant irrespective of the power factor of secondary burden.
- (c) decreases with increase in power factor of secondary burden
- (d) none of the above.
- (ii) Turns compensation used in current transformers 1  
primarily for reduction of
- (a) phase angle error
- (b) both ratio and phase angle errors
- (c) ratio error, reduction in phase angle error is incidental
- (d) none of the above
- (iii) Post acceleration is needed in a CRO if the 1  
frequency of the signal is
- (a) Less than 1 MHz
- (b) More than 1 MHz
- (c) More than 10 MHz
- (d) More than 10 Hz
- (iv)  $P_1$  phosphor material is used for display in 1  
CRTs for
- (a) photographic application
- (b) general purpose application
- (c) television application
- (d) all of the above

- (v) Frequency can be measured by using 1
- (a) Maxwell bridge
  - (b) Schering bridge
  - (c) Heaviside Campbell bridge
  - (d) Wien bridge
- (vi) A wheatstone bridge has ratio arms of  $1000\ \Omega$  1  
and  $100\ \Omega$  resistances, the standard resistance arm consists of 4 decade resistance boxes of 1000, 100, 10,  $1\ \Omega$  steps. The maximum and minimum values of unknown resistance which can be determined with this setup are
- (a)  $111100\ \Omega$ ,  $1\ \Omega$
  - (b)  $11110\ \Omega$ ,  $10\ \Omega$
  - (c)  $111100\ \Omega$ ,  $10\ \Omega$
  - (d) none of the above
- (vii) Give two important advantages of Maxwell bridge. 2
- (viii) Name four fluorescent materials used for CRT 2  
screen.
- (b) Draw the block diagram of CRO and explain the function 8  
of different blocks.
- 5** (a) With the help of block diagram, explain the working of 8  
Dual beam oscilloscope.
- (b) In a low voltage Schering bridge designed for the 8  
measurement of permittivity, the arm ab consists of two electrodes between which the specimen under test may be inserted; arm bc is a non-reactive resistor  $R_3$  in parallel with a standard capacitor  $C_3$  arm cd is a non-reactive resistor  $R_4$  in parallel with a standard capacitor  $C_4$ ; arm da is a standard air capacitor of capacitance  $C_2$ .

Without the specimen between the electrodes, balance is obtained with the following values;  $C_3 = C_4 = 120 pF$ ,  $C_2 = 150 pF$ ,  $R_3 = R_4 = 5000 \Omega$ . With the specimen inserted, these values become;  $C_3 = 200 pF$ ,  $C_4 = 1000 pF$ ,  $C_2 = 900 pF$  and  $R_3 = R_4 = 5000 \Omega$ . In each test,  $\omega = 5000 \text{ rad/s}$ . Find the relative permittivity of the specimen.

**OR**

- 5 (a) Describe in detail the vertical amplifier used in CRO. 8
- (b) (i) a bridge consists of the following : 4

Arm ab- a choke coil having a resistance  $R_1$  and inductance  $L_1$

Arm bc- a non-inductive resistance  $R_3$

Arm cd- a mica condenser  $C_4$  in series with a non-inductive resistance  $R_4$

Arm da -a non inductive resistance  $R_2$

When this bridge is fed from a source of 500 Hz, balance is obtained under following conditions :

$$R_2 = 2410 \Omega; R_3 = 750 \Omega; C_4 = 0.5 \mu F; R_4 = 64.5 \Omega$$

The series resistance of capacitor is  $= 0.4 \Omega$ . Calculate the resistance and inductance of the choke coil. The supply is connected between a and c and detector between b and d.

- (ii) A sheet of bakelite 4.5 mm thick is tested at 50 Hz 4  
between electrodes 0.12m in diameter. The Schering  
bridge employs a standard air capacitor  $C_2$  of  
106pF capacitance, a non-reactive resistance  $R_4$  of  
1000/πΩ in parallel with a variable capacitor  $C_4$   
and a non-reactive variable resistance  $R_3$ . Balance  
is obtained with  $C_4 = 0.5\mu F$  and  $R_3 = 260\Omega$ .  
Calculate the capacitance, power factor and relative  
permittivity of sheet.

**6 Attempt any two : 16**

- (i) Explain how 'Hay bridge' can be used for the  
measurement of inductance.
- (ii) Describe the following :
- (1) Blanking circuit
  - (2) Astigmatism control
  - (3) Sources of synchronization
  - (4) Z-axis modulation.
- (iii) Explain :
- (1) Series type ohmmeter
  - (2) Multirange voltmeter.