



UF-6241
B. E. II (Sem. III) (IT) Examination
May / June – 2012
Elements Of Electrical Engineering
(Old Course)

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

<p>नीचे दृष्टावेक निशानीवाणी विगतो उत्तरवडी पर अवश्य बपवी. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination : B. E. 2 (SEM. 3) (IT)</p> <p>Name of the Subject : ELEMENTS OF ELECTRICAL ENGINEERING</p> <p>Subject Code No. : 6 2 4 1 Section No. (1, 2,.....): Nil</p>	<p>Seat No. : <input type="text"/><input type="text"/><input type="text"/><input type="text"/><input type="text"/><input type="text"/></p> <div style="border: 1px solid black; border-radius: 15px; padding: 10px; text-align: center; width: 100%;">Student's Signature</div>
---	---

- (2) Attempt all questions.
(3) Assume suitable data wherever necessary.
(4) Figure to the right indicate full marks.

- 1 (a) Short questions : 10
- (i) Define commutation.
 - (ii) Write equation for EMF of DC generator.
 - (iii) Explain how the flux in transformer core is independent of loading ?
 - (iv) Classify losses in transformer.
 - (v) Explain slip in case of an induction motor.
- (b) (i) Explain the term "BACK-EMF". 4
- (ii) Classify losses in DC machines and write equation for efficiency of DC generator. 6
- 2 Attempt any two : 16
- (i) Explain an elementary theory of an ideal transformer. Show how an ideal transformer differs from an actual transformer ?
 - (ii) Explain how the efficiency of the transformer can be determined ? Also derive the condition for maximum efficiency.
 - (iii) Explain Swinburne's Test.

- 3 Attempt any two : 14
- (i) Classify Induction Motors. Explain different parts of an induction motor and also explain the operation of an Induction motor.
 - (ii) Write different techniques used for speed control of Three-phase induction motor and explain any one.
 - (iii) Derive relationship between stator input (P_1), air gap power (P_g) rotor copper losses (P_{co}) and mechanical power (P_m) in case of 3-phase induction motor.

- 4 (a) Short questions : 10
- (i) Two coils with self inductances of L_1 and L_2 are coupled through a mutual inductance M , the coefficient of coupling is given by_____.
 - (ii) Define open circuit parameters.
 - (iii) Define laplace transform.
 - (iv) Define "Unit Doublet" Function.
 - (v) Find Laplace of ramp function.

- (b) (i) State and explain DOT rule. 4
- (ii) Using Nodal voltage analysis find out power 6
supplied by $2 \angle 0^\circ A$ current source for the network of Fig. 1

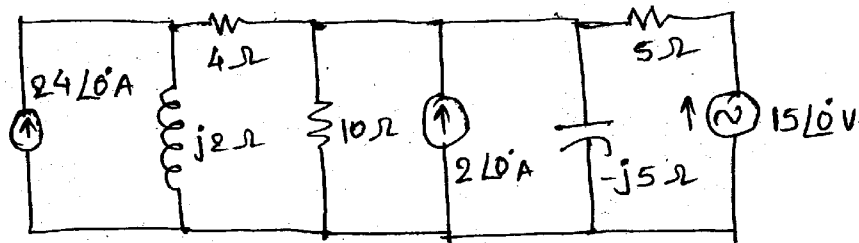


Fig. 1.

- 5 (a) For the network of Fig. 2 switch "K" is closed at time $t=0$. Capacitor C is initially charged at 10V. Using laplace transformation solve for current $i(t)$

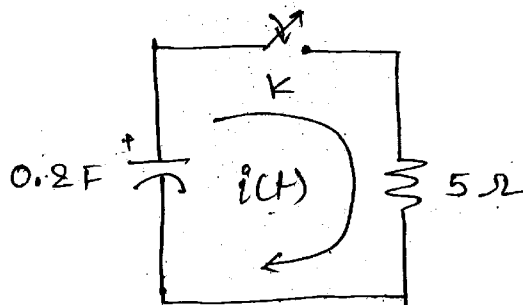


Fig. 2

OR

- (a) Find trigonometric fourier series for the wave form of Fig. 3 10

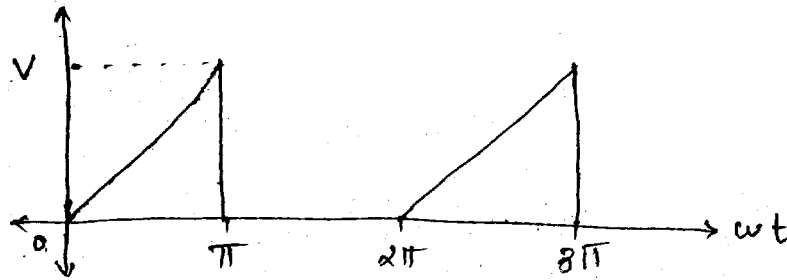


Fig. 3.

- (b) Explain meaning of symetry in fourier series and also explain its effect on fourier series constants. 5

6 Attempt any three :

15

- (a) Obtain inverse laplace transform of following transfer functions.

$$F(s) = \frac{2S^2 + 6S + 5}{(s+1)^2 (s+2)}$$

$$F(s) = \frac{3S^2 + 4}{S(S^2 + 4)}$$

- (b) Find laplace transform of given non-recurring wave forms. (Fig 4 and Fig. 5)

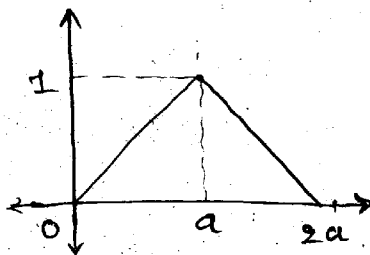


Fig. 4.

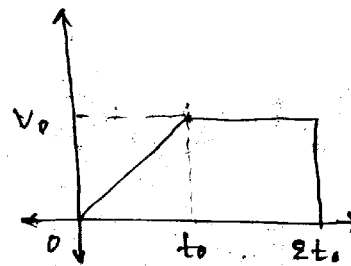


Fig 5.

- (c) Obtain Y parameters for the network shown in fig. 6


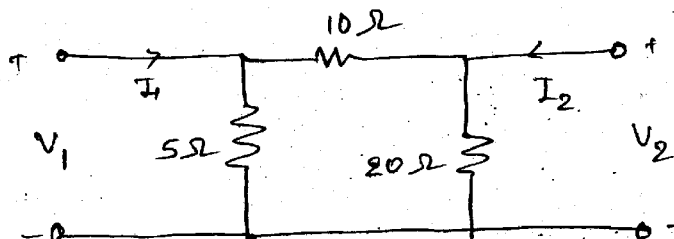


Fig. 6.

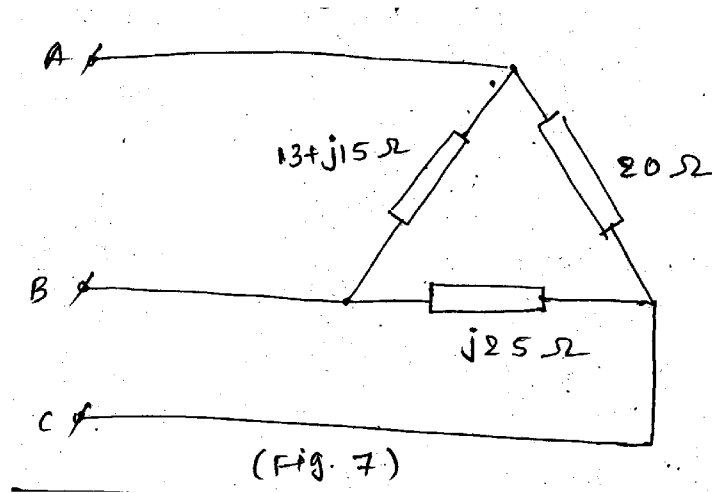- (d) A delta connected load is supplied through 415 V, 3- ϕ ABC supply. Determine line currents (Fig. 7)



- (e) Using mesh current analysis find I_3 for the network shown in fig. 8

