



UH-6181

B. E - II (Sem. - III) (Common with EC & C)

Examination

May/June - 2012

Electrical Network - I

Time : 3 Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दृशावेव निशानीवाणी विगतो उत्तरवाडी पर अवश्य कभववी.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :  
B. E - II (Sem. - III) (COMMON WITH EC & C)

Name of the Subject :  
Electrical Network - I

Subject Code No. : 6 1 8 1 Section No. (1, 2,.....): Nil


Seat No. :  
[ ] [ ] [ ] [ ] [ ] [ ]

Student's Signature


- (2) Attempt all questions.
- (3) Figures to right indicate marks.
- (4) Scientific calculator upto casio-super fx 100D, 100W, 100MS series and equivalent are permitted.
- (5) Assume suitable data wherever necessary.

1 (a) Fill in the following blanks :

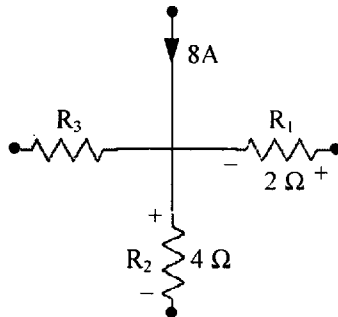
- (i) The mutual inductance in a coupled circuit is given by \_\_\_\_\_ 1
- (ii) While calculating  $R_{TH}$ , constant current source in the circuit is replaced by \_\_\_\_\_ 1
- (iii) In an electrical circuit, dual of capacitor is \_\_\_\_\_ 1
- (iv) The voltage drops across  $R_1$  and  $R_2$  are 10V and 16V with polarities as indicated, The current in  $R_3$  is \_\_\_\_\_ 1



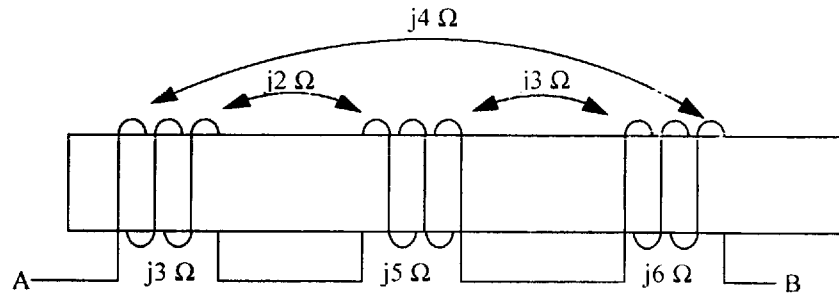
- (v) The mesh analysis is primarily based on the application of \_\_\_\_\_ 1
- (b) State and explain maximum power transfer theorem. 5
- (c) Explain independent and dependent sources. 5
- (d) Equivalent reactance between A-B is \_\_\_\_\_. 5



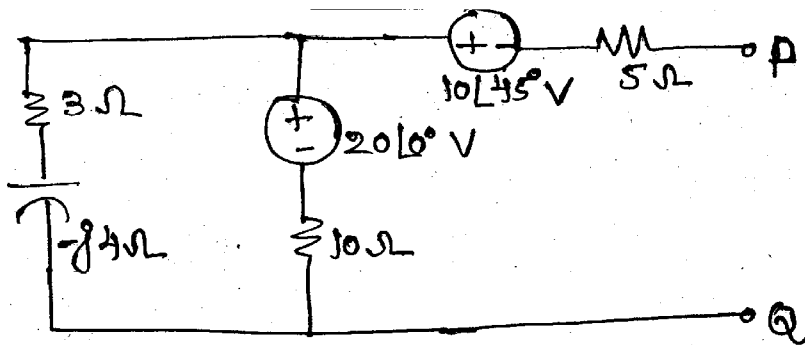
- 2 Attempt any three : 15
- (i) Obtain Thevenin's equivalent circuit for the network shown in the figure below at terminals P-Q.



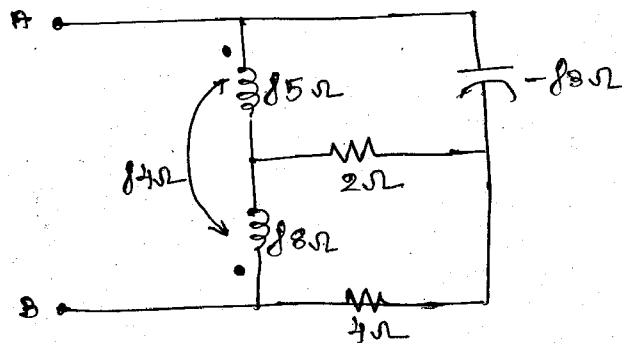
- (ii) Determine equivalent impedance between terminals A-B for the coupled circuit given below. (Assume  $k=1$ .)



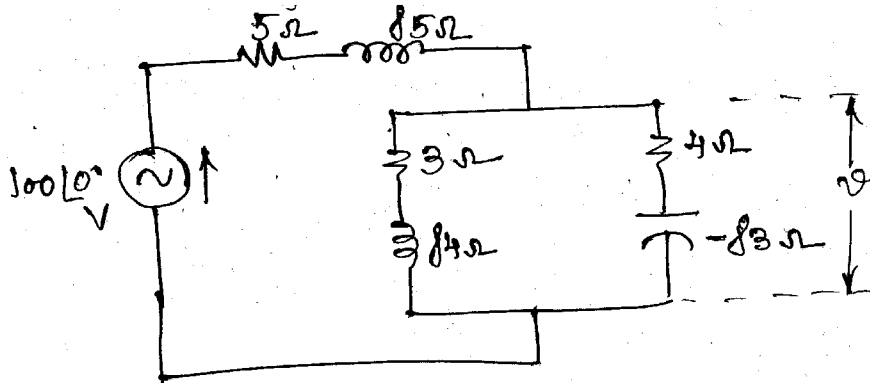
- (iii) Find the voltage across the parallel impedance by the modal method.



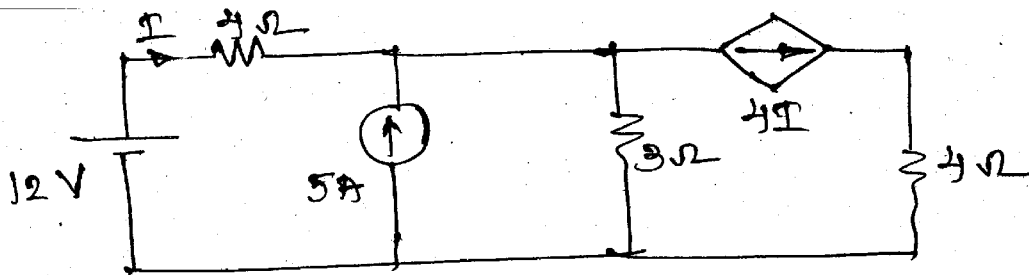- (iv) Find current I by Thevenin's theorem for the network given below.




- (v) Calculate current I for the coupled circuit given.

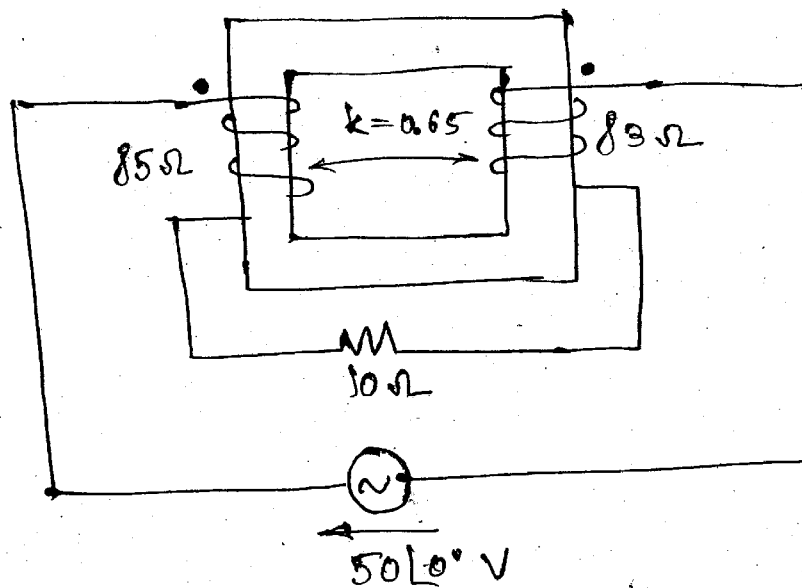

3 Attempt any two :

15

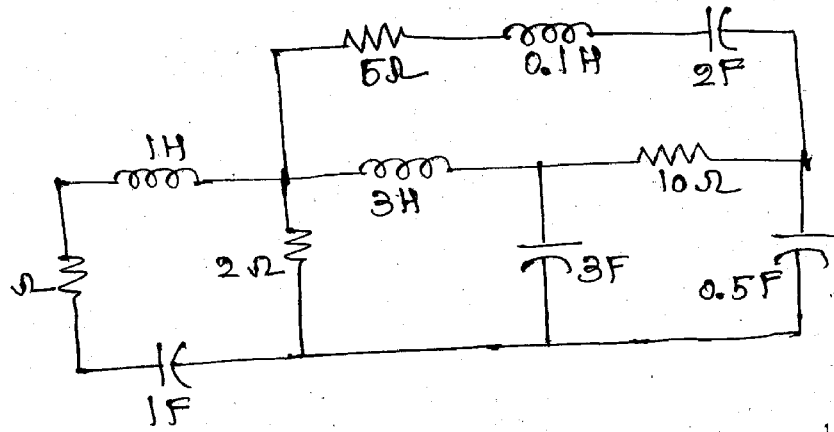
- (i) Explain the concept of duality and obtain the dual of following network.



- (ii) A three phase, 3 wire, 100V, ABC system supplies a delta connected three equal impedances of  $5\angle 45^\circ \Omega$ . Determine the line currents  $I_A, I_B, I_C$ . Draw phasor diagram.
- (iii) Derive the expression of displacement neutral voltage for unbalanced, three-wire, star connected load.

4 (a) Do as directed :

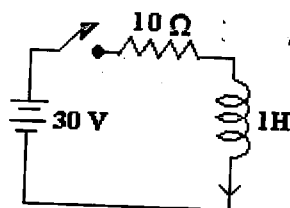- (i) Write equation for voltage across capacitor in a series RC circuit. 1
- (ii) For the circuit shown below current through the circuit at  $t = \infty$  is \_\_\_\_\_. 4



(iii) Write basic equations for Y-parameters and its values. 3



(iv) Define unit step function and obtain its laplace transform. 2

(b) Match the following functions with their Laplace transformations. 5


Function	Laplace Transform
(1) $u(t)$	$1/s^2$
(2) impulse	1
(3) $e^{at}$	$s/(s^2 + \omega^2)$
(4) $\cos \omega t$	$1/(s-a)$
(5) ramp	$1/s$

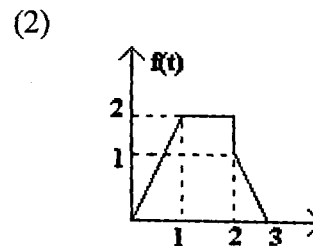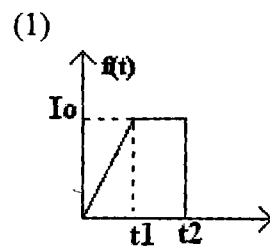(c) State and prove final value theorem. 5

5 (a) Obtain Laplace transform of the following waveforms : 5




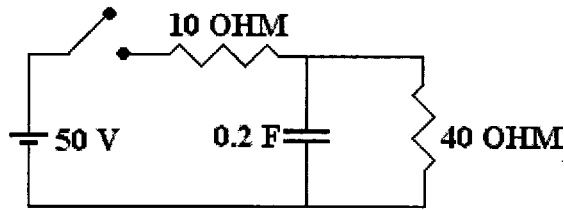(b) In two mesh N/W shown; there is no initial charge on the capacitor. Find the loop currents  $i_1$  and  $i_2$  which result when the switch is closed at  $t=0$ . 10




OR

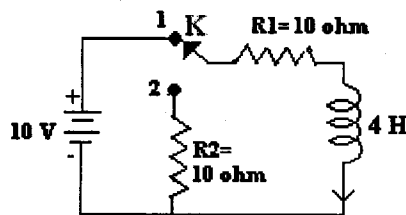- 5 (a) Obtain Inverse Laplace transformation for the following 5  
function :
- (i)  $F(s) = (2s^2+6s+5)/(s+1)^2(s+2)$
- (ii)  $F(s) = 2s + 5/(s^2+5s+6)$
- (b) In the RL circuit shown, the s/w K moved from position 10  
1 to position 2 at  $t=0$ . The steady state current having  
previously established in the RL circuit. Find the  
particular solution for current  $i(t)$  after switching.




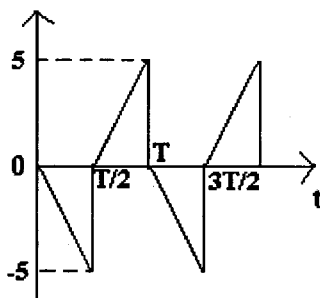- 6 (a) Evaluate the Fourier coefficient for the Fourier series. 5
- (b) Find trigonometric Fourier series for the periodic wave 10  
shown in fig. below.



OR

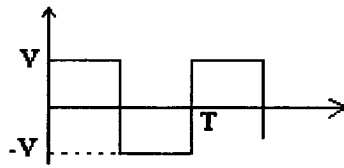- (b) Find exponential Fourier series for the periodic wave shown in fig. below. **10**



---