



UH-6185

B. E. II (Sem. III) (EC/ECC/IC) Examination

May / June – 2012

Electronics Devices & Circuits

Time : Hours]

[Total Marks : 100

Instructions :

(1)

नीचे दृष्टावेक निशानीवाणी विगतो उतरवडी पर अवश्य लपवी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. 2 (Sem. 3) (EC/ECC/IC)

Name of the Subject :
Electronics Devices & Circuits

Subject Code No. : 6 1 8 5 Section No. (1, 2,.....): Nil

Seat No. :

Student's Signature

- (2) Attempt all questions.
(3) Figures to the right indicate full marks.
(4) Programmable calculators are not allowed.
(5) Assume suitable data whenever necessary.

1 (a) Answer the following questions : (any ten) 10

- (i) The electronics in the _____ band are responsible for the flow of current
(a) forbidden
(b) valence
(c) conduction
- (ii) For a certain transistor $\alpha_{dc} = 0.97$ and $I_E = 5\text{mA}$. Calculate I_C and I_B .
- (iii) In a transistor _____ region is very lightly doped and very thin.
(a) Collector
(b) Emitter
(c) Base
- (iv) The peak inverse voltage of each diode in a full wave rectifier with centertap transformer is _____.
(a) V_m
(b) $2V_m$
(c) $U_{m/2}$

- (v) The _____ impurity is called as a donor impurity.
- trivalent
 - tetravalent
 - pentavalent
- (vi) Name the three operating region of the transistor.
- (vii) The photo diode operates on _____ effect.
- photoconductive
 - Photovoltaic
 - Photo emissive
- (viii) The process of adding impurities to intrinsic semiconductor is known as _____
- (ix) The relation between α and β _____.
- $\beta = \frac{\alpha}{1+\alpha}$
 - $\beta = \frac{1+\alpha}{\alpha}$
 - $\beta = \frac{\alpha}{1-\alpha}$
- (x) The transition capacitance is _____ proportional to the width of depletion region.
- directly
 - inversely
- (xi) The depletion region penetrates more into _____ doped region.
- heavily
 - lightly
 - equally
- (xii) The DC resistance of the diode is also known as _____ resistance.
- dynamic
 - static
 - forward
- (b) (i) Explain the input and output characteristic of CB 5 configuration of transmitter.
- (ii) Explain the forward and reverse characteristic of 5 PN junction diode.

2 (a) Explain the full wave Centertap Rectifier and derive the following parameters : 8

- (i) $I_{L,rms}$
- (ii) $V_{L,rms}$
- (iii) $P_{L,de}$

OR

(a) Explain the full wave Bridge Rectifier and derive the following parameters. 8

- (i) TUF
- (ii) Rectifier efficiency
- (iii) Ripple factor

(b) Explain the base width modulation. 7

3 Write short notes : (any three) 15


- (i) Light emitting diode
- (ii) Rectifier with different filters.
- (iii) Zener diode as a voltage Regulator.
- (iv) Diode capacitances.
- (v) Emitter follower

4 (a) Answer the following in brief : 10


- (i) Why silicon type transistors are more often used than germanium type ?
- (ii) What is quiescent point ?
- (iii) What is the difference between voltage amplifier and power amplifier ?
- (iv) Define the following h-parameters :
 - (a) h_{ie}
 - (b) h_{oe}
- (v) What are the main characteristics of darlington amplifier ?

(b) Explain current amplification in the transistor. 5

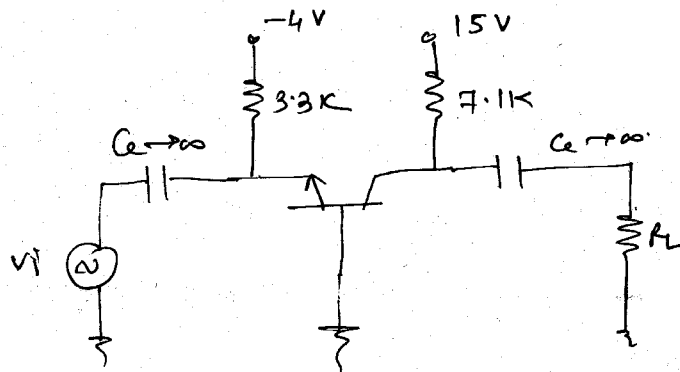(c) For Si transistor of fig. given below $\beta=100$, $I_{CBO} = 0$ find I_{BQ} and V_{CEQ} . 5



- 5 (a) Draw and explain direct coupled push-pull amplifier. 7
Write its advantages and disadvantages.
- (b) In the figure given below the BJT has $h_{fe} = 50$. All 8
bypass and coupling capacitors are assumed to have zero reactance at signal frequency.
Find
- quiescent conditions
 - small signal equivalent circuit neglecting h_{oe} , h_{re}
 - The current gain $A_i = i_L/i_i$
 - i/p and o/p impedances.

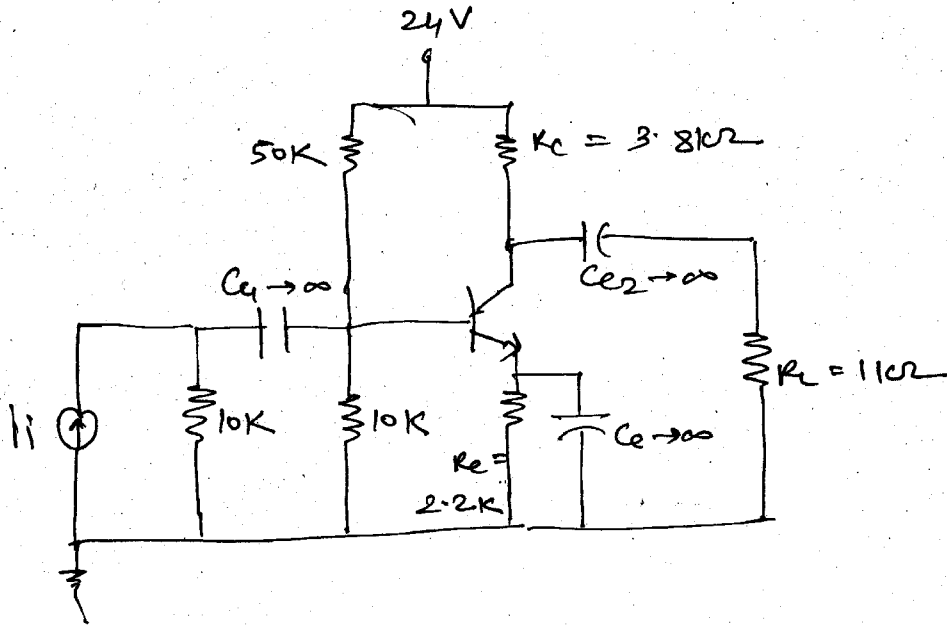

OR

- 5 Answer the following :
- Obtain CB h-parameters in terms CE h-parameters. 8
 - A single transistor is operating as an ideal class-B. 7
amplifier with $1\text{ K}\Omega$ load. A dc meter in the collector circuit reads 10 mA. How much signal power is delivered to the load ?
- 6 Write shortnotes on : (any three) 15
- Cascade amplifier
 - Impedance reflection in the transistor
 - Class C-amplifier
 - Difference amplifier with constant current source.