



UH-6223

B. E. II (Sem. - III) (IC) Examination
May/June - 2012
Electrical Circuit Theory

Time : 3 Hours]

[Total Marks :100

Instructions :

(1)

नीचे दर्शाविए निशानीवाणी विगतो उत्तरवडी पर अवश्य लपवी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. 2 (Sem. - 3) (IC)

Name of the Subject :
Electrical Circuit Theory

Subject Code No. : **6 2 2 3** Section No. (1, 2,.....) : **Nil**


Seat No. :

Student's Signature

- (2) Attempt all questions.
(3) Assume necessary data whenever necessary.
(4) Extreme right figures indicate full marks of question.
(5) Scientific calculator FX-100 W or equivalent students may use.

1 (a) Do as directed :

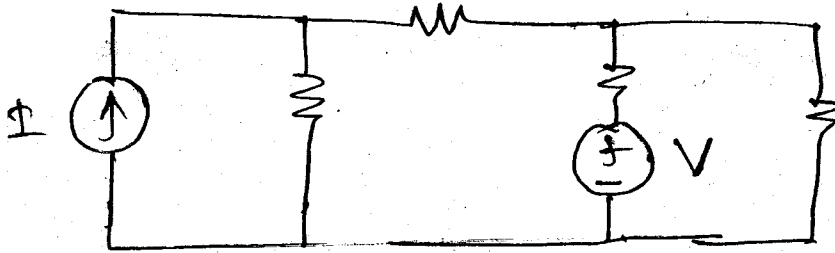
- (i) A network is said to be non linear if it does not satisfy super position condition. (True/False) 1
- (ii) Draw the oriented graph and all the possible trees for the following network. 2




- (iii) Distinguish between dependent and independent sources. 2
- (iv) If the coefficient of coupling $k=1$, it is called perfect coupling. (True/false) 1
- (v) Explain maximum power transfer theorem. 2

(vi) Find total inductance of the coil.


2

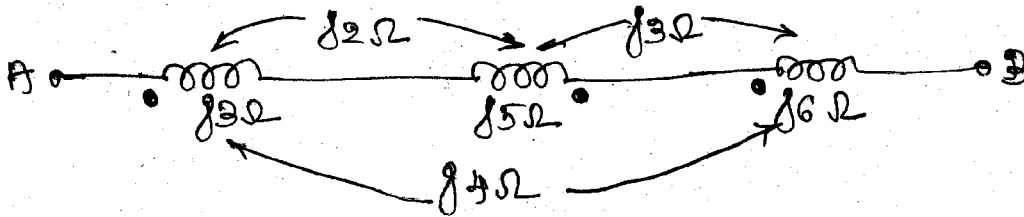

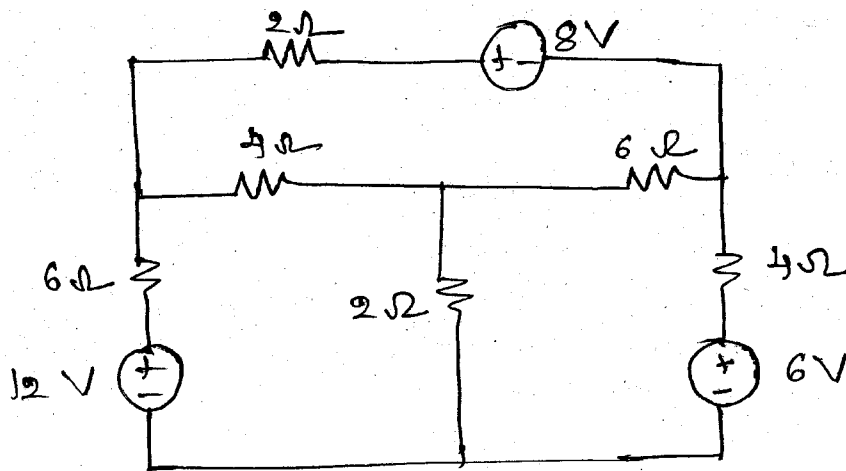(b) For the network shown below draw the oriented graph, write the tie-set schedule and hence obtain all branch currents. 10



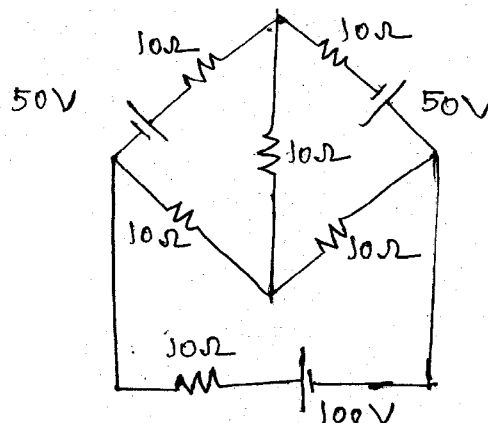
2 (a) State and explain dot rule for mutually coupled coils. 5
 (b) Determine the current supplied by the 100 V battery for the circuit shown below. 10




OR

2 (a) Explain mesh analysis and nodal analysis as applied to electrical networks. 5

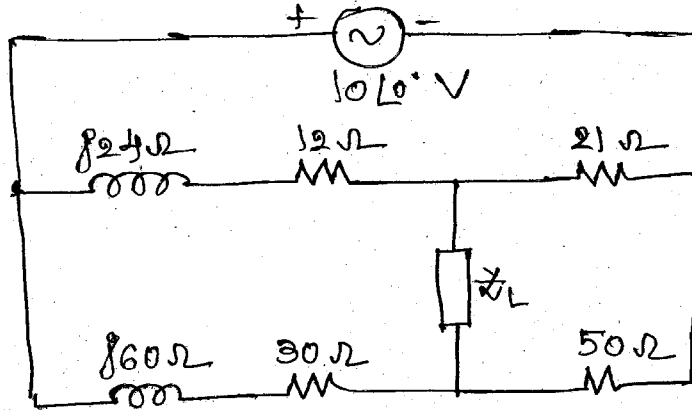
- (b) For the network shown in fig. below, find the value of Z_L so that the power transfer from the source is maximum. Also calculate P_{\max} . 10



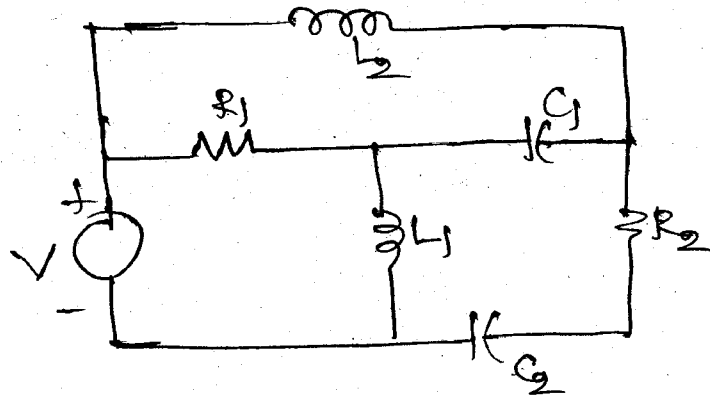
- 3 Attempt any three : 15
 (a) Explain duality. Obtain the dual of the given network.



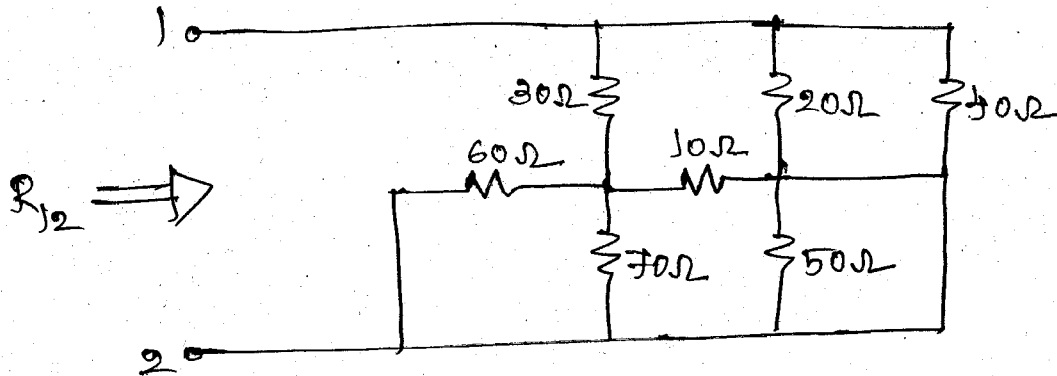
- (b) Find the equivalent resistance as viewed from terminals 1-2.



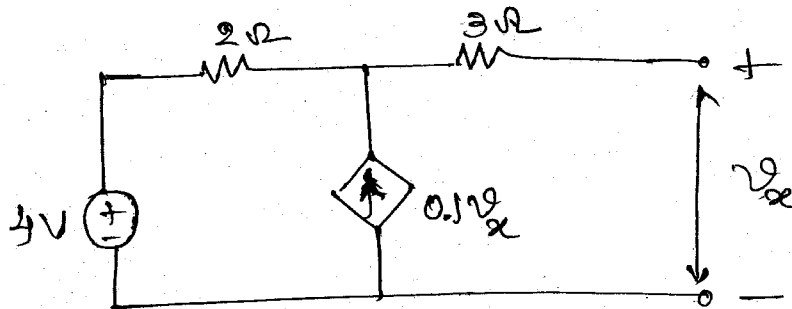
- (c) Obtain Thevenin's equivalent circuit for the network given below.



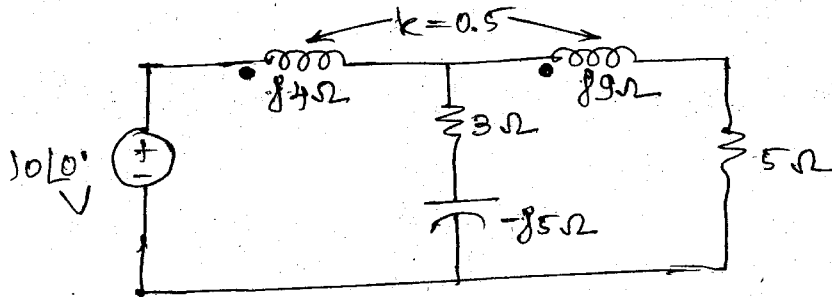- (d) Explain the term mutual inductance and compare with self inductance of coil.
 (e) Find the voltage across $3-j5\Omega$ branch for the given network.




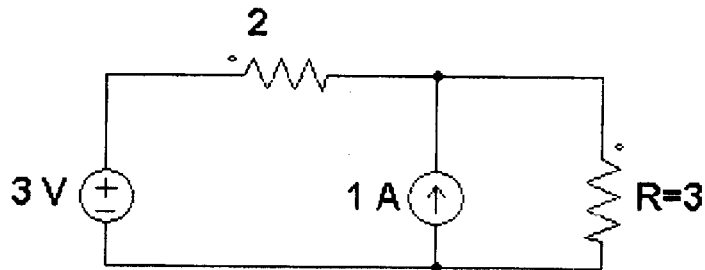- 4 (a) Attempt all (each question carries equal marks) 10
 (i) Find the current through Resistor R using Norton's theorem.



- (ii) Define and explain Final Value Theorem.
 (iii) Find the laplace transformation of $f(t) = t^n$.
 (iv) Find the laplace transformation of $f(t) = e^{-at}$.
 (v) State and explain superposition's theorem with example.

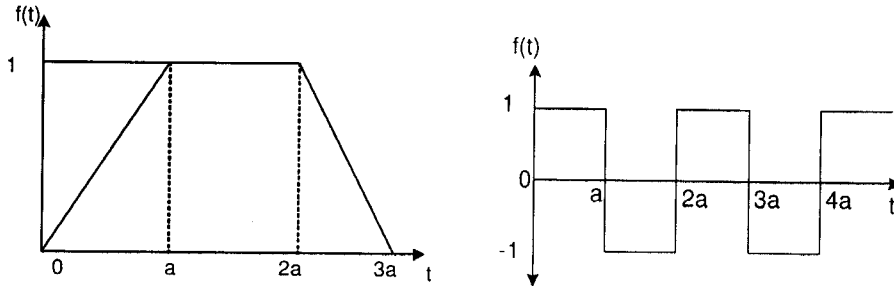- (b) Obtain the laplace transform of the following waveform : 5
- Non-recurring wave-form
 - Recurring wave-form



- (c) Obtain inverse laplace of the following functions : 5


(i) $F(s) = \frac{s+5}{s(s^2+2s+5)}$

(ii) $F(s) = \frac{3s^2+4}{s(s^2+4)}$

- 5 (a) For RLC circuit $Y(s) = \frac{s}{s^2+6s+25}$, find 7


- Damping factor
- Damping ratio
- Actual frequency of oscillation
- Bandwidth
- Q-factor
- Half power frequency
- Pole-zero location

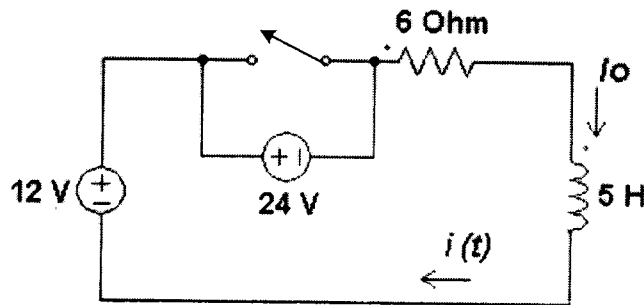- (b) Find the current in the circuit shown in the figure below at an instant t , after opening the switch if a current of 0.5 A had been passing through the circuit at the instant of opening. 8




OR

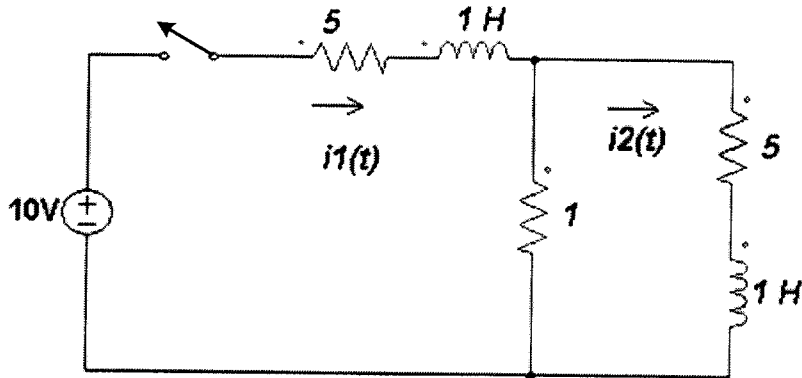- (b) Using Laplace Transform, find $i_2(t)$ at $t=0+$ following closing at $t=0$ of switch k . Assume initial conditions to be zero. 8



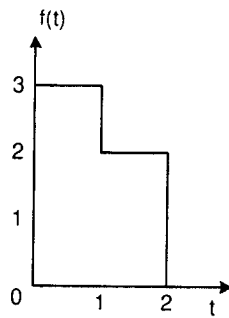
- 6 Attempt any three : 15
- (i) (a) Find the Laplace Transform of following waveform.




- (b) Draw the waveform from wave equation

$$f(t) = 5u(t-t_1) + 1u(t-t_2) - 10u(t-t_3)$$

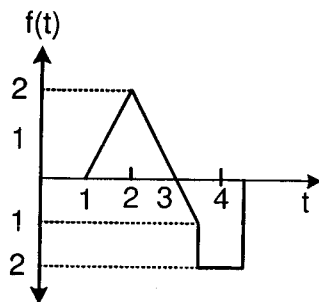- (ii) Define following and obtain its laplace transform
- (a) Unit step function
- (b) Unit impulse function
- (iii) Find the Laplace Transform of following waveform.




(a)

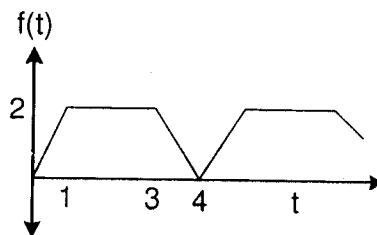

(b)

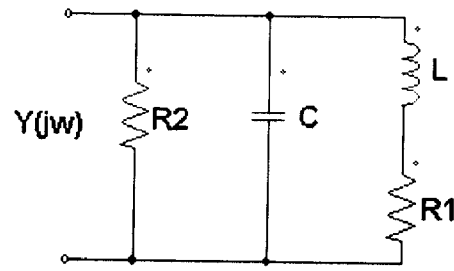(iv) Draw the polar plot of the following circuit.



(v) Prove convolution theorem to determine inverse Laplace transform.
