



R A N - 2 1 0 3 0 0 0 2 0 6 0 2 1 0 0 5

**RAN-2103000206021005****B.Sc. (Sem. VI) Examination October - 2023****Physics – X – PH-610 : Analog and Digital Electronics****[ Total Marks: 50****સૂચના : / Instructions**

(૧)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.  
Fill up strictly the details of signs on your answer book

Name of the Examination:

B.Sc. (Sem. VI)

Name of the Subject :

Physics – X – PH-610 : Analog and Digital Electronics

Subject Code No.: 2103000206021005

Seat No.:

Student's Signature

- (2) Draw neat diagrams wherever necessary.
- (3) Symbols used in the paper have their usual meaning.
- (4) Question 1 is compulsory and figures to the right indicate full marks of the question.

**Q. 1****Answer the following questions in short:****(10)**

1. Write voltage gain equation for non-inverting amplifier for an OP-amp.
2. Voltage gain is unity for buffer amplifier of an OP-amp. (True/False)
3. Define CMRR and slew rate.
4. What is differential and operational amplifier?
5. What is 555-timmer?
6. Full form of ICVS and VCIS in negative feedback amplifier.
7. Define multi-vibrator and duty cycle.
8. Write oscillation frequency equation of phase shift oscillator.
9. Write application of flip flop.
10. Write the name of types of flip flop.

- Q. 2 (A) Write anyone of the following. (06)**
- (1) Prove that voltage gain equation for inverting amplifier of an OP-amp is  

$$A_v = - \left( \frac{R_f}{R_i} \right)$$
  - (2) Write short note on instrumentation amplifier of an OP-amp.
- (B) Write anyone of the following. (04)**
- (1) What is common mode rejection ratio of an LF157A at low frequency? Convert this decibel value of an ordinary number.
  - (2) Write short note on summing amplifier of an OP-amp.
- Q. 3 (A) Write anyone of the following. (06)**
- (1) Define oscillator. Obtain an expression for the frequency of an oscillation for Colpitt oscillator using transistor.
  - (2) Write short note on Wein bridge oscillator.
- (B) Write anyone of the following. (04)**
- (1) Write short note on Astable mode 555-timmer.
  - (2) A Hartley oscillator like the one inductance  $L_1 = 1 \mu\text{H}$  and  $L_2 = 0.2 \mu\text{H}$ . What is the feedback fraction? The frequency of the oscillation if  $C = 1000 \text{ PF}$ ? The minimum voltage gain needed to start oscillation?
- Q. 4. (A) Write anyone of the following. (06)**
- (1) Prove that Pulse width equation  $W = 1.1RC$  for a mono-stable mode 555-timmer.
  - (2) Write a short note on Schmitt trigger of an arithmetic circuit.
- (B) Write anyone of the following. (04)**
- (1) Explain in brief clock waveform of an arithmetic circuit.
  - (2) Write short note on TTL-clock circuit of an arithmetic circuit.
- Q. 5 (A) Write anyone of the following. (06)**
- (1) Construct RS-flip flop using NOR gate with truth table.
  - (2) Write short note on JK-master-slave-flip flop using universal logic gate.
- (B) Write anyone of the following. (04)**
- (1) Construct D-flip flop Edge trigger.
  - (2) Construct Edge trigger JK-flip flop.