



RAN - 1803000201030091



RAN-1803000201030091

F. Y. B. Sc. (Sem. - I) Examination

March - 2023

Electronics : Paper - I

Basic Electrical Circuits

[Total Marks: 50

સૂચના : / Instructions

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fill up strictly the details of signs on your answer book

Name of the Examination:

F. Y. B. Sc. (Sem. - I)

Name of the Subject :

Electronics : Paper - I Basic Electrical Circuits

Subject Code No.: **1803000201030091**

Seat No.:

<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>
----------------------	----------------------	----------------------	----------------------	----------------------	----------------------

Student's Signature

- (2) Figure on right indicate full marks.
- (3) Non programmable Calculator is allowed.
- (4) All symbols and abbreviation have their usual meanings.
- (5) Assume Data if necessary.

***O.M.R. Sheet ભરવા અંગેની અગત્યની સૂચનાઓ આપેલ
O.M.R. Sheetની પાછળ છાપેલ છે.***

***Important instructions to fillup O.M.R. Sheet
are given on back side of the provided O.M.R. Sheet.***

Section - I

Each question carries 1 marks

(20)

- Q. 1.** How is a $3.9\text{ k}\Omega \pm 5\%$ resistor color-coded?
- a) Red, white, red, Gold b) Red, white, red, Silver
c) Red, white, red d) All
- Q. 2.** _____ is often used to analyze multiple source circuit.
- a) Thevenin's Theorem b) Superposition Theorem
c) Norton's Theorem d) Kirchhoff's Law
- Q. 3.** With Ohm's law, if voltage increases and the current increases:
- a) Can't say
b) Resistance increases
c) Resistance remains the same
d) Resistance decreases
- Q. 4.** What current is flowing in the circuit, with 12 V dc battery in series with $24\text{ k}\Omega$ resistor?
- a) 500A b) 500mA
c) $500\mu\text{A}$ d) None
- Q. 5.** Kirchhoff's Current Law, states that algebraic sum of _____ at _____ is zero.
- a) Voltage, junction b) voltage, Branch
c) Current, Junction d) Current, branch
- Q. 6.** For $P = V^2/R$, a increase in resistance should produce.
- a) A decrease in power b) An increase in power
c) An increase in Voltage d) A decrease in current

Q. 13. According to Norton's theorem, any network with two open terminals can be replaced by - _____ source in _____ with a single Resistance R_N .

- a) Current, parallel
- b) Current, series
- c) Voltage, series
- d) Voltage, parallel

Q. 14. Potentiometer is _____ terminal component and used to change.

- a) 3, Voltage
- b) 4, Current
- c) 2, Current
- d) 2, Voltage


Q. 15. A Capacitor stores 0.20 μ Coulomb of charge at 5 Volts. Its Capacitance is

- a) 0.04 F
- b) 0.4 μ F
- c) 0.04 μ F
- d) 4 μ F

Q. 16. A voltage is induced in a transformer secondary winding by the action of the:

- a) Secondary magnetic field
- b) Primary turns ratio
- c) Primary magnetic field
- d) Secondary counter emf

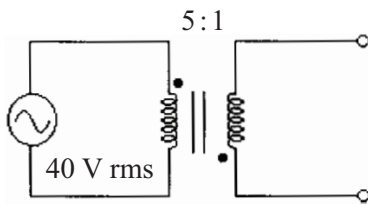Q. 17. What is the secondary voltage in the given circuit?




- a) 8 v rms out of phase
- b) 200 v out of phase
- c) 200 v in phase
- d) 8 v rms in phase

Q. 18. The Energy band of Valance band and Conduction band in Conductor, semiconductor and Insulator is _____ respectively.

- a) Little apart, Overlap, Far apart
- b) Far apart, Overlap, Little apart
- c) Overlap, Little apart, Far apart
- d) Little apart, Far apart, Overlap

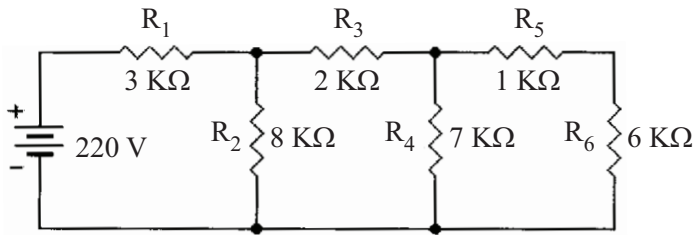Q. 25. What is the power dissipated by R2, R4, and R6?



- a) 1640mW, 758.57mW, 650.20mW
- b) 1640kW, 758.57kW, 650.20kW
- c) 1.640mW, 7.5857mW, 6.5020mW
- d) 16.40mW, 75.857mW, 65.020mW

Q. 26. With 42 voltage applied, If R1 is 10 Ω, R2 = 70 Ω and R3 = 30Ω, What is current of R2, If R1 is in series connected with parallel connection of R2 and R3.

- a) 406.45 mA
- b) 800 mA
- c) 600 mA
- d) 4.06mA

Q. 27. What are the values of resistors with colour codes: Brown, Black, Red and Brown, Black, Orange

- a) 1 K Ω, 10 K Ω
- b) 1 K Ω, 20 K Ω
- c) 10 K Ω, 1 K Ω
- d) 100 Ω, 10 Ω

Q. 28. In a series circuit with E = 40 V, R1 = 8Ω and the voltage drop across R2 is 15V. Find the Voltage drop across R1 and the resistance value of R2.

- a) 25 V, 4.8 Ω
- b) 10.5 V, 2.4 Ω
- c) 12.5 V, 2.4 Ω
- d) 11.5 V, 2.4 Ω

Q. 29. Which one of them is not active component?

- a) Diode
- b) Transistor
- c) Capacitor
- d) Zener Diode

SPACE FOR ROUGH WORK