



RAN - 1803000201030091



**RAN-1803000201030091**

**F. Y. B. Sc. (Sem. - I) Examination**

**March - 2023**

**Electronics : Paper - I**

**Basic Electrical Circuits**

**[ Total Marks: 50**

**સૂચના : / Instructions**

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.  
**Fill up strictly the details of signs on your answer book**

Name of the Examination:

**F. Y. B. Sc. (Sem. - I)**

Name of the Subject :

**Electronics : Paper - I Basic Electrical Circuits**

Subject Code No.: **1803000201030091**

Seat No.:

<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>
----------------------	----------------------	----------------------	----------------------	----------------------	----------------------

Student's Signature

- (2) Figure on right indicate full marks.
- (3) Non programmable Calculator is allowed.
- (4) All symbols and abbreviation have their usual meanings.
- (5) Assume Data if necessary.

***O.M.R. Sheet ભરવા અંગેની અગત્યની સૂચનાઓ આપેલ  
O.M.R. Sheetની પાછળ છાપેલ છે.***


***Important instructions to fillup O.M.R. Sheet  
are given on back side of the provided O.M.R. Sheet.***

**Section - I**

**Each question carries 1 marks**

**(20)**

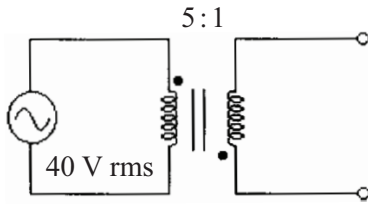**Q. 1.** What is the secondary voltage in the given circuit?



- a) 8 v rms out of phase
- b) 200 v out of phase
- c) 200 v in phase
- d) 8 v rms in phase

**Q. 2.** The Energy band of Valance band and Conduction band in Conductor, semiconductor and Insulator is \_\_\_\_\_ respectively.

- a) Little apart, Overlap, Far apart
- b) Far apart, Overlap, Little apart
- c) Overlap, Little apart, Far apart
- d) Little apart, Far apart, Overlap

**Q. 3.** In a series electronic circuit with  $E = 15 \text{ V}$ ,  $R_1 = 6 \Omega$  and  $R_2 = 5 \Omega$  the current is equal to

- a) 1.36 A
- b) 0.136 A
- c) 1.36 mA
- d) 0.00136

**Q. 4.** Three capacitor of value  $1 \mu\text{F}$ ,  $3 \mu\text{F}$  and  $8 \mu\text{F}$  are connected in series, what is its total Capacitance :

- a)  $6.66 \mu\text{F}$
- b)  $0.66 \mu\text{F}$
- c)  $12 \mu\text{F}$
- d)  $0.12 \mu\text{F}$

**Q. 5.** How is a  $3.9 \text{ k}\Omega \pm 5\%$  resistor color-coded?

- a) Red, white, red, Gold
- b) Red, white, red, Silver
- c) Red, white, red
- d) All

- Q. 6.** \_\_\_\_\_ is often used to analyze multiple source circuit.
- a) Thevenin's Theorem                      b) Superposition Theorem  
c) Norton's Theorem                      d) Kirchhoff's Law
- Q. 7.** With Ohm's law, if voltage increases and the current increases:
- a) Can't say  
b) Resistance increases  
c) Resistance remains the same  
d) Resistance decreases
- Q. 8.** What current is flowing in the circuit, with 12 V dc battery in series with 24k  $\Omega$  resistor?
- a) 500A                                      b) 500mA  
c) 500 $\mu$ A                                      d) None
- Q. 9.** Kirchhoff's Current Law, states that algebraic sum of \_\_\_\_\_ at \_\_\_\_\_ is zero.
- a) Voltage, junction                      b) voltage, Branch  
c) Current, Junction                      d) Current, branch
- Q. 10.** For  $P = V^2/R$ , a increase in resistance should produce.
- a) A decrease in power                      b) An increase in power  
c) An increase in Voltage                      d) A decrease in current
- Q. 11.** When a 1  $\mu$ F capacitor is connected to a 2 kHz source, what is its capacitive reactance?
- a) 0.796  $\Omega$                                       b) 796.10  $\Omega$   
c) 79.61 $\Omega$                                       d) 7.96  $\Omega$








**Q. 31.** How many amperes used by 60 watt, 120 V light bulb?

- a) 500 mA
- b) 0.5 mA
- c) 200 mA
- d) 2 mA

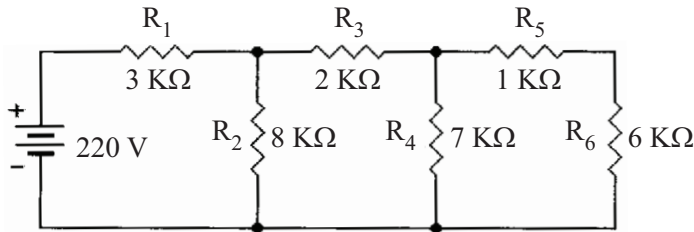**Q. 32.** What is the power dissipated by R2, R4, and R6?



- a) 1640mW, 758.57mW, 650.20mW
- b) 1640kW, 758.57kW, 650.20kW
- c) 1.640mW, 7.5857mW, 6.5020mW
- d) 16.40mW, 75.857mW, 65.020mW

**Q. 33.** With 42 voltage applied, If R1 is 10 Ω, R2 = 70 Ω and R3 = 30Ω, What is current of R2, If R1 is in series connected with parallel connection of R2 and R3.

- a) 406.45 mA
- b) 800 mA
- c) 600 mA
- d) 4.06mA

**Q. 34.** What are the values of resistors with colour codes: Brown, Black, Red and Brown, Black, Orange

- a) 1 K Ω, 10 K Ω
- b) 1 K Ω, 20 K Ω
- c) 10 K Ω, 1 K Ω
- d) 100 Ω, 10 Ω

**Q. 35.** In a series circuit with E = 40 V, R1 = 8Ω and the voltage drop across R2 is 15V. Find the Voltage drop across R1 and the resistance value of R2.

- a) 25 V, 4.8 Ω
- b) 10.5 V, 2.4 Ω
- c) 12.5 V, 2.4 Ω
- d) 11.5 V, 2.4 Ω

**SPACE FOR ROUGH WORK**